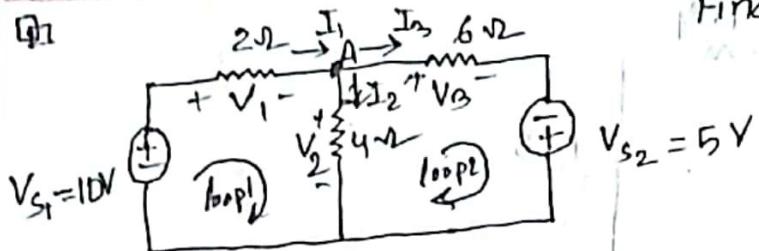


## Loop Analysis 2

Date : 02 - 07 - 2025

Q1



Find  $I_1, I_2, I_3, V_1, V_2, V_3$

Using KVL in loop 1,

$$-10 + 2I_1 + 4I_2 = 0$$

$$\Rightarrow 2I_1 + 4I_2 = 10 \quad \text{--- (1)}$$

KVL in loop 2,

$$-4I_2 + 6I_3 - 5 = 0$$

$$\Rightarrow 6I_3 - 4I_2 = 5 \quad \text{--- (2)}$$

Using KCL in node A,

$$I_1 = I_2 + I_3 \quad \text{--- (3)}$$

(1) in (3)  $\Rightarrow$

$$2I_2 + 2I_3 + 4I_2 = 10$$

$$\Rightarrow 6I_2 + 2I_3 = 10 \quad \text{--- (4)}$$

$$\Rightarrow 3I_2 + I_3 = 5$$



$$eq(11) \times 3 + eq(14) \times 4 \Rightarrow$$

$$-I_2 12 + I_3 18 = 15$$

$$I_2 12 + I_3 4 = 20$$

$$22I_3 = 35$$

$$\therefore I_3 = \frac{35}{22} = 1.59 A$$

Putting  $I_3 = 1.59 A$  in eq(11)

$$-I_2 4 + (1.59) \times 6 = 5$$

$$\therefore I_2 = 1.136 A$$


$$\therefore I_1 = 1.136 + 1.59 \\ = 2.73 A$$

Using Ohm's Law,

$$V_1 = I_1 2 = 2.73 \times 2 = 5.46 V$$

$$V_2 = I_2 4 = 1.136 \times 4 = 4.5 V$$

$$V_3 = I_3 6 = 1.59 \times 6 = 9.5 V$$

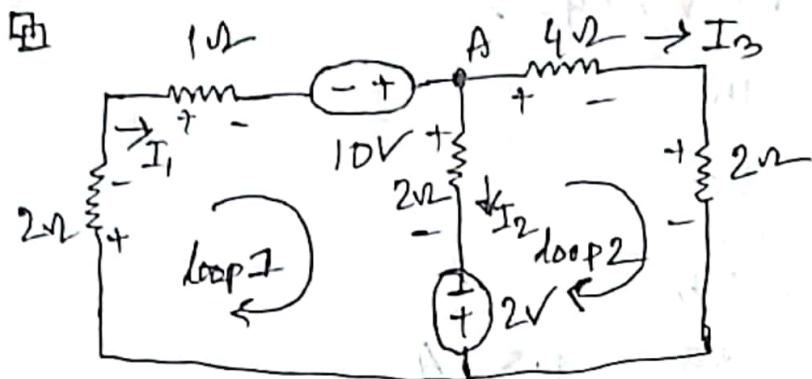

Using KVL in loop 1,

$$2I_1 + I_1 - 10 + 2I_2 - 2 = 0$$

$$\Rightarrow 3I_1 + 2I_2 = 12 \quad \textcircled{1}$$

Using KVL in loop 2,

$$2 - 2I_2 + 4I_3 + 2I_3 = 0$$

$$\Rightarrow -2I_2 + 6I_3 + 2 = 0$$

$$\Rightarrow 2I_2 - 6I_3 = 2 \quad \textcircled{II}$$

Using KCL in node A,

$$I_1 = I_2 + I_3 \quad \textcircled{III}$$

$\textcircled{III}$  in  $\textcircled{1} \Rightarrow$

$$3I_2 + 3I_3 + 2I_2 = 12$$

$$\Rightarrow 5I_2 + 3I_3 = 12 \quad \textcircled{IV}$$

$$eq\text{ (ii)} + eq\text{ (iv)} \times 2 \Rightarrow$$

$$2I_2 - 6I_3 = 2$$

$$10I_2 + 6I_3 = 24$$

$$12I_2 = 26$$

$$\Rightarrow I_2 = \frac{26}{12} = 2.17A$$

$$I_2 = 2.17A \text{ in } eq\text{ (ii)} \Rightarrow$$

$$2(2.17) - 6I_3 = 2$$


$$\Rightarrow 4.34 - 6I_3 = 2$$

$$\Rightarrow I_3 = \frac{2.34}{6} = 0.39A$$

$$\therefore I_1 = 2.17 + 0.39$$

$$= 2.56A$$

## Mesh Analysis 4

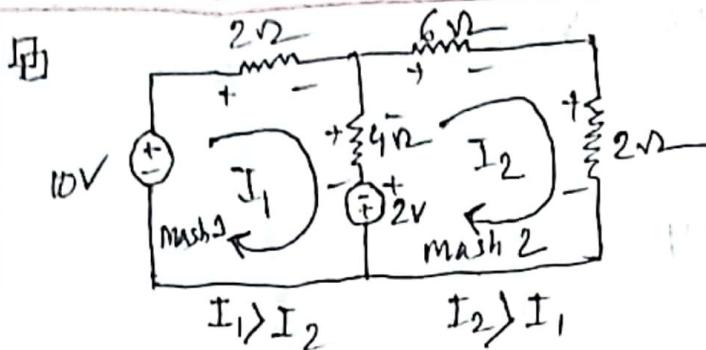

Applying KVL in mesh 1:

$$-10 + 2I_1 + 4(I_1 - I_2) - 2 = 0$$

$$\Rightarrow -10 + 2I_1 + 4I_1 - 4I_2 - 2 = 0$$

$$\Rightarrow 6I_1 - 4I_2 = 12 \quad \text{--- (1)}$$

Applying KVL in mesh 2:

$$2 + 4(I_2 - I_1) + 6I_2 + 2I_2 = 0$$

$$\Rightarrow 2 + 4I_2 - 4I_1 + 6I_2 + 2I_2 = 0$$

$$\Rightarrow -4I_1 + 12I_2 = -2$$

$$\Rightarrow 4I_1 - 12I_2 = 2 \quad \text{--- (2)}$$

$$(1) \times 3 - (2) \Rightarrow$$

$$18I_1 - 12I_2 = 36$$

$$\begin{array}{r} 4I_1 - 12I_2 = 2 \\ (-) \quad (+) \end{array} \xrightarrow{\quad} \frac{14I_1 = 34}{14I_1 = 34}$$

$$\therefore I_1 = 2.4 \text{ A}$$

Type - 4

$$I_1 = 2.4 \text{ A} \quad \text{in eq (11)} \Rightarrow$$

$$4(2.4) - 12I_2 = 2$$

$$\Rightarrow I_2 = \frac{7.6}{12}$$

$$\therefore I_2 = 0.6 \text{ A}$$

~~Type-2~~ Using Cramen's rule,

$$\begin{bmatrix} 3 & -2 \\ -2 & 6 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 6 \\ -1 \end{bmatrix}$$


$$\Delta = \begin{bmatrix} 3 & -2 \\ -2 & 6 \end{bmatrix} = 14$$

$$\Delta_1 = \begin{bmatrix} 6 & -2 \\ -1 & 6 \end{bmatrix} = 34$$

$$\Delta_2 = \begin{bmatrix} 3 & 6 \\ -2 & -1 \end{bmatrix} = 9$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{34}{14} = 2.4$$
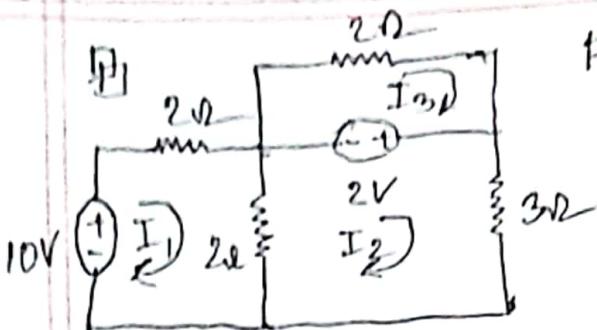
$$I_2 = \frac{\Delta_2}{\Delta} = \frac{9}{14} = 0.6$$



find mesh current and power across  $3\Omega$  resistor.

Using KVL in mesh 1,

$$-10 + 2I_1 + 2(I_1 + I_2) = 0$$

$$\Rightarrow -10 + 2I_1 + 2I_1 - 2I_2 = 0$$

$$\Rightarrow 4I_1 - 2I_2 = 10 \quad \text{--- (1)}$$

Using KVL in mesh 2,

$$2(I_2 - I_1) - 2 + 3I_2 = 0$$

$$\Rightarrow 2I_2 - 2I_1 - 2 + 3I_2 = 0$$

$$\Rightarrow -2I_1 + 5I_2 - 2 = 0$$

$$\Rightarrow 2I_1 - 5I_2 = -2 \quad \text{--- (11)}$$

$$\text{eq(1)} - \text{eq(11)} \times 2 \Rightarrow$$

$$4I_1 - 2I_2 = 10$$

$$\underline{\underline{(+) \frac{4I_1 - 10I_2}{(-)}}}$$

$$8I_2 = 12$$

$$\therefore I_2 = 1.5 \text{ A}$$

Using KVL in mesh 3,

$$2 + 2I_3 = 0$$

$$\Rightarrow I_3 = -1$$

$I_2 = 1.5A$  in eq(1)  $\Rightarrow$  value of  $I_1$  is 1.5

$$4I_1 - 2(1.5) = 10$$

$$\Rightarrow 4I_1 = 13$$

$$\therefore I_1 = 3.25 A$$

$$P = I_2^2 R$$
$$= (1.5)^2 \times 3$$
$$= 6.75 W$$

A shorted load current

$$I_L = 100 \text{ A}$$

At different voltage


With shorted load current

At  $I_L = 100A$

$I_1 = 3.25 A$

$I_2 = 1.5 A$

current

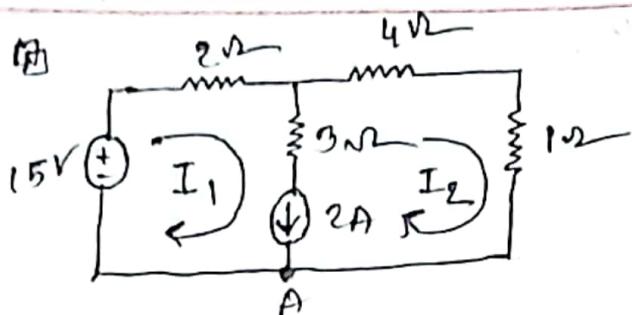

Using KVL in mesh 1,

$$-15 + 2I_1 + 3(I_1 - I_2) + 2 = 0 \quad (1)$$


$$\Rightarrow -15 + 2I_1 + 3I_1 - 3I_2 + 2 = 0 \quad (1) \rightarrow 5I_1 - 3I_2 = 13$$

$$\Rightarrow 5I_1 - 3I_2 = 13 \quad \text{--- (1)}$$

Using KVL in supermesh,

$$-15 + 2I_1 + 4I_2 + I_2 = 0$$
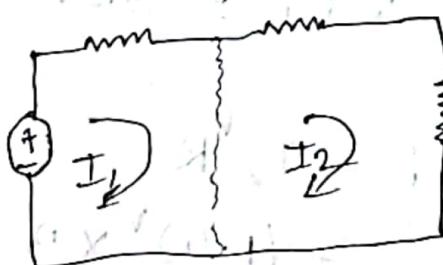
$$\Rightarrow 2I_1 + 5I_2 = 15 \quad \text{--- (2)}$$



Applying KCL at node A,

$$I_1 = 2 + I_2 \quad \text{--- (3)}$$


$$I_1 = 2 + I_2 \text{ in eq (1)} \Rightarrow$$

$$2(2 + I_2) + 5I_2 = 15 \quad \left| \begin{array}{l} \therefore I_1 = 2 + 1.5x \\ = 3.5x \end{array} \right.$$

$$\Rightarrow 4 + 2I_2 + 5I_2 = 15$$

$$\Rightarrow 7I_2 = 11$$

$$\therefore I_2 = 1.57A$$

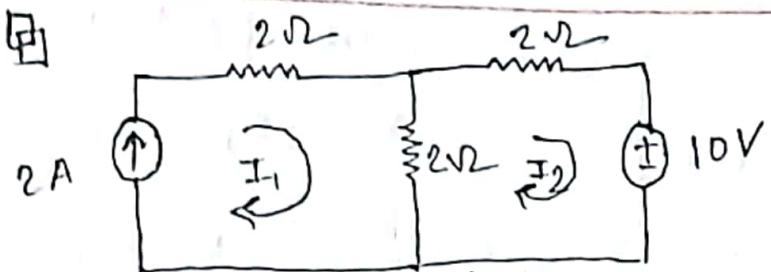

Using KVL in mesh 1

$$2I_1 + 2(I_1 - I_2) = 0$$

$$\Rightarrow 2I_1 + 2I_1 - 2I_2 = 0$$

$$\Rightarrow 4I_1 - 2I_2 = 0 \quad \text{--- (1)}$$

From mesh 1,

$$I_1 = 2A$$

Using KVL in mesh 2,

$$10 + 2(I_2 - I_1) + 2I_2 = 0$$

$$\Rightarrow 10 + 2I_2 - 2I_1 + 2I_2 = 0$$

$$\Rightarrow 4I_2 - 2I_1 = -10$$


$$\Rightarrow 4I_2 = -6$$

$$\Rightarrow I_2 = -\frac{6}{4} = -1.5A$$

Practice

## Nodal Analysis

**6**

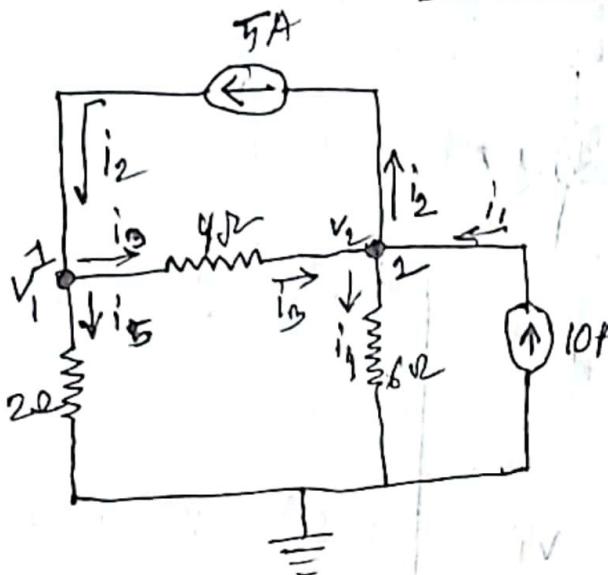

$$i_0 = \frac{v_1 - v_2}{4}$$

$$i_2 = 5A$$

$$i_1 = 10A$$

$$i_4 = \frac{v_2}{6}$$

$$i_5 = \frac{v_1}{2}$$

Applying KCL in node 1,

$$i_2 = i_3 + i_5$$

$$\Rightarrow 5 = \frac{v_1 - v_2}{4} + \frac{v_1}{2}$$

$$\Rightarrow 5 = \frac{v_1}{4} - \frac{v_2}{4} + \frac{v_1}{2}$$

$$\Rightarrow 5 = \frac{1}{4} (v_1 - v_2 + 2v_1)$$

$$\Rightarrow 5 = \frac{1}{4} (3v_1 - v_2)$$

$$\Rightarrow 3v_1 - v_2 = 20 \quad \text{---(1)}$$

$$\therefore \text{eq (solve)} \Rightarrow v_1 = 13.33V$$

$$v_2 = 20V$$

Applying KCL in node 2,

$$i_1 + i_3 = i_2 + i_4$$


$$\Rightarrow 10 + \frac{v_1 - v_2}{4} = 5 + \frac{v_2}{6}$$

$$\Rightarrow$$

$$\Rightarrow$$

$$\Rightarrow 3v_1 + 5v_2 = -60 \quad \text{---(2)}$$

Q) Determine the node voltage.

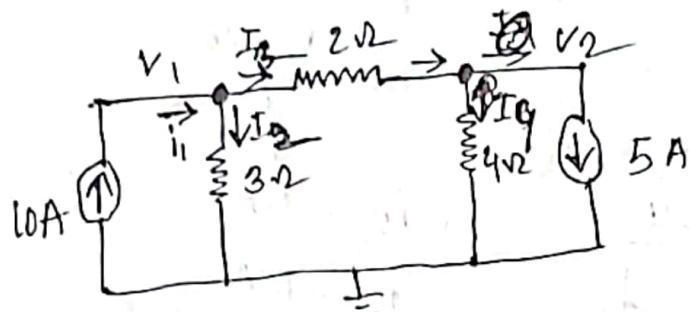

Applying KCL in node 1,

$$i_1 = i_2 + i_3$$

$$\Rightarrow 10 = \frac{V_1 - V_2}{2} + \frac{V_1}{3}$$

$$\Rightarrow 10 = \frac{V_1}{2} - 10 + \frac{V_1}{3}$$

$$\Rightarrow \frac{2V_1}{3} = 20 \Rightarrow V_1 = 60$$

Applying KCL in node 2,

$$i_2 = I_4 + 5$$

$$\Rightarrow 10 = \frac{V_2}{4} + 5$$

$$\Rightarrow \frac{V_2}{4} = 10 - 5$$

$$\Rightarrow V_2 = 20 \text{ V}$$

Applying KCL in node 1,

$$i_1 = 10 \text{ A}$$

$$i_1 = i_2 + i_3$$

$$i_2 = \frac{v_1}{3}$$

$$\Rightarrow 10 = \frac{v_1}{3} + \frac{v_1 - v_2}{2}$$

$$i_3 = \frac{v_1 - v_2}{2}$$

$$\Rightarrow 5v_1 - 3v_2 = 60 \quad \textcircled{1}$$

$$i_4 = \frac{v_2}{4}$$

$$i_5 = 5 \text{ A}$$

Applying KCL at node 2,

$$i_3 = i_4 + i_5 = pi$$

$$\Rightarrow \frac{v_1 - v_2}{2} = \frac{v_2}{4} + 5$$

$$\Rightarrow \frac{v_1}{2} - \frac{v_2}{2} - \frac{v_2}{4} = 5$$


$$\Rightarrow \frac{1}{4}(2v_1 - 2v_2 - v_2) = 5$$

$$\Rightarrow 2v_1 - 3v_2 = 20 \quad \textcircled{11}$$

eq (solve)  $\Rightarrow$

$$v_1 = ?$$

$$v_2 = ?$$

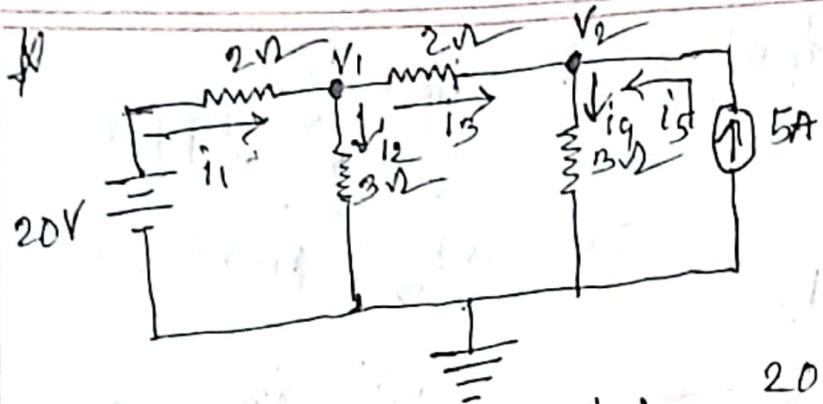

KCL at node 1,

$$i_1 = i_2 + i_3$$

$$\Rightarrow \frac{20 - V_1}{2} = \frac{V_1}{3} + \frac{V_1 - V_2}{2}$$

$$\Rightarrow 10 = \frac{V_1}{2} + \frac{V_1}{3} + \frac{V_1}{2} - \frac{V_2}{2}$$

$$\Rightarrow 10 = \frac{1}{6}(5V_1 + 2V_1 + 3V_1 - 3V_2)$$

$$\Rightarrow 60 = 8V_1 - 3V_2 \quad \text{(1)}$$

$$i_1 = \frac{20 - V_1}{2}$$

$$i_2 = \frac{V_1}{3}$$

$$i_3 = \frac{V_1 - V_2}{2}$$

$$i_4 = \frac{V_2}{3}$$

$$i_5 = 5A$$

KCL at node 2,

$$i_3 + i_5 = i_4$$

$$V_1 = 12.58 \text{ V}$$

$$V_2 = 13.55 \text{ V}$$

$$\Rightarrow \frac{V_1 - V_2}{2} + 5 = \frac{V_2}{3}$$


$$\Rightarrow \frac{V_1}{2} - \frac{V_2}{2} + 5 = \frac{V_2}{3}$$

$$\Rightarrow \frac{V_1}{2} - \frac{V_2}{2} - \frac{V_2}{3} + 5 = 0$$

$$\Rightarrow \frac{1}{6}(3V_1 - 3V_2 - 2V_2) = -5$$

$$\Rightarrow 3V_1 - 5V_2 = -30 \quad \text{(2)}$$

Q1

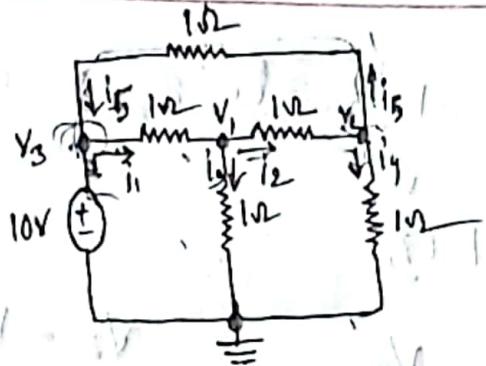

Applying KCL at node 3,  
 $i_1 = i_5$

$$V_3 = 10 \text{ V}$$

$$\Rightarrow \frac{V_3 - V_1}{1} = \frac{V_2 - V_3}{1}$$

$$\Rightarrow V_3 - V_1 = V_2 - V_3$$

$$\Rightarrow 10 - V_1 = V_2 - 10$$

$$\Rightarrow -V_1 - V_2 = -10 - 10$$

$$\Rightarrow V_1 + V_2 = 20 \quad \text{--- (1)}$$

Applying KCL at node 1,

$$i_1 = i_2 + i_3$$

$$\Rightarrow \frac{V_3 - V_1}{1} = \frac{V_1 - V_2}{1} + \frac{V_1}{1}$$

$$\Rightarrow 10 - V_1 = V_1 - V_2 + V_1$$

$$\Rightarrow 3V_1 - V_2 = 10 \quad \text{--- (2)}$$

Applying KCL at node 2,

$$i_2 = i_4 + i_5$$

$$\Rightarrow \frac{V_1 - V_2}{1} = \frac{V_2}{1} + \frac{V_2 - V_3}{1}$$

$$\Rightarrow V_1 - V_2 = V_2 + V_2 - 10$$

$$\Rightarrow V_1 - 2V_2 = -10 \quad \text{--- (1)}$$

$$01 - 2V + V = V - 01$$

$$01 - 01 - V + V = 0$$

$$01 = V - V \quad (2)$$


Subtract eqn (2) from (1),

$$2V + 2V = 0$$

$$\frac{01}{1} + \frac{2V - V}{1} = \frac{V - V}{1} \quad (3)$$

$$01 + 0V - 0V = V - 01 \quad (3)$$

$$01 = V - V \quad (3)$$

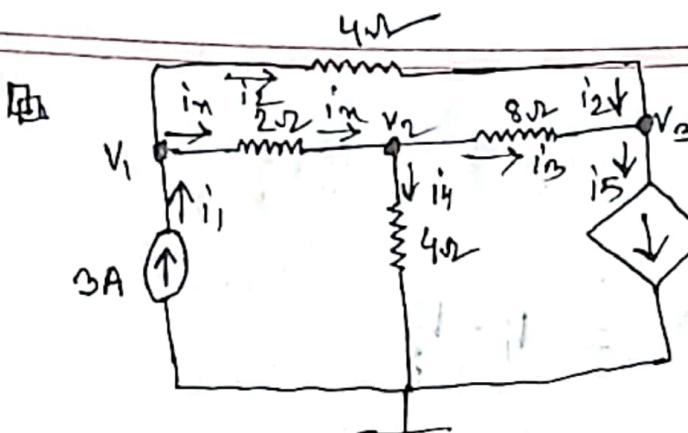

$$i_1 = 3A$$

$$i_n = \frac{V_1 - V_2}{2}$$

$$i_2 = \frac{V_1 - V_3}{8}$$

Applying KCL in node-1,

$$i_1 = i_2 + i_n$$

$$\Rightarrow 3 = \frac{V_1 - V_3}{4} + \frac{V_1 - V_2}{2}$$

$$\Rightarrow i_2 = V_1 - V_3 + 2V_1 - 2V_2$$

$$\Rightarrow i_2 = 3V_1 - 3V_2$$

$$\Rightarrow V_1 - V_2 = 4$$

$$\Rightarrow 3V_1 - 2V_2 - V_3 = 12 \quad \text{--- (1)}$$

Applying KCL in node-2,

$$i_n = i_3 + i_4$$

$$\Rightarrow \frac{V_1 - V_2}{2} = \frac{V_2 - V_3}{8} + \frac{V_2}{4}$$

$$\Rightarrow 4V_1 - 4V_2 = V_2 - V_3 + 2V_2$$

$$\Rightarrow 4V_1 - 4V_2 - V_2 + V_3 - 2V_2 = 0$$

$$\Rightarrow 4V_1 - 2V_2 + V_3 = 0 \quad \text{--- (11)}$$

KCL at node - 3

$$i_2 + i_3 = i_5$$

$$\Rightarrow \frac{V_1 - V_3}{4} + \frac{V_2 - V_3}{8} = V_1 - V_2$$

$$\Rightarrow 2V_1 - 2V_3 + V_2 - V_3 = 8V_1 - 8V_2$$

$$\Rightarrow 2V_1 - 2V_3 + V_2 - V_3 - 8V_1 + 8V_2 = 0$$

$$\Rightarrow 2V_1 - 3V_2 + V_3 = 0 \quad \text{(III)}$$

Using Cramen's rule,

$$\begin{bmatrix} 3 & -2 & -1 \\ 4 & -8 & 1 \\ 2 & -3 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 3 & -2 & -1 \\ 4 & -8 & 1 \\ 2 & -3 & 1 \end{bmatrix} = \Delta_3 = \begin{bmatrix} 3 & -2 & 12 \\ 4 & -8 & 0 \\ 2 & -3 & 0 \end{bmatrix} = 24$$

$$\Delta_1 = \begin{bmatrix} 12 & -2 & -1 \\ 0 & -8 & 1 \\ 0 & -3 & 1 \end{bmatrix} = -48 \quad \Delta = 3(-7+3) + 2(4-2) - 1(-12+14)$$


$$\Delta_2 = \begin{bmatrix} 3 & 12 & -1 \\ 4 & 0 & 1 \\ 2 & 0 & 1 \end{bmatrix} = -24 \quad = -12 + 4 - 2 = -10$$

$$V_1 = \frac{A_1}{\Delta} = \frac{-48}{-10} = 4.8V$$

$$V_2 = \frac{A_2}{\Delta} = \frac{-24}{-10} = 2.4V$$

$$V_3 = \frac{A_3}{\Delta} = \frac{24}{-10} = -2.4V$$

Q4

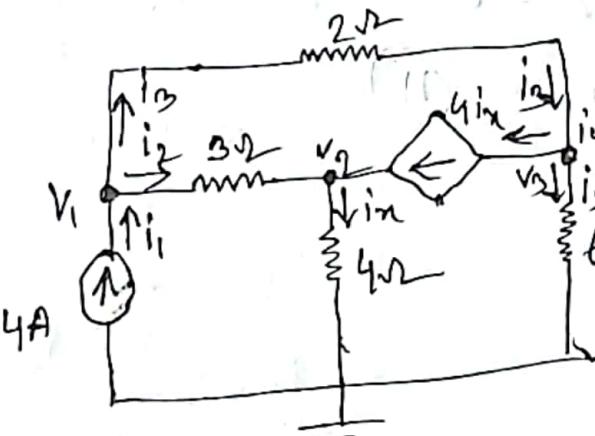

$$i_1 = 4A$$

Applying KCL in node 1,

$$i_2 = \frac{V_1 - V_2}{3}$$

$$i_1 = i_2 + i_3$$

$$i_3 = \frac{V_1 - V_3}{2}$$

$$\Rightarrow 4 = \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{2}$$

$$i_4 = 4im$$

$$\Rightarrow 24 = 2V_1 - 2V_2 + 3V_1 - 3V_3 \quad \therefore 4 \cdot \frac{V_2}{4} = V_2$$

$$\Rightarrow 24 = 5V_1 - 2V_2 - 3V_3$$

$$i_m = \frac{V_2}{4}$$

$$\Rightarrow 5V_1 - 2V_2 - 3V_3 - 24 = 0$$

$$i_5 = \frac{V_3}{6}$$

KCL in node - 2,

$$i_2 + i_4 = i_m$$

$$\Rightarrow \frac{v_1 - v_2}{3} + v_2 = \frac{v_2}{4}$$

$$\Rightarrow 4v_1 - 4v_2 + 12v_2 - 3v_2 = 0$$

$$\Rightarrow 4v_1 + 8v_2 - 3v_2 = 0$$

$$\Rightarrow 4v_1 + 5v_2 = 0 \quad \text{--- (11)}$$

KCL in node - 3,

$$i_3 = i_4 + i_5$$

$$\Rightarrow \frac{v_1 - v_3}{2} = v_2 + \frac{v_3}{6}$$

$$\Rightarrow 3v_1 - 3v_3 = 6v_2 + v_3$$

$$\Rightarrow 3v_1 - 3v_3 - 6v_2 - v_3 = 0$$

$$\Rightarrow 3v_1 - 6v_2 - 4v_3 = 0 \quad \text{--- (11)}$$

~~22~~  
 117

$$\Delta = \begin{bmatrix} 5 & -2 & -3 \\ 4 & 5 & 0 \\ 3 & -6 & -4 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 24 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{aligned} \Delta &= \begin{bmatrix} 5 & -2 & -3 \\ 4 & 5 & 0 \\ 3 & -6 & -4 \end{bmatrix} \\ &= 5(-20) + 2(-16) - 3(-24 - 15) \\ &= -100 - 32 + 117 \\ &= -15 \end{aligned}$$

$$\begin{aligned} \Delta_1 &= \begin{bmatrix} 24 & -2 & -3 \\ 0 & 5 & 0 \\ 0 & -6 & -4 \end{bmatrix} \\ &= 24(-20) + 2(0) - 3(0) \\ &= -480 \end{aligned}$$

$$\begin{aligned} \Delta_2 &= \begin{bmatrix} 5 & 24 & -3 \\ 4 & 0 & 0 \\ 3 & 0 & -4 \end{bmatrix} \\ &= 5(0) - 24(-16) - 3(0) \\ &= 384 \end{aligned}$$


$$\begin{aligned} \Delta_3 &= \begin{bmatrix} 5 & -2 & 24 \\ 4 & 5 & 0 \\ 3 & -6 & 0 \end{bmatrix} \\ &= 5(0) + 2(0) + 24(-24 - 15) \\ &= -936 \end{aligned}$$

$$v_1 = \frac{\Delta_1}{\Delta} = \frac{-480}{-15} = 32$$

$$v_2 = \frac{\Delta_2}{\Delta} = \frac{384}{-15} = -25.6$$

$$v_3 = \frac{\Delta_3}{\Delta} = \frac{-936}{-15} = 62.4$$
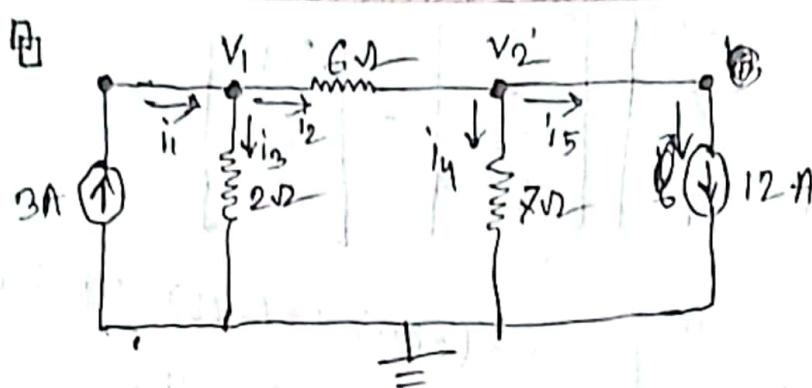
$$1 + \frac{6}{7} \\ \Rightarrow \frac{13}{7}$$



KCL at node 1,

$$i_1 = i_2 + i_3$$

$$\Rightarrow 3 = \frac{v_1 - v_2}{6} + \frac{v_1}{2}$$

$$\Rightarrow 18 = v_1 - v_2 + 3v_1$$

$$\Rightarrow 4v_1 - v_2 = 18 \quad \text{--- (1)}$$

KCL at node 2,

$$i_2 = i_4 + i_5$$

$$\Rightarrow \frac{v_1 - v_2}{6} = \frac{v_2}{7} + 12$$

$$\Rightarrow v_1 - v_2 = \frac{6}{7}v_2 + 72$$

$$\Rightarrow v_1 - v_2 - \frac{6}{7}v_2 = 72$$

$$\Rightarrow v_1 - \frac{13}{7}v_2 = 72$$

$$i_1 = 3A$$

$$i_2 = \frac{v_1 - v_2}{6}$$

$$i_3 = \frac{v_1}{2}$$

$$i_4 = \frac{v_2}{7}$$

$$i_5 = \underline{\underline{v_2 - v_1}}$$

$$i_5 = 12A$$

KCL at node 3,

$$\Delta = \begin{bmatrix} 4 & -1 \\ 1 & -\frac{13}{x} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 18 \\ 72 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 4 & -1 \\ 1 & -\frac{13}{x} \end{bmatrix} = -x \cdot 4 + 1 = -6 \cdot 4$$

$$\Delta_1 = \begin{bmatrix} 18 & -1 \\ 72 & -\frac{13}{x} \end{bmatrix} = -33 \cdot 4 + 72 = 38.6$$


$$\Delta_2 = \begin{bmatrix} 4 & 18 \\ 1 & 72 \end{bmatrix} = 288 - 18 = 270$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{38.6}{-6.4} = -6 \text{ V}$$


$$V_2 = \frac{\Delta_2}{\Delta} = \frac{270}{-6.4} = -42.2 \text{ V}$$

# Super Node

Q)

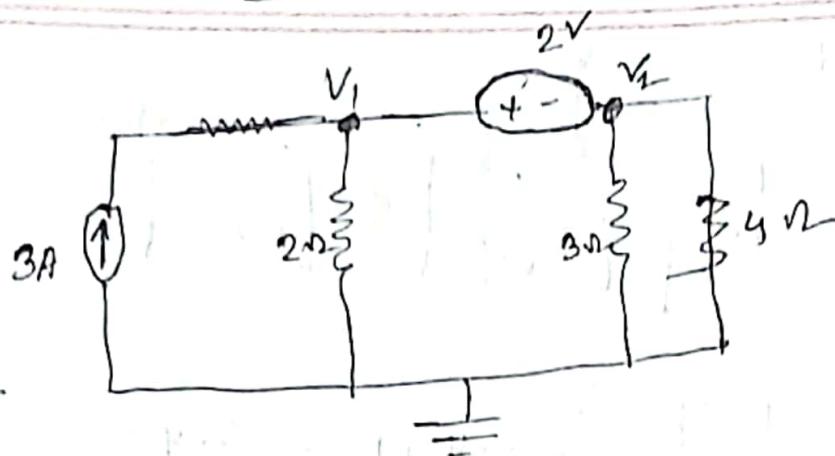

Solve

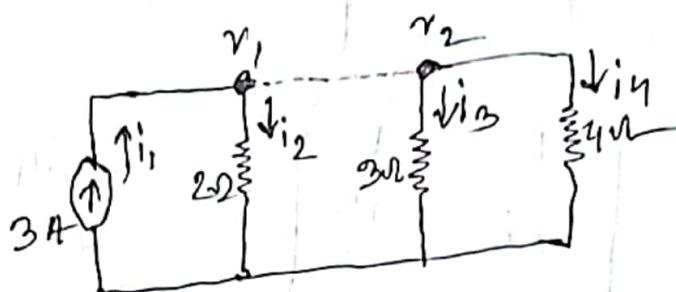

Applying KCL at super node,

$$i_1 = i_2 + i_3 + i_4$$

$$\Rightarrow 3 = \frac{V_1}{2} + \frac{V_2}{3} + \frac{V_2}{4}$$

$$\Rightarrow 6V_1 + 7V_2 = 36 \quad \text{--- (1)}$$


Applying KVL,


$$-V_1 + 2 + V_2 = 0$$

$$\Rightarrow V_1 - V_2 = 2 \quad \text{--- (2)}$$

$$V_1 = 3.84V$$


$$V_2 = 1.82V$$

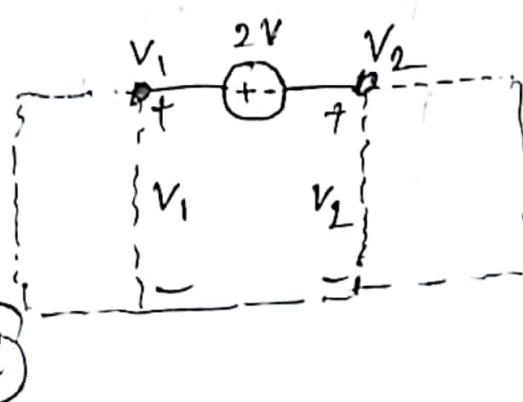

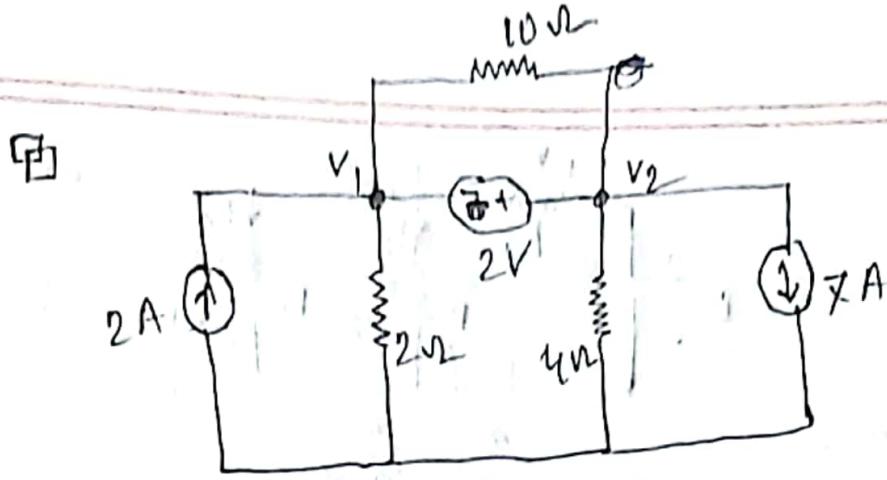

Solve

Applying KCL at  
super node,

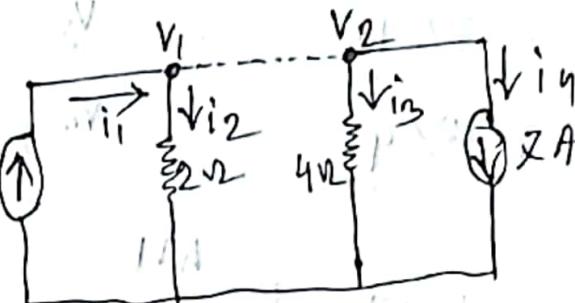

$$i_1 = i_2 + i_3 + i_y$$

$$\Rightarrow 2 = \frac{V_1}{2} + \frac{V_2}{4} + \cancel{i_y}$$

$$\Rightarrow 8 = 2V_1 + V_2 + \cancel{4V_2} \Rightarrow 2V_1 + V_2 = -20 \quad \textcircled{1}$$

~~$$\Rightarrow 56 = 14V_1 + 8V_2 + 4V_2$$~~

~~$$\Rightarrow 14V_1 + 11V_2 = 56 \quad \textcircled{1}$$~~


Applying KVL,

$$-V_1 - 2 + V_2 = 0$$

$$\Rightarrow V_2 - V_1 = 2$$

$$V_1 = -7.34$$

$$V_2 = -5.3$$

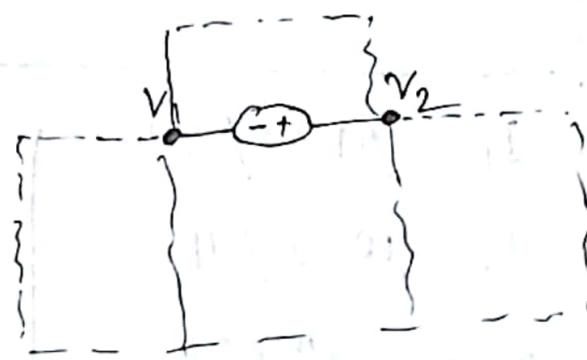

$$V = 3^{\vee}$$

$$R_1 = 97.88$$

$$R_2 = 98.9$$

$$R_3 = 98.2$$

$$I_1 = \frac{5}{30} / \frac{5}{18}$$


$$I_2 = \frac{7}{11} / \frac{10}{10}$$

$$I_3 = 12 / 4$$

$$I_1 = I_2 + I_3$$

$$\Rightarrow 18 \neq 14$$

$$\Rightarrow 30 \neq 19$$

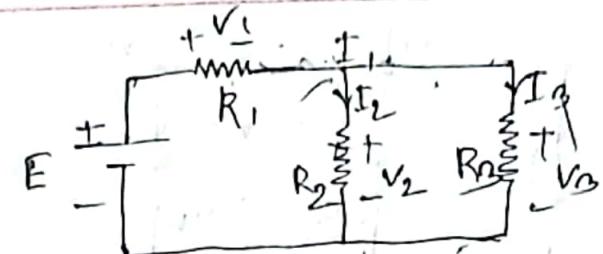

$$V_1 = 2.3 / 3.7$$

$$V_2 = 0.9 / 1.3$$

$$V_3 = 0.7 / 1.1$$

KVL

$$-E +$$

$$I_1 = 2.9 \text{ mA} \quad \frac{3}{24.25}$$

$$I_2 = 7 \text{ mA} \quad \frac{10}{16}$$

$$I_3 = 13 \text{ mA} \quad \frac{12}{18.23}$$

$$I_1 = 2.9 \text{ mA}$$

$$I_2 = 7 \text{ mA}$$

$$I_3 = 13 \text{ mA}$$

$$I_1 = 31$$

$$I_2 = 10$$

$$I_3 = 29$$

$$I_1 = 21.22 / 3.3$$

$$V_1 = 2.3 / 3.7$$

$$R_1 = 97.8$$

$$I_2 = 10.7 / 11$$


$$V_2 = 0.9 / 1.3$$

$$R_2 = 98.9$$

$$I_3 = 13 / 20$$

$$V_3 = 0.7 / 1.1$$

$$R_3 = 48.2$$

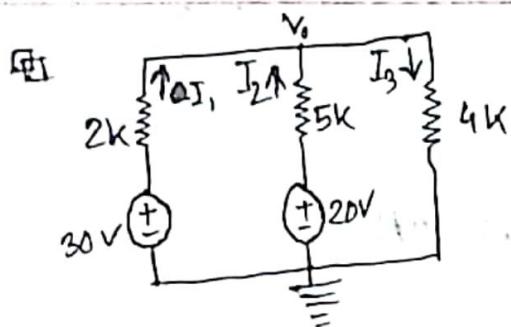


Applying KCL,

$$I_1 + I_2 = I_3$$



~~Super Position Theorem~~

5

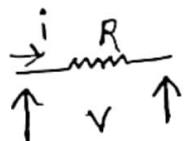

$$V = iR \quad [R=2]$$

$$\Rightarrow V = 2i$$

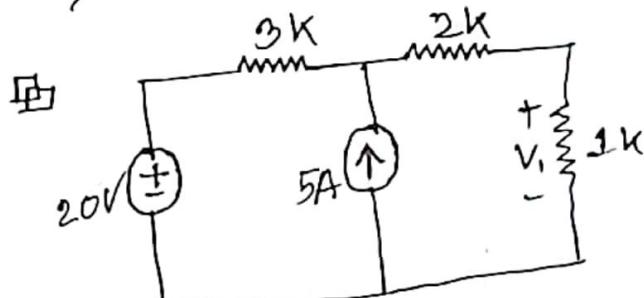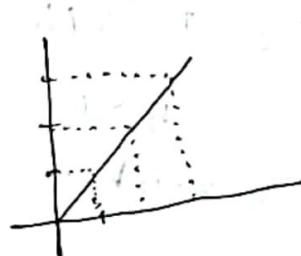

$$[V_i = V_i' + V_i'']$$

[current - open  
voltage - short]

Solve

Fig - 1 using VDR,

$$V_i' = \frac{20 \times 1}{3+2+1} = 3.3V$$

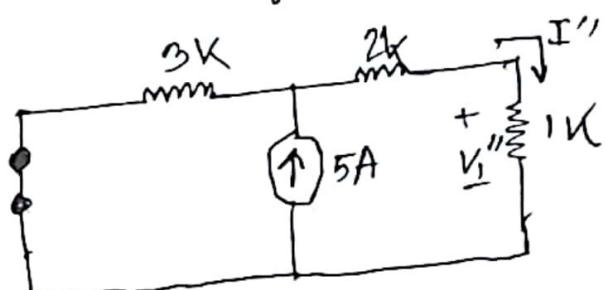
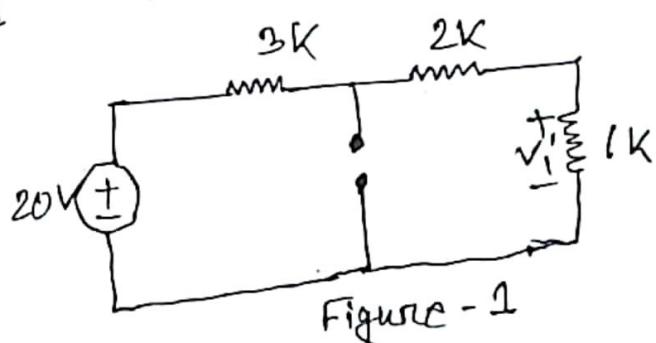


Figure - 2

Fig-2

Using CDR,

$$I'' = \frac{5 \times (2+1)}{3+(2+1)} = 2.5 \text{ mA}$$


Using Ohm's Law,

$$\begin{aligned} V_1'' &= I'' \times 1k \\ &= 2.5 \times 1 \\ &= 2.5 \text{ V} \end{aligned}$$

$$V_1 = V_1' + V_1''$$

$$= 3.3 + 2.5$$

$$= 5.8 \text{ V}$$

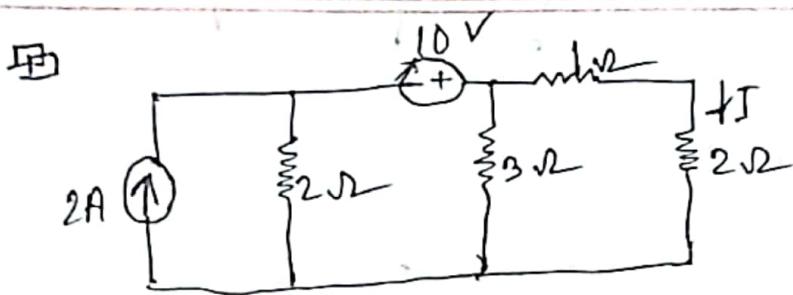

Solve

Fig 1.

Using CDR,

$$I' = \frac{2 \times 3}{3 + (2+1)}$$

$$= \frac{6}{6} = 1A$$


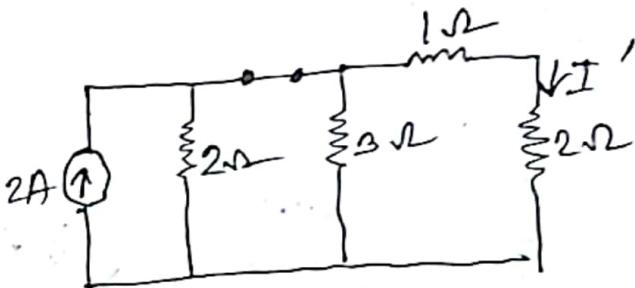


Fig - 2,

Using CDR,

$$I'' =$$

Using VDR,

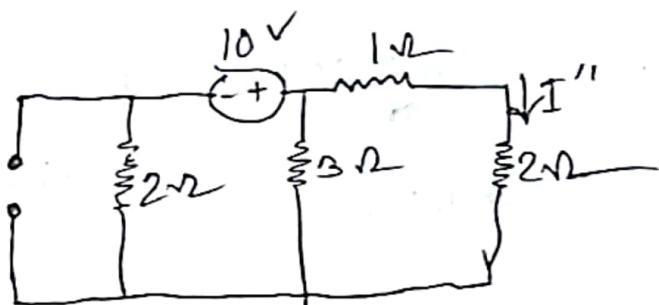

V

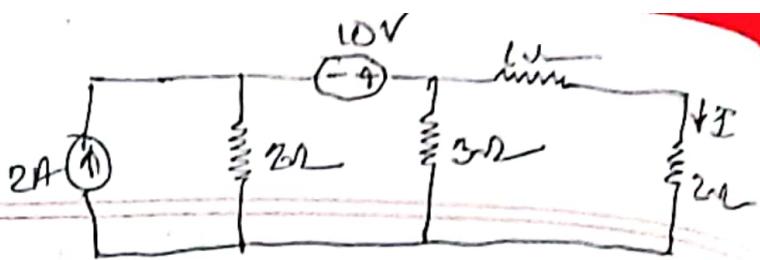


Fig-1

$$(2 || 3) = \frac{2 \times 3}{2 + 3} = 1.2 \Omega$$

$$(1 + 2) \Omega = 3 \Omega$$

Using CDR,

$$I' = \frac{2 \times 1.2}{1.2 + 3} = 0.77 A$$


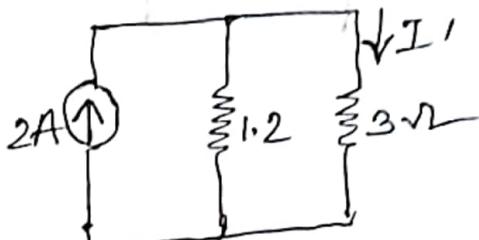


Fig-2

Using ohm's Law,

$$(3 || 3) = \frac{3 \times 3}{3 + 3} = 1.5 \Omega$$

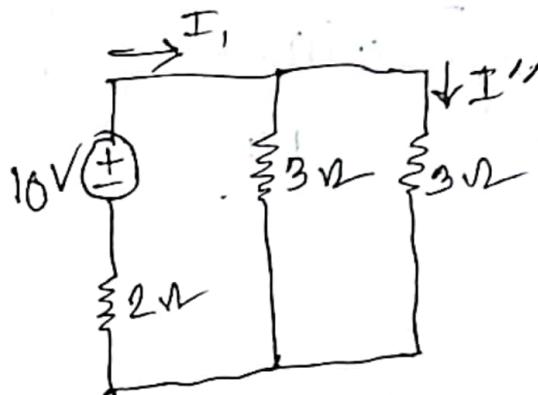



$$I_1 = \frac{10}{2 + 1.5} = 2.86 A$$

$$I'' = \frac{I_1 \times 3}{3 + 3} = \frac{2.86 \times 3}{3 + 3}$$

$$= 1.43 A$$

$$\begin{aligned} I &= I' + I'' \\ &= 0.77 + 1.43 \\ &= 2A \end{aligned}$$

Q

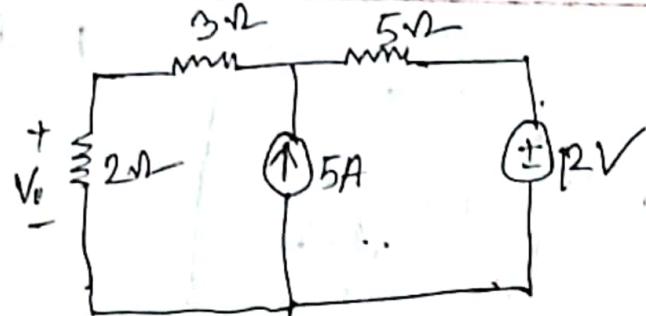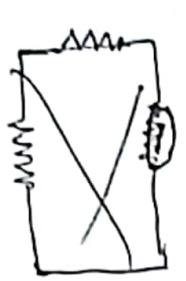

SOL VE

Fig -1

Using VDR,

$$V_o' = \frac{12 \times 2}{2+3+5} = \frac{24}{10} = 2.4V$$


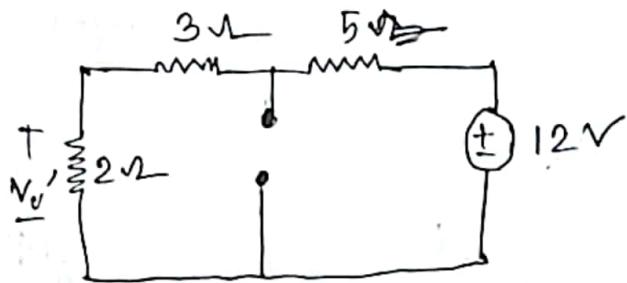


Fig -2

Using CDR,
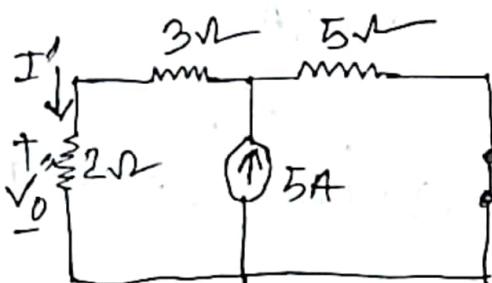
$$I' = \frac{5 \times 5}{(3+2)+5} = \frac{25}{10} = 2.5$$




$$V_o'' = I' \times 2 \\ = 2.5 \times 2$$

$$= 5$$

$$\therefore V = V_o' + V_o'' \\ = 2.4 + 5 = 7.4V$$

Q1

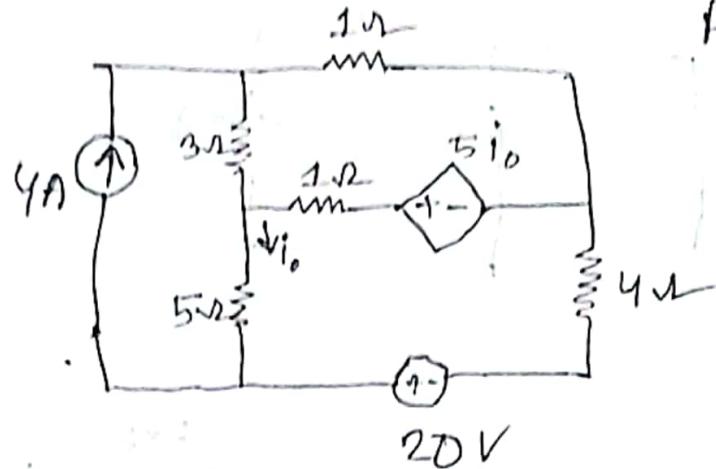

Find  $i_o$

SOLVE

Using KCL,

$$i_o' + i_2 = i_1$$

$$\therefore i_o' = i_1 - i_2 = 4 - i_2$$

$$\text{Mash-1 : } i_1 = 4A \xrightarrow{\text{---} (1)} = 4 - 0.94 = 3.06A$$

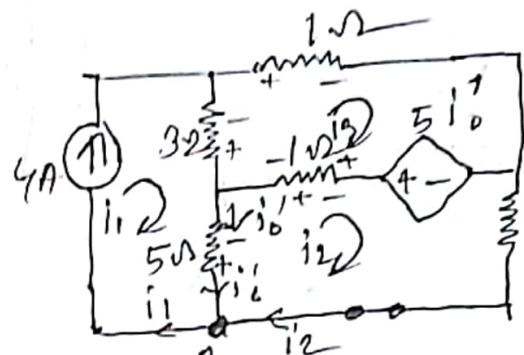


Fig - 1

Mash-2 using KVL,

$$5(i_2 - i_1) + 1(i_2 - i_3) + 5i_0' + 4i_2 = 0$$

$$\Rightarrow 5(i_2 - 4) + i_2 - i_3 + 5(4 - i_2) + 4i_2 = 0$$

$$\Rightarrow 5i_2 - 20 + i_2 - i_3 + 20 - 5i_2 + 4i_2 = 0$$

$$\Rightarrow 5i_2 - i_3 = 0 \xrightarrow{\text{---} (1)}$$

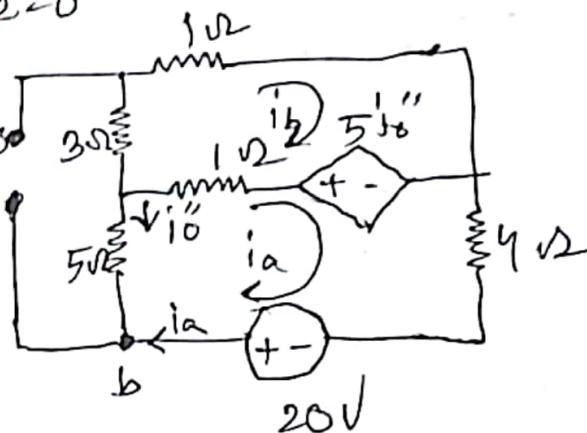


Fig - 2

Fig - 2

KCL node-b

$$i_a + i_o'' = 0$$

$$\therefore i_o'' = -i_a$$

KVL in mesh-3

$$3(i_3 - i_4) + 2i_3 - 5(4 - i_2) + 1(i_3 - i_2) = 0$$

$$\Rightarrow 3i_3 - 12 + 2i_3 - 20 + 5i_2 + i_3 - i_2 = 0$$

$$\Rightarrow 4i_2 + 6i_3 - 32 = 0$$

$$\Rightarrow 2i_2 + 3i_3 = 16 \quad \text{--- (1)}$$

eq (1) & (11)  $\Rightarrow$

$$15i_2 - 3i_3 = 0$$

$$2i_2 + 3i_3 = 16$$

$$12i_2 = 16$$

$$\therefore i_2 = 0.4A$$

Fig - 2

KCL node-b,

$$i_a + i_o'' = 0$$

$$\Rightarrow i_o'' = -i_a$$

Applying KVL, mesh-1,

$$5i_a + 1(i_a - i_b) + 5i_o'' + 4i_a^{+20} = 0$$

$$\Rightarrow 5i_a + i_a - i_b + 5(-i_a) + 4i_a^{+20} = 0$$

$$\Rightarrow 5i_a + i_a - i_b - 5i_a + 4i_a^{+20} = 0$$

$$\Rightarrow 5i_a - i_b = 20 \quad \text{--- (1)}$$

KCL mesh-2,

$$3i_b + 2i_b - 5i_o'' + 1(i_b - i_a) = 0$$

$$\Rightarrow 3i_b + 2i_b - 5(-i_a) + i_b - i_a = 0$$

$$\Rightarrow 4i_a + 6i_b = 0 \quad \text{--- (2)}$$

eq solving,


$$i_a = 3.5A$$

$$i_o'' = -3.5A$$

$$i_o = i_o' + i_o''$$

$$= 3.06 - 3.5$$

$$= -0.4A$$

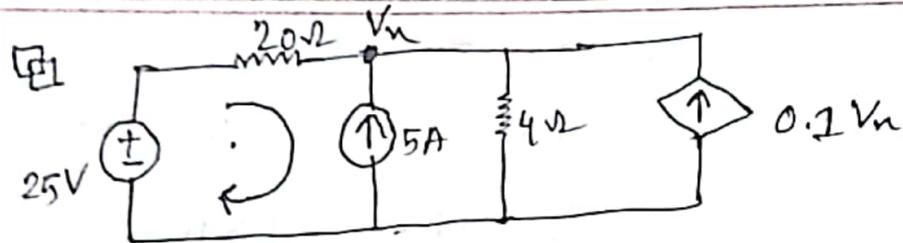


Find  $V_m$

Solve

Using nodal Analysis,

$$i_1 + i_2 = i_3$$
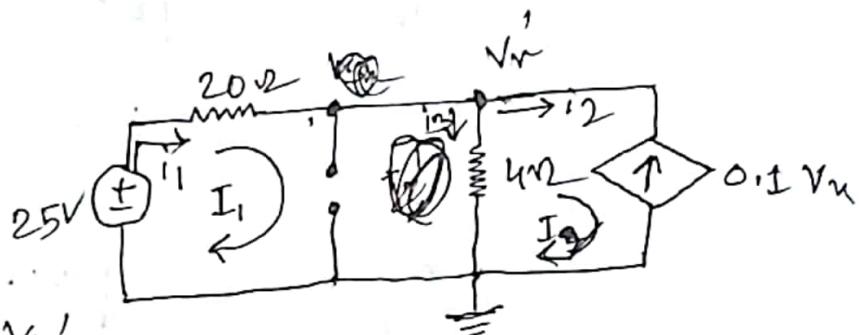
$$\Rightarrow \frac{25 - V_m'}{20} + 0.1 V_m = \frac{V_m'}{4}$$




$$\therefore V_m' =$$

$$\Rightarrow \frac{25}{20} - \frac{V_m'}{20} + 0.1 V_m - \frac{V_m'}{4} = 0$$

$$\Rightarrow 25 - V_m' + 2 V_m - 5 V_m' = 0$$

$$\Rightarrow 25 - 4 V_m' = 0$$
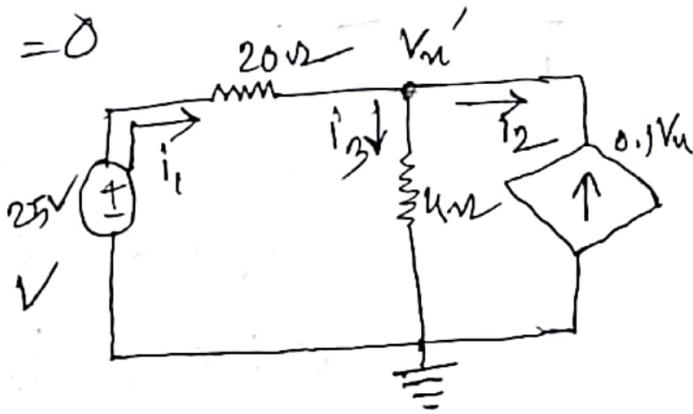
$$\Rightarrow V_m' = \frac{25}{4} = 6.25 \text{ V}$$



MID

Applying KCL,

$$5 + 0.1V_m'' = i_1 + i_2$$

$$\Rightarrow 5 + 0.1V_m'' = \frac{V_m''}{20} + \frac{V_m''}{4}$$

$$\Rightarrow \frac{V_m''}{20} + \frac{V_m''}{4} = 0.1V_m'' + 5$$

$$\Rightarrow V_m'' + 5V_m'' = 2V_m'' + 100$$

$$\Rightarrow V_m'' + 5V_m'' - 2V_m'' - 100 = 0$$



$$\Rightarrow 4V_m'' = 100$$

$$\therefore V_m'' = 25V$$

$$V_m = V_m' + V_m''$$

$$= 6.25 + 25$$

$$= 31.25V$$

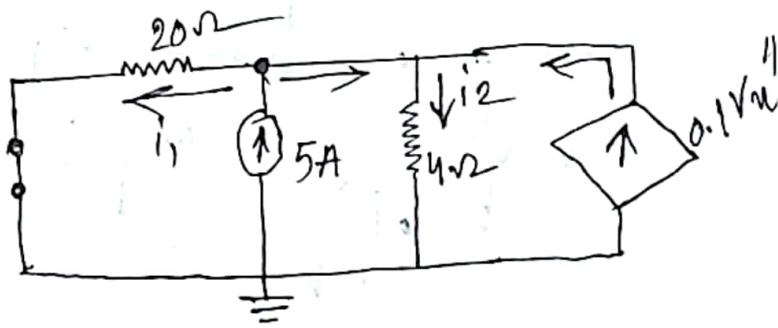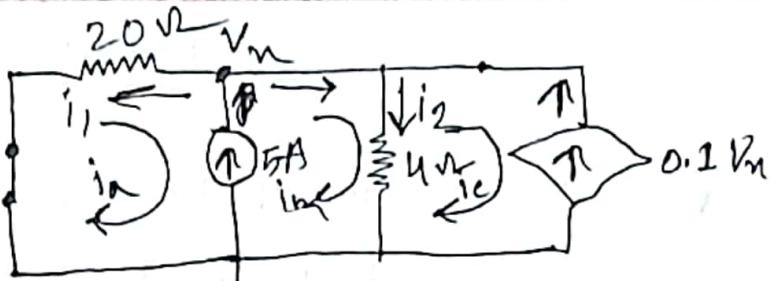


Practice

Q In a certain application, the circuit in the following figure must be designed to meet this two criteria:

$$a) \frac{V_o}{V_s} = 0.05 \quad b) R_{eq} = 40k\Omega$$

If the load resistor ~~meet the criteria~~  $5k\Omega$  is fixed,  
find  $R_1$  and  $R_2$  to meet the criteria.

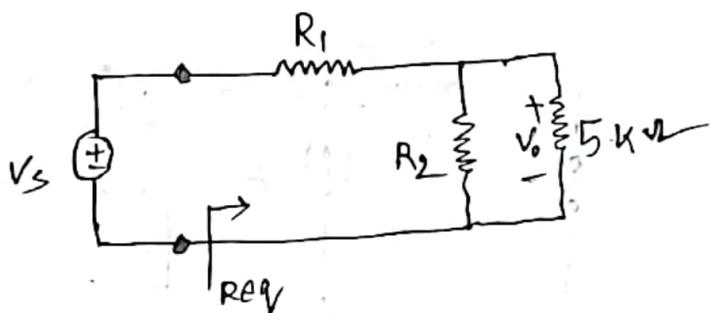Solve

$$\frac{V_o}{V_s} = 0.05$$

KVL in loop 2,  
~~I~~  $\leftarrow 5I$

$$R_{eq} = 40k\Omega$$

Using VDR,

$$V_o = \frac{V_s (R_2 || 5k\Omega)}{R_1 + (R_2 || 5k\Omega)}$$

KVL in loop 1,  
 $-V_s + I R_1 + I_1 R_2 = 0$

$$\Rightarrow \frac{V_o}{V_s} = \frac{R_2 || 5}{R_1 + R_2 || 5}$$

$$\Rightarrow 0.05 = \frac{R_2 || 5}{R_{eq}}$$

$$\Rightarrow 0.05 = \frac{R_2/15}{40}$$

$$\Rightarrow R_2/15 = 0.05 \times 40$$

$$\Rightarrow \frac{R_2 \times 5}{R_2 + 5} = 0.05 \times 40$$

$$\Rightarrow R_2 \times 5 = (0.05 \times 40)(R_2 + 5)$$

$$\Rightarrow R_2 \times 5 = (0.05 \times 40)R_2 + (0.05 \times 40 \times 5)$$

$$\Rightarrow (R_2 \times 5) - (0.05 \times 40)R_2 = 0.05 \times 40 \times 5$$

$$\Rightarrow R_2(5 - 0.05 \times 40) = 0.05 \times 40 \times 5$$

$$\Rightarrow R_2 = \frac{0.05 \times 40 \times 5}{5 - 0.05 \times 40}$$

$$\therefore R_2 = 3.33 \text{ k}\Omega$$


$$\therefore R_{eq} = R_1 + (R_2/15)$$

$$\Rightarrow 40 = R_1 + \frac{R_2 \times 5}{R_2 + 5}$$

$$\Rightarrow 40 = R_1 + \frac{3.33 \times 5}{3.33 + 5}$$

$$\Rightarrow 40 = R_1 + \frac{16.65}{8.33}$$
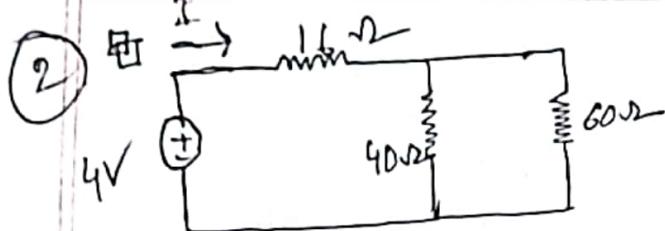
$$\Rightarrow R_1 = 40 - \frac{16.65}{8.33} = 38.002 \text{ k}\Omega$$




- a) Find the current  $I$   
 b) An ammeter with an internal resistance of  $1\Omega$  is inserted in the network to measure the current through  $16\Omega$  resistor  
 c) calculate the percent error introduced by the meter as  $\left| \frac{I - I'}{I} \right| \times 100\%$ .

SOLVE

a) Applying KCL in node-A,

$$I = I_1 + I_2$$

Applying KVL in loop-1,

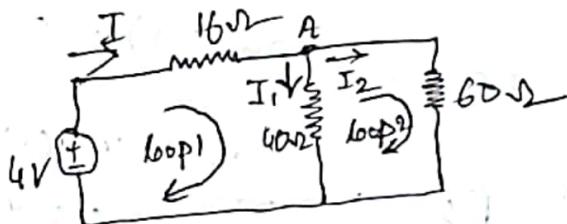

$$a) \left(40/160\right) = \frac{40 \times 60}{40+60} = 29\Omega$$

Using Ohm's Law,


$$I = \frac{4}{16+29} = 0.1 A$$

b)

$$R_{eq} = (16+1) + (40/160)$$

$$= 17 + \frac{40 \times 60}{40+60}$$

$$= 41\Omega$$

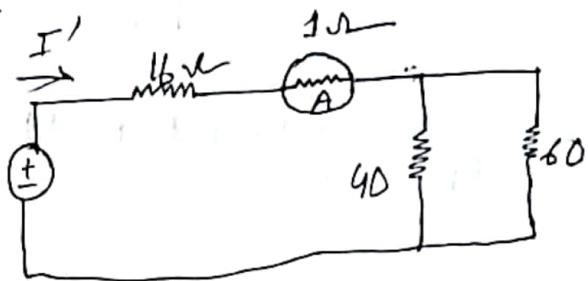

Using Ohm's Law,


$$I' = \frac{4}{41} = 0.098 A$$

c) Percent of error,

$$\left| \frac{I - I'}{I} \right| \times 100\%$$

$$= \left| \frac{0.1 - 0.098}{0.1} \right| \times 100\%$$

$$= 2\%$$


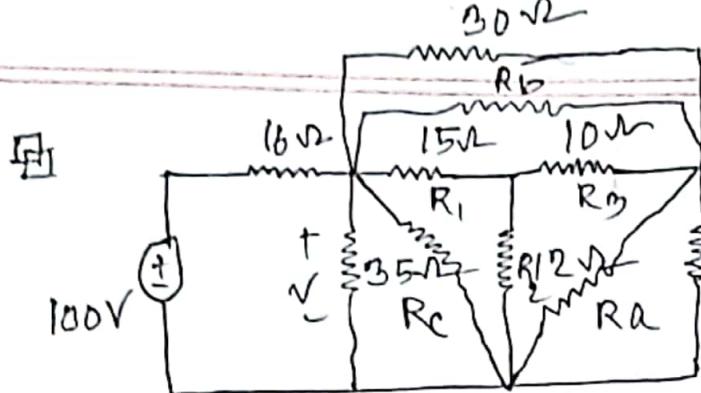


\* V (use  $\Delta \rightarrow Y$ )


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = 30$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = 32.5$$
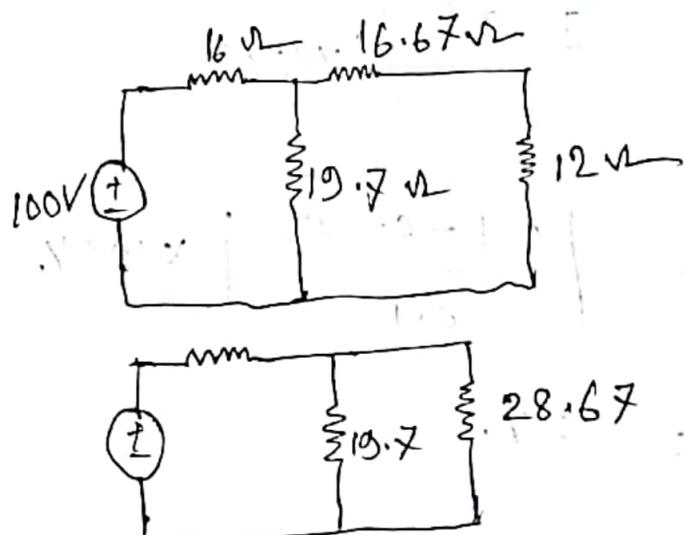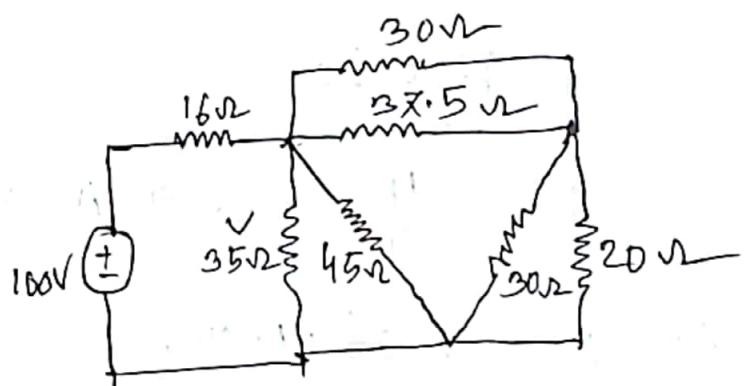
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = 45$$




Using VDR,

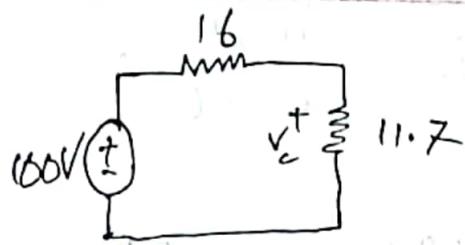

$$V = \frac{V_s \times 11.7}{16 + 11.7}$$

$$= 42.24 \text{ V}$$

(4)

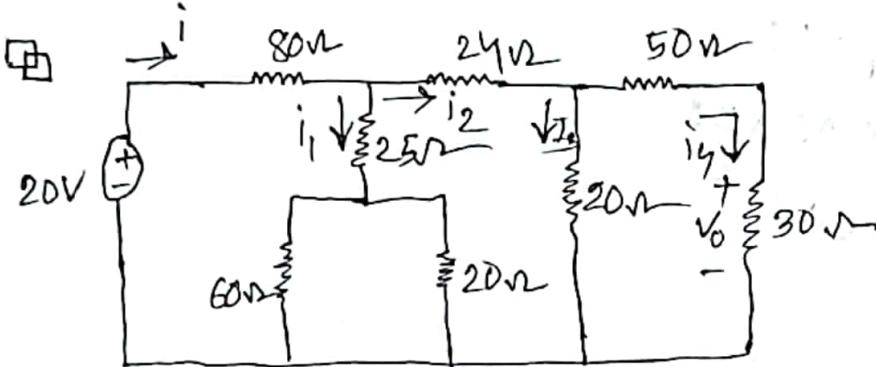

Find I and V\_o.

$$(50 + 30) = 80 \Omega$$

$$(80 || 20) = \frac{80 \times 20}{80 + 20} = 16 \Omega$$

$$(16 + 24) = 40$$



$$(60 || 20) = \frac{60 \times 20}{60 + 20} = 15 \Omega$$

$$(15 + 25) = 40 \Omega$$

$$(40 || 40) = \frac{40 \times 40}{40 + 40} = 20 \Omega$$

Using VDR,

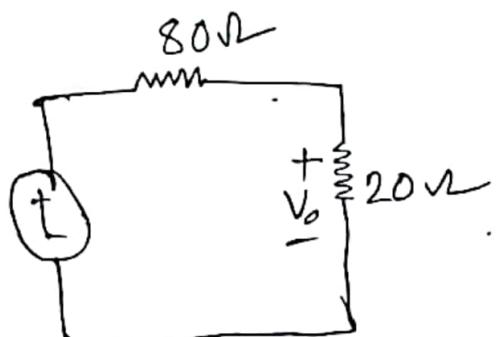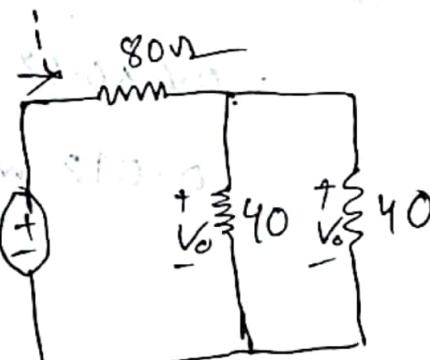~~$$V_o = \frac{20 \times 20}{80 + 20} = 4 \text{ V}$$~~



Using Ohm's Law,  
 $I = \frac{20}{80 \Omega} = 0.25 \text{ A}$

$$\text{Using CDR, } i_2 = \frac{i_1 \cdot 40}{40+40} = \frac{0.2}{2} = 0.1 A$$

$$i_4 = \frac{i_2 \times 20}{20+8} = 0.02 A$$

Using ohm's Law,


$$\begin{aligned} V_0 &= i_4 \times 30 \\ &= 0.02 \times 30 \\ &= 0.6 V \end{aligned}$$

$$P_{30\text{V}2} = V_0 i_4$$

$$\begin{aligned} &= 0.6 \times 0.02 \\ &= 0.012 W \end{aligned}$$

$$V = IR$$

$$\Rightarrow R = \frac{V}{I}$$

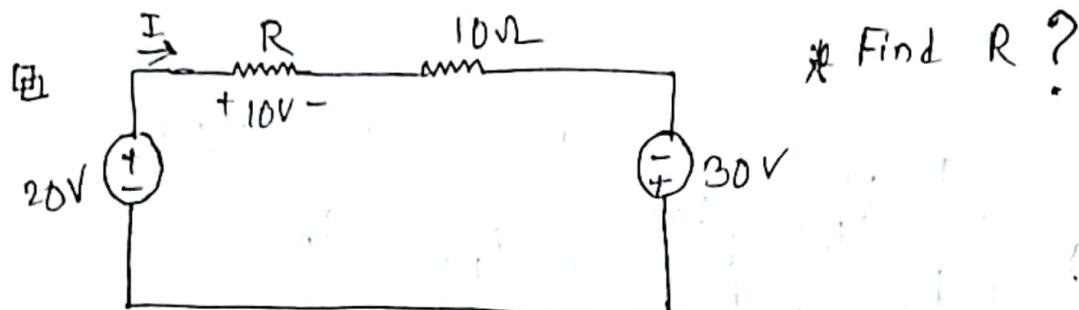

Solve

$$-20 + 10 + 10 - 30 = 0$$

$$\Rightarrow IR = 40 \Rightarrow I = \frac{40}{10} = 4 \text{ A}$$


$$\Rightarrow R = \frac{40}{4} \quad \text{Using ohm's law,}$$

$$V = IR$$

$$\Rightarrow 10 = 4R$$

$$\Rightarrow R = \frac{10}{4} = 2.5 \Omega$$

6

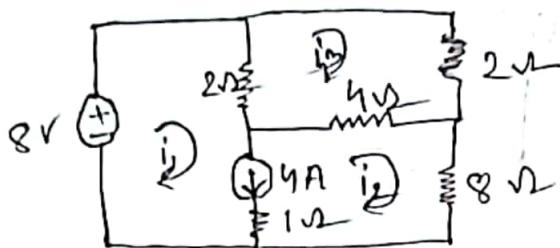

Use mesh analysis

$i_1, i_2, i_3$

Solve


Applying KVL in super mesh,

$$-8 + 2(i_1 - i_3) + 4(i_2 - i_3) + 8i_2 = 0$$

$$\Rightarrow -8 + 2i_1 - 2i_3 + 4i_2 - 4i_3 + 8i_2 = 0$$

$$\Rightarrow 2i_1 + 12i_2 - 6i_3 = 8$$
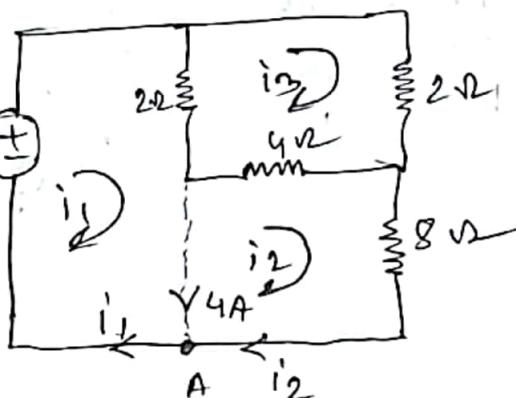
$$\Rightarrow i_1 + 6i_2 - 3i_3 = 4 \quad \text{--- (1) } \times 2$$



Applying KVL in mesh-3,

$$2(i_3 - i_1) + 2i_3 + 4(i_3 - i_2) = 0$$

$$\Rightarrow -i_1 - 2i_2 + 4i_3 = 0 \quad \text{--- (2)}$$

$$\Rightarrow i_1 + 2i_2 - 4i_3 = 0$$

Applying KCL in node-A,

$$i_1 = 4 + i_2 \quad \text{--- (3)}$$

14 Days Left

MID

30 July

$$\textcircled{1} \times 4 - \textcircled{11} \times 3$$

$$4i_1 + 24$$

$$\text{eq. (1)} \Rightarrow$$

$$4 + i_2 + 6i_2 - 3i_3 = 4$$

$$\Rightarrow 7i_2 - 3i_3 = 0 \quad \text{--- \textcircled{11}}$$

$$\text{eq. (11)}$$

$$4 + i_2 + 2i_2 - 4i_3 = 0$$

$$\Rightarrow 3i_2 - 4i_3 + 4 = 0 \quad \text{--- \textcircled{11}}$$

$$\textcircled{11} \times 4 - \textcircled{11} \times 3$$

$$28i_2 - 12i_3 = 0$$

$$9i_2 - 12i_3 + 12 = 0$$

$$\begin{array}{r} (+) \\ (-) \end{array}$$

$$\underline{19i_2 - 12 = 0}$$

$$\Rightarrow i_2 = \frac{12}{19} = 0.63$$

$$\textcircled{i_2} \text{ in eq. (v)} \Rightarrow$$


$$\begin{aligned} i_1 &= 4 + 0.63 \\ &= 4.63 \end{aligned}$$

$i_2$  in eq. (11)

$$(7 \times 0.63) - 3i_3 = 0$$

$$\Rightarrow i_3 = \frac{4.41}{3} = 1.47$$

Date: 23-07-2025


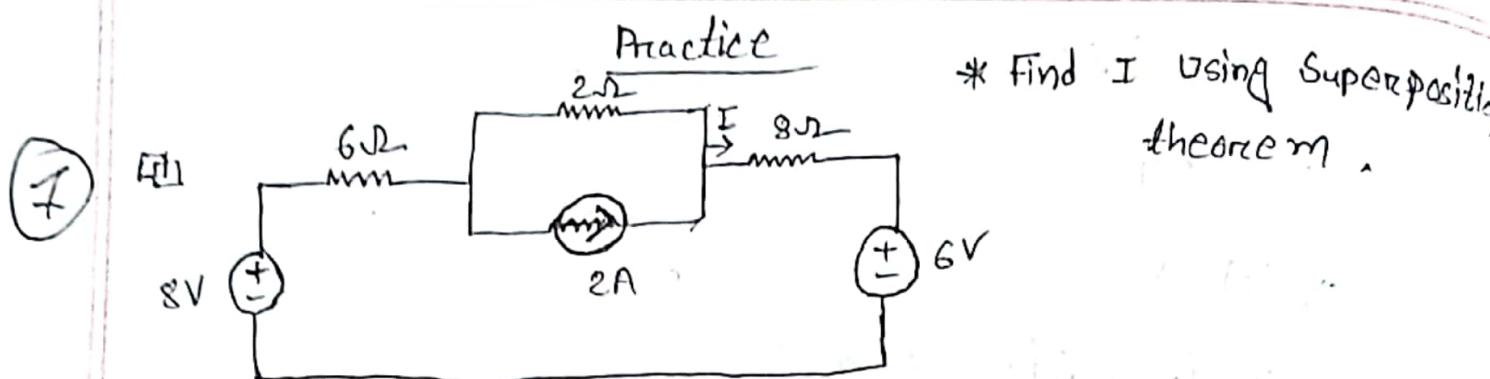


\* Find  $I$  using Superposition theorem.

SOLVE


Using Ohm's Law,
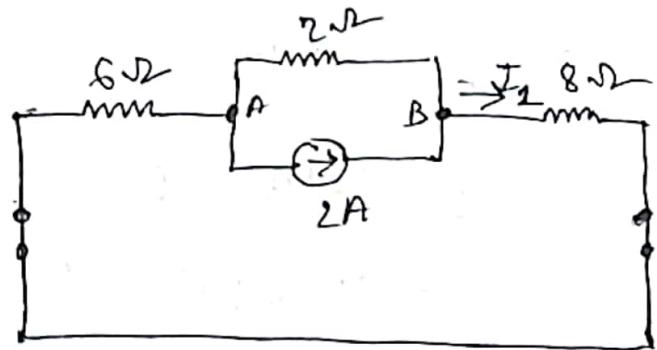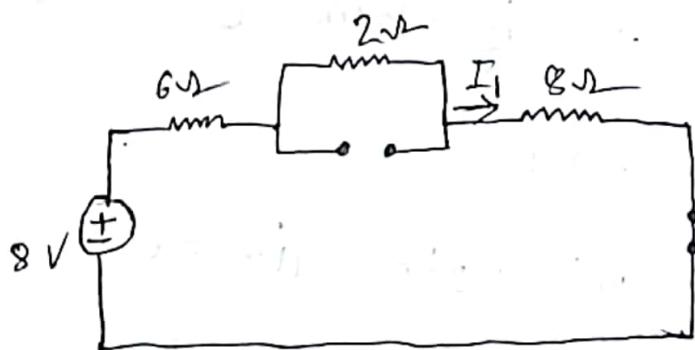
$$I_1 = \frac{8}{6+2+8} = 0.5 \text{ A}$$



Using CDR,
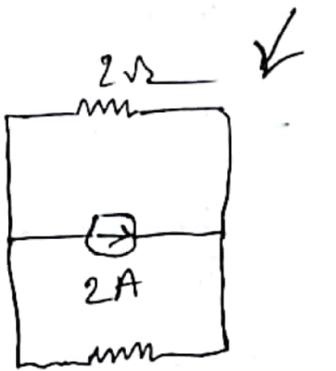
$$I_2 = \frac{2 \times 2}{2 + 14} = 0.25 \text{ A}$$



$$6+8=14\Omega$$


mid  $\rightarrow$  Q-5

120  
5

Using ohms law; KVL,

$$I_3 \cdot 6 + 2I_3 + 8I_3 + 6 = 0$$
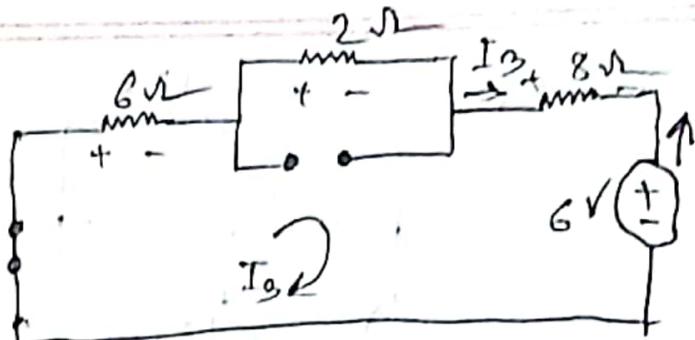
$$\Rightarrow I_3 = -\frac{6}{6+2+8} = -0.375 \text{ A}$$




$$I = I_1 + I_2 + I_3$$

$$= 0.5 + 0.25 - 0.375$$

$$= 0.375 \text{ A}$$

$$= 375 \text{ mA} \quad \underline{\text{Ans:}}$$

8

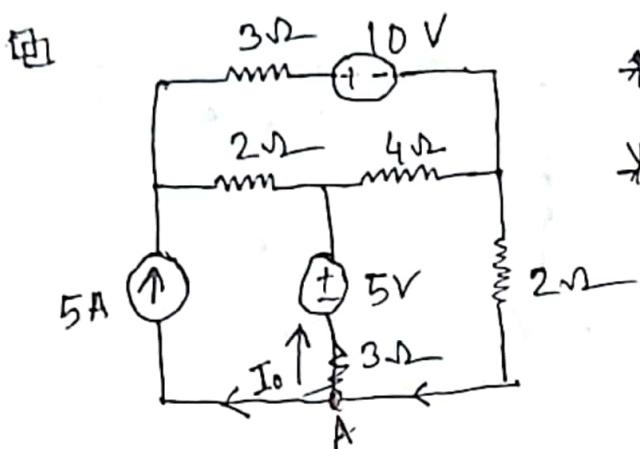


- \* Find the mesh currents.
- \* Find the current  $I_0$ .

SOLVE

From mesh 1,

$$I_1 = 5A$$

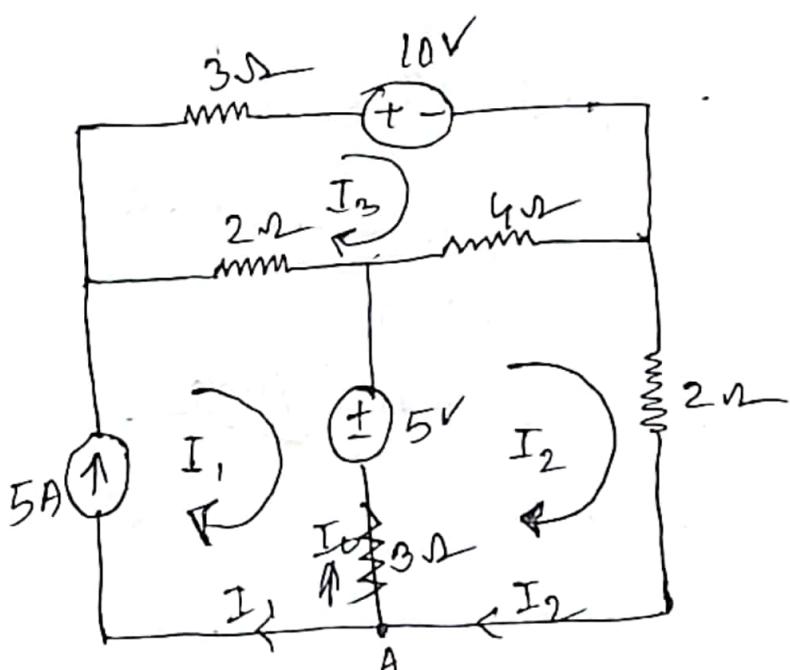

Applying KVL in mesh 2,

$$3(I_2 - I_1) - 5 + 4(I_2 - I_3) + 2I_2 = 0$$

$$\Rightarrow 3I_2 - 3I_1 - 5 + 4I_2 - 4I_3 + 2I_2 = 0$$

$$\Rightarrow -3I_1 + 9I_2 - 4I_3 = 5$$

$$\Rightarrow (-3 \times 5) + 9I_2 - 4I_3 = 5$$

$$\Rightarrow 9I_2 - 4I_3 = 20 \quad \text{--- (1)}$$

Applying KVL in mesh 3,

$$4(I_3 - I_2) + 2(I_3 - I_1) + 3I_3 + 10 = 0$$

$$\Rightarrow 4I_3 - 4I_2 + 2I_3 - 2I_1 + 3I_3 + 10 = 0$$

$$\Rightarrow -2I_1 - 4I_2 + 9I_3 + 10 = 0$$

$$\Rightarrow (-2 \times 5) - 4I_2 + 9I_3 + 10 = 0$$

$$\Rightarrow -4I_2 + 9I_3 = 0 \quad \text{--- (II)}$$

solving eq (I) & (II)  $\Rightarrow$

$$I_2 = 2.8 A$$

$$I_3 = 1.23 A$$


Applying KCL at node A,

$$I_1 + I_0 = I_2$$

$$\Rightarrow I_0 = 2.8 - 5$$

$$\therefore I_0 = -2.2 A$$

⑨

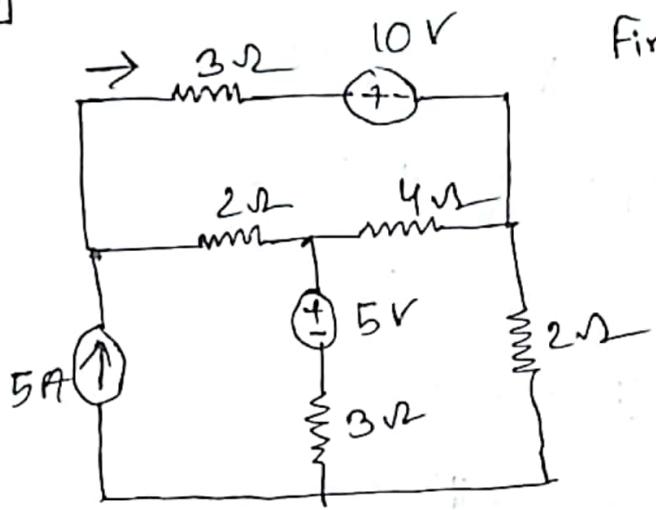

Find I using superposition theorem.


Modal Analysis

Solve  $\frac{4}{4+2} = \frac{4 \times 2}{6+2} = 1.5$

Using Ohms Law,

$$I_1 = \frac{10}{\frac{4 \times 2}{6+2}} = \frac{10}{1.5 \times 3} = \frac{10}{4.5} = 2.22 \text{ A}$$

$$= 10 \text{ A}$$

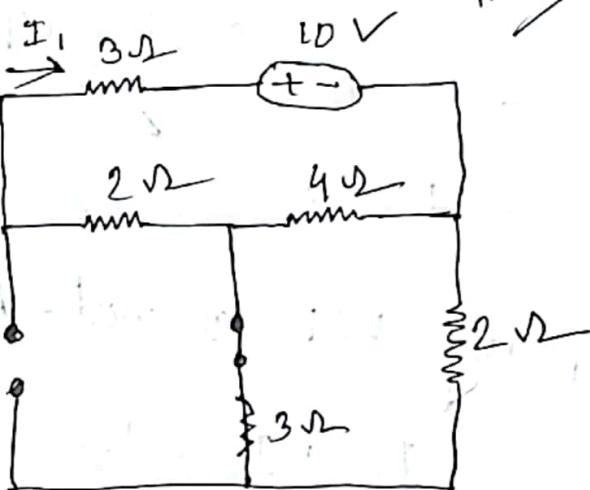


$$\frac{2}{2+3} = \frac{2 \times 3}{2+3} = 0.75$$

$$0.75 \parallel 4 = \frac{0.75 \times 4}{0.75+4} = 0.63 \text{ V}$$

$$0.63 \parallel 2 = \frac{0.63 \times 2}{0.63+2} = 0.48 \text{ V}$$

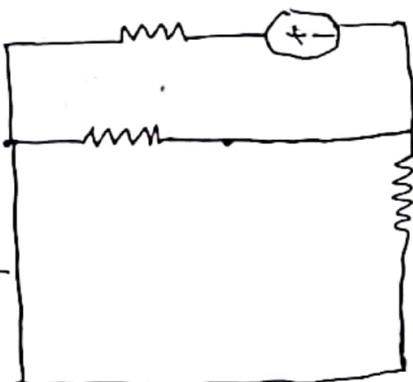
Using Ohms Law,  $I_1 = \frac{10}{\frac{0.48 \times 3}{0.48+3}} = 24.17 \text{ A}$



Using

From mesh 1,

$$I_1 = 5A$$

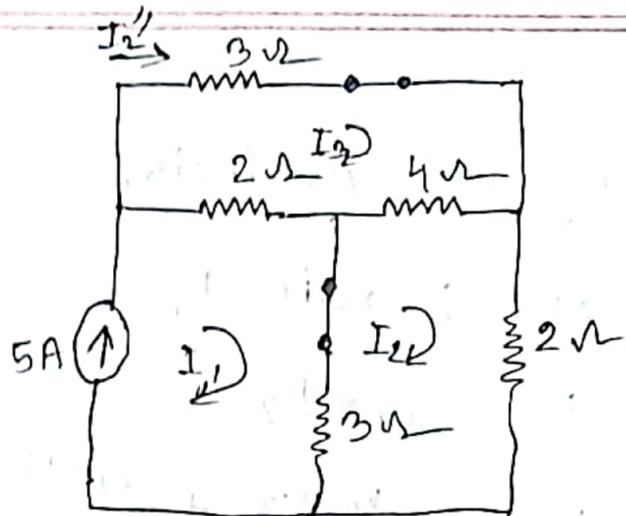

(mesh-2) Using KVL,

$$3(I_2 - I_1) + 4(I_2 - I_3) + 2I_2 = 0$$

$$\Rightarrow 3I_2 - 3I_1 + 4I_2 - 4I_3 + 2I_2 = 0$$

$$\Rightarrow -3I_1 + 9I_2 - 4I_3 = 0$$

$$\Rightarrow (-3 \times 5) + 9I_2 - 4I_3 = 0$$

$$\Rightarrow 9I_2 - 4I_3 = 10 \quad \text{--- (1)}$$

(mesh-3) Using KVL,

$$4(I_3 - I_2) + 2(I_3 - I_1) + 3I_3 = 0$$

$$\Rightarrow 4I_3 - 4I_2 + 2I_3 - 2I_1 + 3I_3 = 0$$

$$\Rightarrow -2I_1 - 4I_2 + 9I_3 = 0 \quad \left| \begin{array}{l} I_1 = 5A \\ I_2 = 2A \end{array} \right.$$

$$\Rightarrow -4I_2 + 9I_3 = 10 \quad \left| \begin{array}{l} I_2 = 2A \\ I_3 = 2A \end{array} \right.$$

$$\therefore I_2'' = 2 + 2 = 4A$$

grid circuit

start

Using nodal Analysis,

KCL in node-1,

$$I_3 = I_1 + I_2$$

$$\Rightarrow 5 = \frac{v_1 - v_3}{3} + \frac{v_1 - v_2}{2}$$

$$\Rightarrow 30 = (v_1 - v_3)2 + (v_1 - v_2)3$$

$$\Rightarrow 5v_1 - 3v_2 - 2v_3 = 30 \quad \text{--- (1)}$$

Applying KCL in node 2,

$$I_2 = I_4 + I_5$$

$$\Rightarrow \frac{v_1 - v_2}{2} = \frac{v_2}{5} + \frac{v_2 - v_3}{4}$$

$$\Rightarrow 6v_1 - 13v_2 + 3v_3 = 0 \quad \text{--- (2)}$$

KCL in node 3,

$$I_1 + I_5 = I_6$$

$$\Rightarrow \frac{v_1 - v_3}{3} + \frac{v_2 - v_3}{4} = \frac{v_3}{2}$$

$$\Rightarrow 4v_1 + 3v_2 - 13v_3 = 0 \quad \text{--- (3)}$$

Using Cramen's rule,

$$\begin{bmatrix} 5 & -3 & -2 \\ 6 & -13 & 3 \\ 4 & 3 & -13 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 30 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 5 & -3 & -2 \\ 6 & -13 & 3 \\ 4 & 3 & -13 \end{bmatrix} = 3490$$

$$\Delta_1 = \begin{bmatrix} 30 & -3 & -2 \\ 0 & -13 & 3 \\ 0 & 3 & -13 \end{bmatrix} = 4800$$

$$\Delta_2 = \begin{bmatrix} 5 & 30 & -2 \\ 6 & 0 & 3 \\ 4 & 0 & -13 \end{bmatrix}$$

$$\Delta_3 = \begin{bmatrix} 5 & -3 & 30 \\ 6 & -13 & 0 \\ 4 & 3 & 0 \end{bmatrix} = 2100$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{4800}{3490} = +5.05 \text{ A} \quad V$$

$$I_2 = \frac{\Delta_2}{\Delta} =$$



$$I_3 = \frac{\Delta_3}{\Delta} = \frac{2100}{3490} = 3.5 \text{ A} \quad \checkmark$$

$$I_1 = \frac{v_1 - v_3}{3}$$

$$= 2.30$$


$$(3+2) = 5\Omega$$


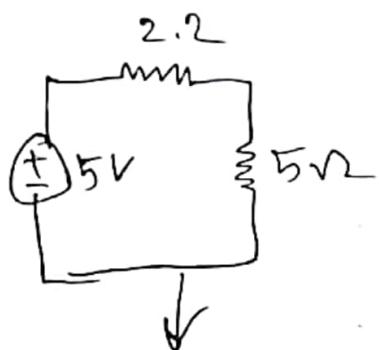
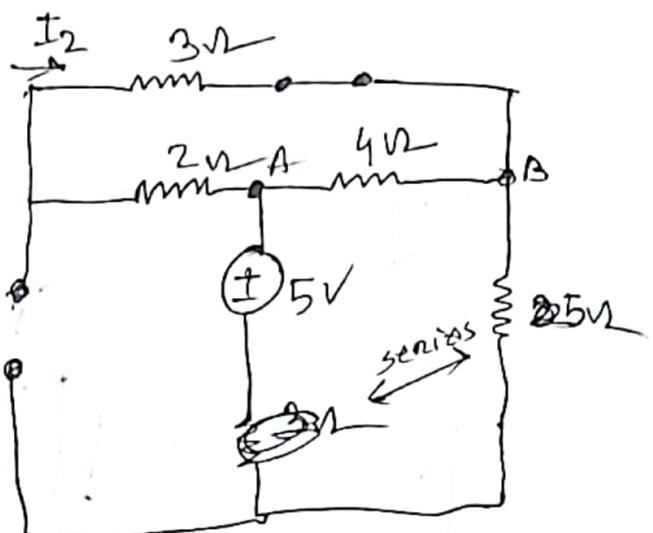
$$5/14 = \frac{5 \times 4}{5+4} = 2.2\Omega$$



Using ~~Ohm's~~, Ohm's Law

$$I' = \frac{5}{5+2.2} = 0.69$$

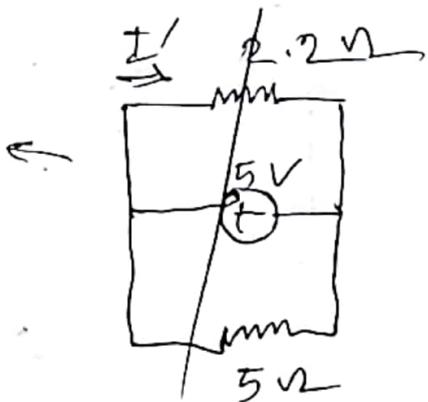

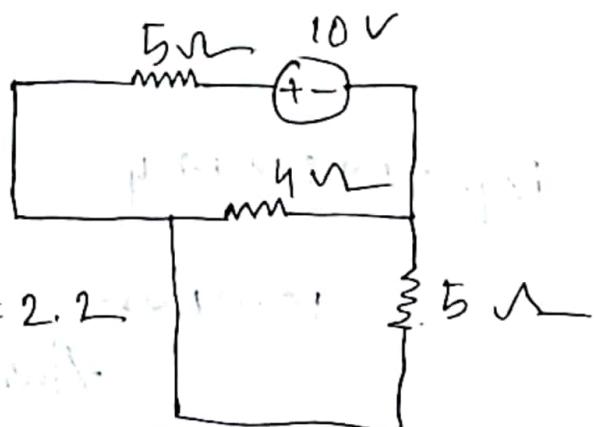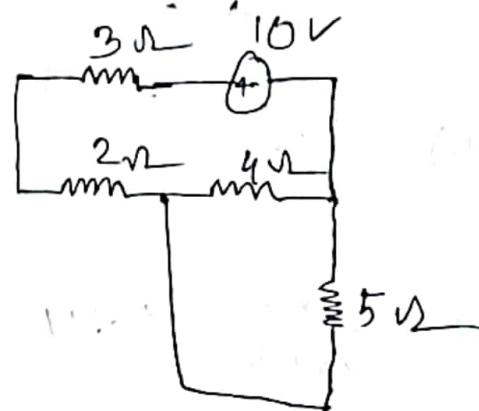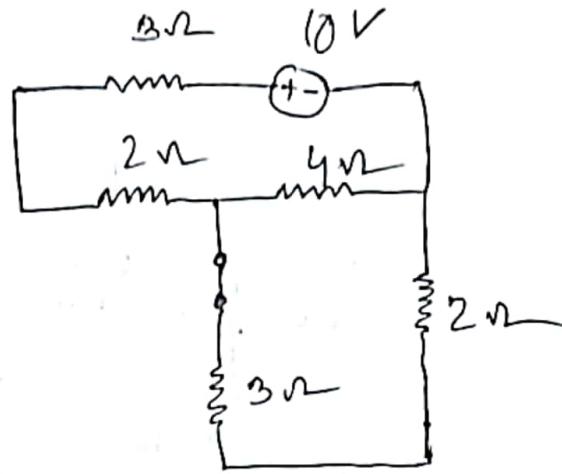


$$I_{4 \parallel 5} = \frac{4 \times 5}{4+5} = \frac{20}{9} = 2.2$$

$$I_3 = -\frac{10}{5+2.2} = -1.39 \text{ A}$$

$$\begin{aligned} I &= I_1 + I_2 + I_3 \\ &= 2.3 + 0.306 - 1.38 \\ &= 1.226 \text{ A} \quad \underline{\text{Ans:}} \end{aligned}$$


Ques

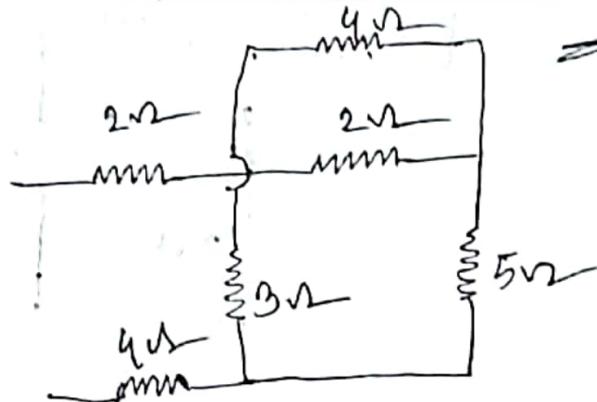

Find the Req.

$$(3+4) = X \Omega$$

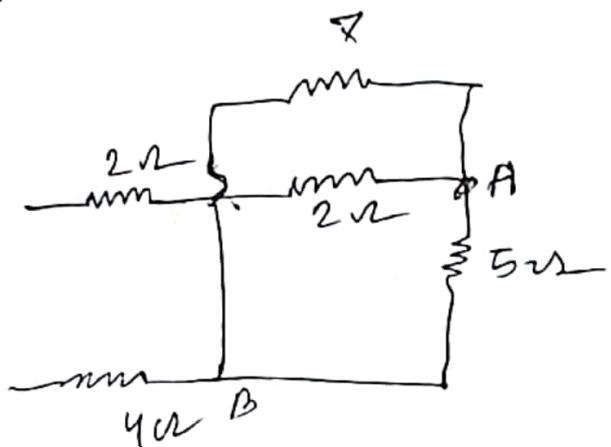
$$5/(X) = \frac{5 \times X}{5+X} = 2.91$$



$$Req = 4 + 2.91 + 4$$

$$= 10.91 \Omega$$

Ans

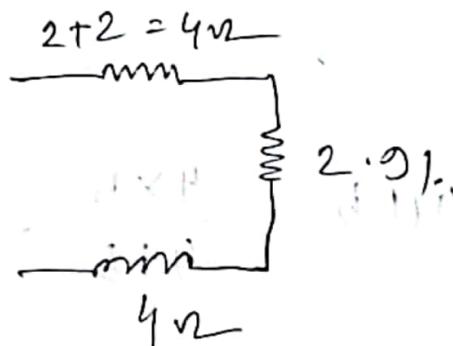

conductance,


$$G_{eq} = \frac{1}{Req}$$

$$= \frac{1}{10.91}$$

$$= 0.09 \text{ S}$$

$$P = VI = I^2 R = \frac{V^2}{R}$$

(11)
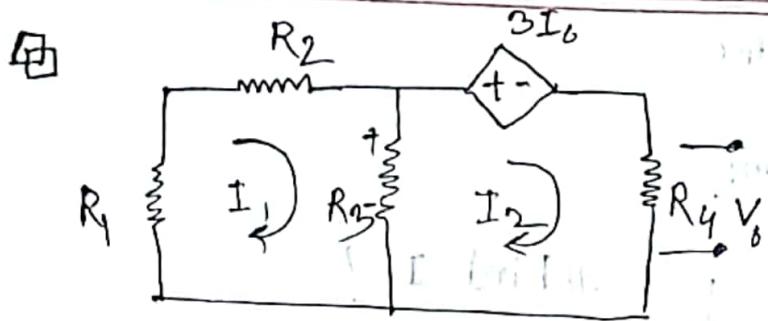
# Find  $V_0$  ?Ans:

Since there is no independent source

$$I_0 = 0A$$

$$V_0 = 0V$$

Solve

Using KVL in loop-1,

~~$I_1 R_1 + I_1 R_2 + I_1 R_3 = 0$~~

~~$I_1 R_1 + I_1 R_2 + R_0(I_1 - I_2) = 0$~~


Using KVL in loop-2

$$I_1 R_1 + I_1 R_2 + I_1 R_3 - I_2 R_3 = 0$$

 $\Rightarrow$


[Date: 28-07-2025]

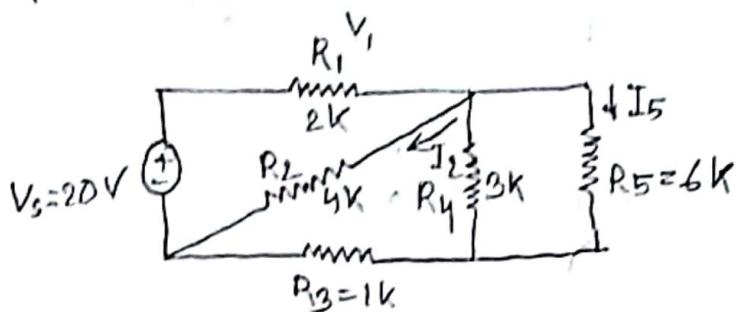**12** Q: Determine the current  $I_2$ ,  $I_5$ ,  $V_1$  & the power across  $R_4$  resistor.



Solve


$$3||6 = \frac{3 \times 6}{3+6} = \frac{18}{9} = 2\text{ k}$$

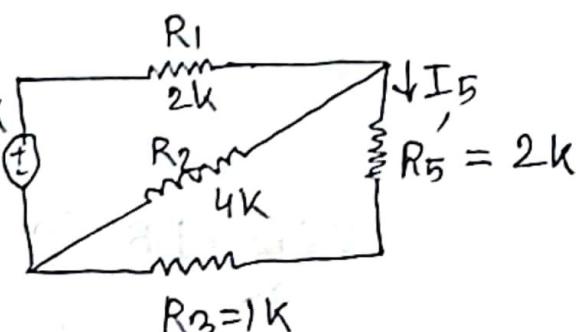

$$R_3' = R_5' + R_3 = 2 + 1 = 3\text{ k}$$

~~Ans~~

~~$$4||3 = \frac{12}{7} = 1.7\text{ k}$$~~

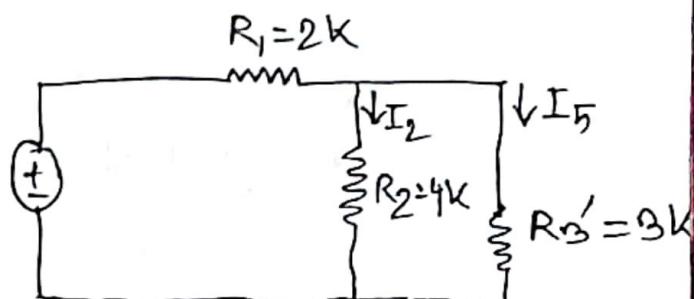


$$I_s = \frac{20}{2+1.7} = 5.4\text{ mA}$$



$$I_5 = \frac{5.4 \times 9}{3+4} = 3.1\text{ mA}$$

$$I_2 = \frac{5.4 \times 3}{4+3} = 2.3\text{ mA}$$
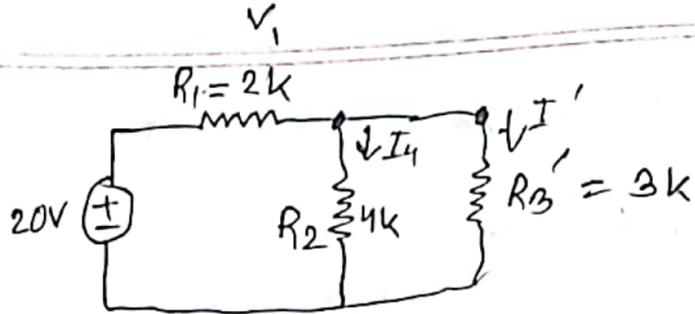
$$V_1 = I_s R_1 \\ = 5.4 \times 2 \\ = 10.8 \text{ V}$$



Applying KCL,

$$I_s = I_2 + I'$$

$$\Rightarrow I' = I_s - I_2 = 5.4 - 2 \cdot 3 = 3.1$$

Using CDR in  $I_5$ ,

$$I_s = \frac{I' R_4}{R_4 + R_5} = \frac{3.1 \times 3}{3 + 6} = 1.13 \text{ mA}$$


Applying KCL,

$$I_4 = I' - I_5 \\ = 3.1 - 1.13 \\ = 1.97$$

Power,


$$P_4 = I_4^2 R_4 \\ = (1.97)^2 \times 3 \\ = 11.65 \text{ W}$$

13 #

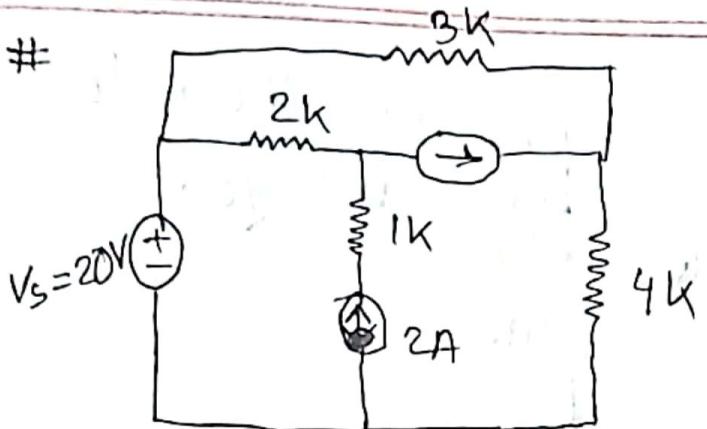

# find the mesh current.

SOLVE

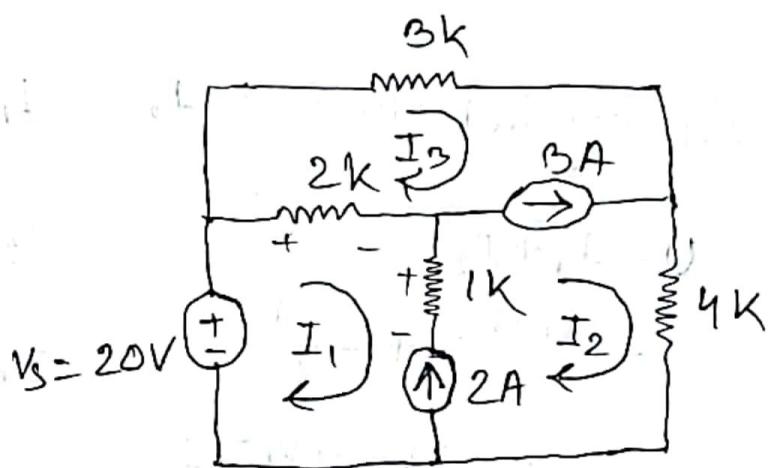

Applying KVL in mesh-1,

$$-20 + 2(I_1 + I_3) + 1(I_1 - I_2) = 0$$


KVL in supernode,

$$-V_s + I_1 2k + I_3 3k + I_2 4k = 0$$

KCL in node -A, B

$$I_1 + 2 = I_2$$

$$3 + I_3 = I_2$$

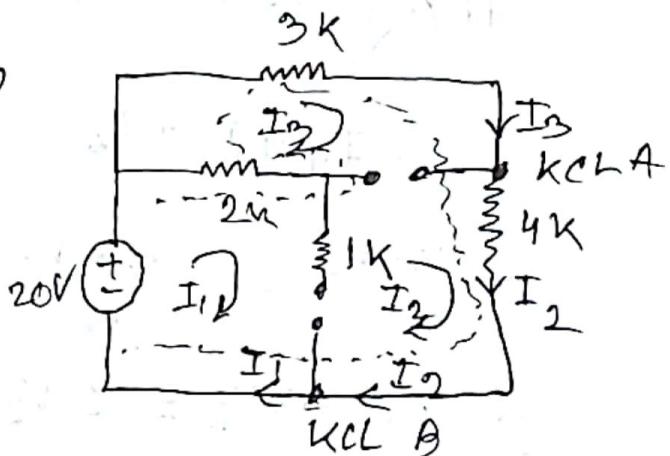


- \* Mesh
- \* Nodal
- \* Supermesh
- \* superposition

- \* Normal
- \* ~~or~~

14

#

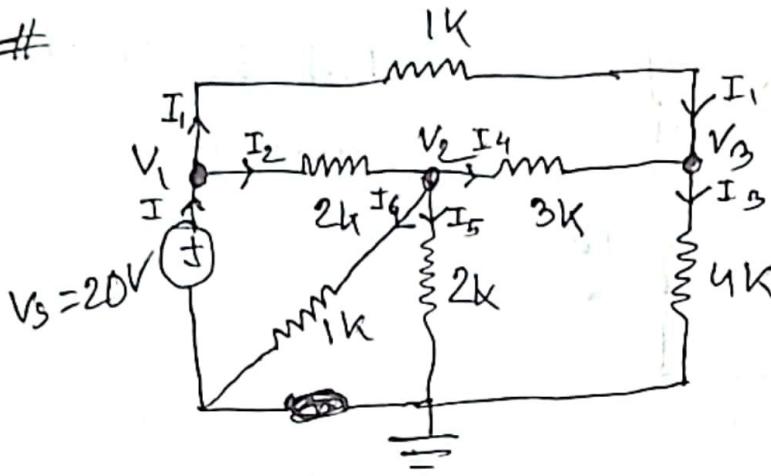

Find the node voltage.

Applying KCL in node-1,  $I_1 = \frac{V_1 - V_3}{1}$

$$\textcircled{1} = I_1 + I_2$$

$$= \frac{V_1 - V_3}{1} + \frac{V_1 - V_2}{2}$$

$$\textcircled{0} = 2V_1 - 2V_3 + V_1 - V_2$$

$$\Rightarrow 3V_1 - V_2 - 2V_3 = \textcircled{0}$$

$$\Rightarrow \textcircled{0} - V_2 - 2V_3 = \textcircled{0} - \textcircled{1} \quad I_4 = \frac{V_2 - V_3}{3}$$

Applying KCL in node-2,

$$I_2 = \frac{V_1 - V_2}{2}$$

$$I_3 = \frac{V_3}{4}$$

$$I_4 = \frac{V_2 - V_3}{3}$$

$$I_5 = \frac{V_2}{2}$$

$$I_6 = \frac{V_2}{1}$$

$$I_2 = I_4 + I_5 + I_6$$

$$\Rightarrow \frac{V_1 - V_2}{2} = \frac{V_2 - V_3}{3} + \frac{V_2}{2} + V_2$$

$$\Rightarrow 3V_1 - 3V_2 = 2V_2 - 2V_3 + 3V_2 + 6V_2 = 0$$

$$\Rightarrow 6V_1 - 3V_2 - 2V_2 + 2V_3 - 3V_2 - 6V_2 = 0$$

$$\Rightarrow -14V_2 + 3V_3 + 6V_1 = 0 \rightarrow \textcircled{11}$$

Applying KCL in node -3,

$$I_3 = I_4 + I_1$$

$$\Rightarrow \frac{v_3}{4} = \frac{v_2 - v_3}{3} + \frac{v_1 - v_3}{1}$$

$$\Rightarrow 3v_3 = 4v_2 - 4v_3 + 12v_1 - 12v_3$$


$$\Rightarrow 3v_3 - 4v_2 + 4v_3 - \cancel{(12 \times 20)} + 12v_3 = 0$$

$$\Rightarrow -4v_2 + 10v_3 - 240 = 0 \quad \text{--- (III)}$$

eq (I) (II) (III) solve ~~solve~~  $\Rightarrow$

15

#

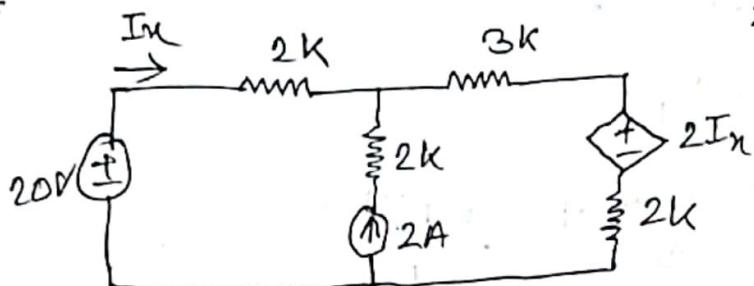

# Using super position theorem and  $I_n$

solve

Applying KVL in loop-1

$$-20 + 2I_n + 3I_n + 2I_n + 2I_n = 0$$

$$\Rightarrow -20 + 7I_n + 2I_n = 0$$

$$\Rightarrow -20 + 9I_n = 0$$

$$\therefore I_n = 2 \cdot 2A$$

Using nodal Analysis,

Using super mesh - KVL

$$2I_1 + 3I_2 + 2I_{n2} + 2I_2 = 0$$


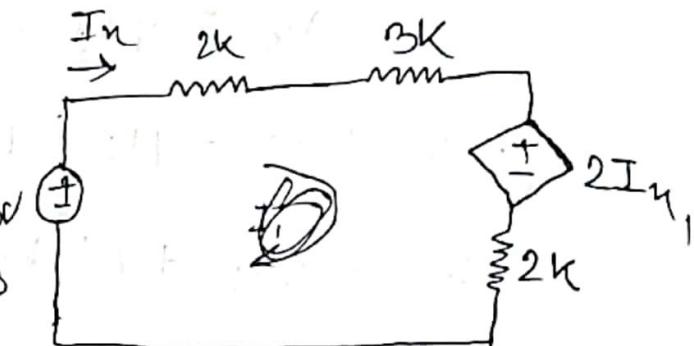


Fig-1

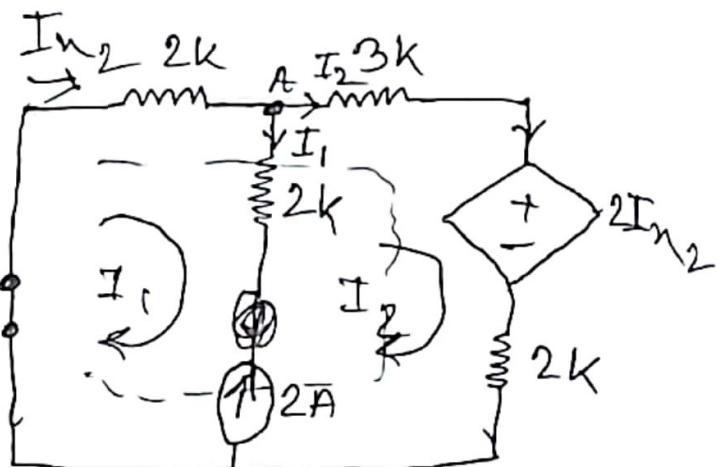

$$\Rightarrow 2I_{n2} + 3I_2 + 2I_{n2} + 2I_2 = 0$$

$$\Rightarrow 4I_{n2} + 5I_2 = 0 \quad \text{---(1)}$$

Fig-2

* Mesh	* KVL
* Nodal	* KCL
* Normal	* CDR
* Superposition	* VDR

KCL in Node - A

$$I_{n_2+2} = I_2 \quad \text{--- (1)}$$

$$\Rightarrow I_{n_2} - I_2 + 2 = 0$$

eq solve  $\Rightarrow$

$$I_{n_2} = -1.1 \text{ mA}$$

$$I_n = I_{n_1} + I_{n_2}$$

$$= 2.2 - 1.1$$

$$= 1.1 \text{ mA} \quad \underline{\underline{\text{Ans}}}$$