



# East West University

## Lab Report

**Semester:** Summer-2025

**Course Title:** Electrical Circuits

**Course Code:** CSE209

**Sec:** 01

**Expt No:** 05

**Expt Name:** Verification of Superposition Theorem.

**Group No:** 05

**Submitted by-**

Md. Arifur Rahman Razu

2024-3-60-503

**Submitted to-**

Dr. Sarwar Jahan  
Associate Professor  
Department of CSE  
East West University

**Date of Submission:** 10-08-2025

**Title:** Verification of Superposition Theorem.

**Objectives:**

1. To verify superposition theorem theoretically, experimentally and using PSpice simulation.

**Theory (Summary):**

The superposition theorem is used for linear circuits with multiple sources. It says that the voltage across or current through any element can be found by considering one source at a time and turning off the others (replacing voltage sources with short circuits). After finding the individual effects, we add them up algebraically to get the final result. In this experiment, we applied the superposition theorem to a circuit with three voltage sources and calculated the total current by adding the contributions from each source separately.

## Circuit Diagram:

$$E_1 = 10V \quad E_2 = 5V \quad E_3 = 5V$$

$$R_1 = 33\Omega \quad R_2 = 47\Omega \quad R_3 = 33\Omega \quad R_4 = 47\Omega \quad R_5 = 47\Omega \quad R_L = 68\Omega$$

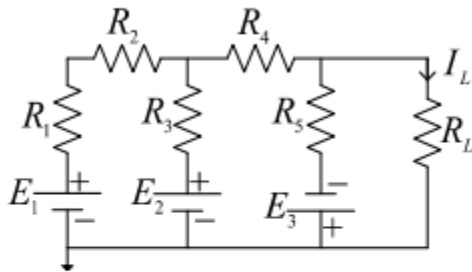


Figure 1. Circuit with all sources active.

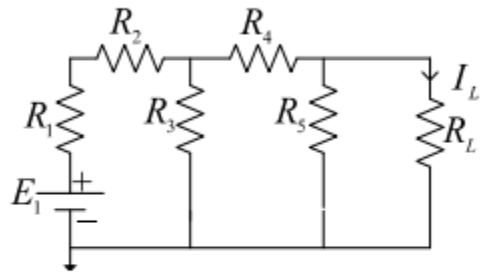


Figure 2. Circuit with  $E_1$  source active.

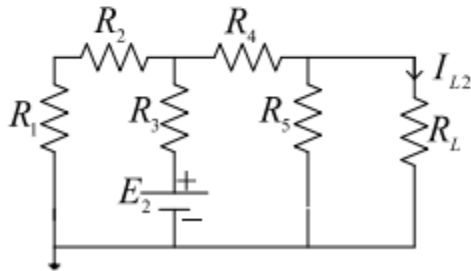


Figure 3. Circuit with  $E_2$  source active.

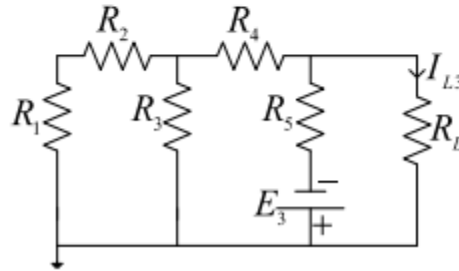


Figure 4. Circuit with  $E_3$  sources active.

## Post-Lab:

1. Theoretically calculate the values of  $I_L$ ,  $I_{L2}$  and  $I_{L3}$  of circuits from figure 1 through 4. From the calculated values, show that the superposition theorem holds, that is,  $I_L = I_{L1} + I_{L2} + I_{L3}$

ANS:

Figure 1,

Applying KVL at mesh1, mesh 2, and mesh 3

$$(33+47+33)i_1 - 33i_2 = 10-5 \dots(1)$$

$$-33i_1 + (33+47+47)i_2 - 47i_3 = 5+5 \dots(2)$$

$$-47i_2 + (47+68)i_3 = -5 \dots(3)$$

By solving

$$I_L = i_3 = -4.269 \text{ mA}$$

Figure 2,

Applying KVL in mesh1,mesh2,mesh3,

$$(33+47+33)i_1 - 33i_2 = 10 \dots(1)$$

$$-33i_1 + (33+47+47)i_2 - 47i_3 = 0 \dots(2)$$

$$-47i_2 + (47+68)i_3 = 0 \dots(3)$$

By solving,

$$I_3 = I_{L1} = 12.16 \text{ mA}$$

Figure 3,

Applying KVL at mesh 1,2 and 3,

$$(33+47+47)i_1 - 33i_2 = -5 \dots(1)$$

$$-33i_1 + (33+47+47)i_2 - 47i_3 = 5 \dots(2)$$

$$-47i_2 + (47+68)i_3 = 0 \dots(3)$$

By solving it,

$$I_3 = I_{L2} = 14.739 \text{ mA}$$

Figure 4,

Applying KVL in mesh 1 mesh 2 and mesh 3,

$$(33+47+33)i_1 - 33i_2 = 0 \dots(1)$$

$$-33i_1 + (33+47+47)i_2 - 47i_3 = 5 \dots(2)$$

$$-47i_2 + (47+68)i_3 = -5 \dots(3)$$

By solving it ,

$$I_3 = I_{L3} = -31.168 \text{ mA}$$

Now,

$$I_{L1} + I_{L2} + I_{L3} = 12.16 + 14.739 + (-31.168) \text{ mA}$$

$$= -4.269 \text{ mA}$$

$$= I_L$$

The superposition theorem is verified.

**Experimental datasheet:**

Measure d Value of $E_1$ (V)	Measure d Value of $E_2$ (V)	Measure d Value of $E_3$ (V)	Measure d value of $I_L$ with all sources active (mA)	Measure d value of $I_{L1}$ with only $E_1$ active (mA)	Measure d value of $I_{L2}$ with only $E_2$ active (mA)	Measure d value of $I_{L3}$ with only $E_3$ active (mA)	Measured values of resistors ( $\Omega$ )
10V	5V	-5V	-3mA	14.5mA	14.8mA	-32mA	$R_1=33\ \Omega$ $R_2=46.5\ \Omega$ $R_3=33\ \Omega$ $R_4=46\ \Omega$ $R_5=46\ \Omega$ $R_L=67\ \Omega$

**Post Lab:**

1. Calculate the values of  $I_L$ ,  $I_{L1}$ ,  $I_{L2}$ , and  $I_{L3}$  of the circuits of Figures 1 through 4 using the measured values of  $E_1$ ,  $E_2$ ,  $E_3$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ ,  $R_5$ , and  $R_L$ . The calculated values show that the superposition theorem holds. Compare these calculated values of currents with the experimental values and comment on any discrepancy observed.

**Ans:**

Here,

$$E_1 = 10V, E_2 = 5V, E_3 = -5V$$

$$R_1 = 33 \Omega, R_2 = 46.5 \Omega, R_3 = 33 \Omega, R_4 = 46 \Omega, R_5 = 46 \Omega \text{ and } R_L = 67\Omega$$

$$i_3 = I_L = ?$$

Applying KVL at mesh 1, 2 and 3,

$$(33 + 46.5 + 33)i_1 - 33i_2 = 10 - 5 \dots (1)$$

$$-33i_1 + (33 + 46 + 46)i_2 - 46i_3 = 5 + 5 \dots (2)$$

$$-46i_2 + (46 + 67)i_3 = -5 \dots (3)$$

By solving equation (1), (2) and (3) we get,

$$i_3 = I_L = -3.2 \text{ mA}$$

Applying KVL at mesh 1, 2 and 3,

$$(33 + 46.5 + 33)i_1 - 33i_2 = 10 \dots (1)$$

$$-33i_1 + (33 + 46 + 46)i_2 - 46i_3 = 0 \dots (2)$$

$$-46i_2 + (46 + 67)i_3 = 0 \dots (3)$$

By solving equation (1), (2) and (3) we get,

$$i_3 = I_{L1} = 14.6 \text{ mA}$$

Applying KVL at mesh 1, 2 and 3,

$$(33 + 46.5 + 33)i_1 - 33i_2 = -5 \dots (1)$$

$$-33i_1 + (33 + 46 + 46)i_2 - 46i_3 = 5 \dots (2)$$

$$-46i_2 + (46 + 67)i_3 = 0 \dots (3)$$

By solving equation (1), (2) and (3) we get,

$$i_3 = I_{L2} = 15 \text{ mA}$$

Applying KVL at mesh 1, 2 and 3,

$$(33 + 46.5 + 33)i_1 - 33i_2 = 0 \dots (1)$$

$$-33i_1 + (33 + 46 + 46)i_2 - 46i_3 = 5 \dots (2)$$

$$-46i_2 + (46 + 67)i_3 = -5 \dots (3)$$

By solving equation (1), (2) and (3) we get,

$$i_3 = I_{L3} = -32.8 \text{ mA}$$

Now,

$$I_{L1} + I_{L2} + I_{L3} = (14.6 + 15 - 32.8) \text{ mA} = -3.2 \text{ mA} = I_L$$

Hence, the Superposition theorem is verified.


Calculated values	Experimental Values
$I_{L1} = 14.6 \text{ mA}$	$I_{L1} = 14.5 \text{ mA}$
$I_{L2} = 15 \text{ mA}$	$I_{L2} = 14.8 \text{ mA}$
$I_{L3} = -32.8 \text{ mA}$	$I_{L3} = -32 \text{ mA}$
$I_L = -3.2 \text{ mA}$	$I_L = -3 \text{ mA}$

There is discrepancy because in experimental values there is error while measuring the exact value and also we did not get the exact value of the resistors. That is what the values are different.



2. Solve the circuits of Figures 1 through 4 using PSpice. Include the PSpice circuits with only currents shown. The PSpice solution show that the superposition theorem holds. Compare the PSpice solutions with the theoretical solutions and comment on any discrepancy found.

Ans:

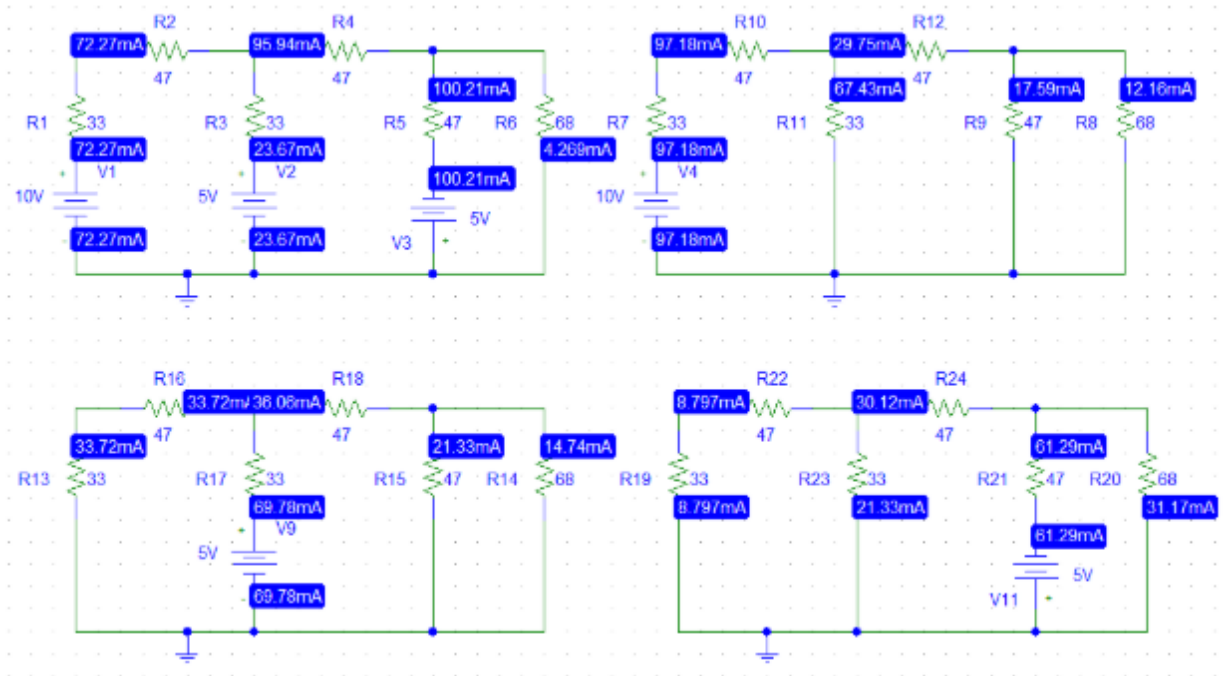

Here,

$$I_{L1} = 12.16mA$$

$$I_{L2} = 14.739mA$$

$$I_{L3} = 31.168mA = -31.168mA \text{ (At opposite direction)}$$

So,

$$I_{L1} + I_{L2} + I_{L3} = (12.16 + 14.739 - 31.168)mA = -4.269mA = I_L$$

So, it holds the superposition theorem.

**Comparison between PSpice solutions with the theoretical solutions,**

<b>PSpice values</b>	<b>Theoretical Values</b>
$I_{L1} = 12.16mA$	$I_{L1} = 12.16mA$
$I_{L2} = 14.739mA$	$I_{L2} = 14.739mA$
$I_{L3} = -31.168mA$	$I_{L3} = -31.168mA$
$I_L = -4.269mA$	$I_L = -4.269mA$

So, there is no discrepancy between PSpice values and theoretical values.

## Discussion:

The experiment successfully verified the superposition theorem through theoretical calculation, experimental measurement, and PSpice simulation. Theoretical and PSpice results matched exactly, confirming the accuracy of analytical methods. Experimental results showed small discrepancies, mainly caused by resistor tolerances, measurement errors, and internal resistance of voltage sources, which are absent in the idealized models. Despite these differences, the measured total current closely matched the sum of individual source contributions, demonstrating the theorem's practical validity. This experiment highlights that while theory and simulation provide precise results, real-world measurements may vary slightly due to non-ideal components and environmental factors.

