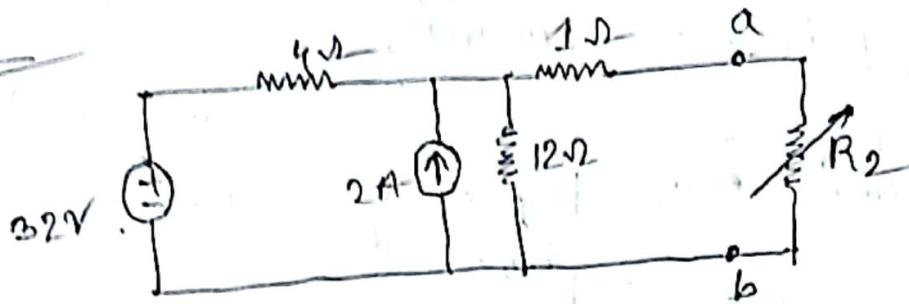



FinalTheremin Theorem.

* $V_{th} \rightarrow$ Theremin equivalent Voltage

* $R_{th} \rightarrow$ Theremin \rightarrow Resistance

Q1:

Draw the Theremin equivalent circuit.

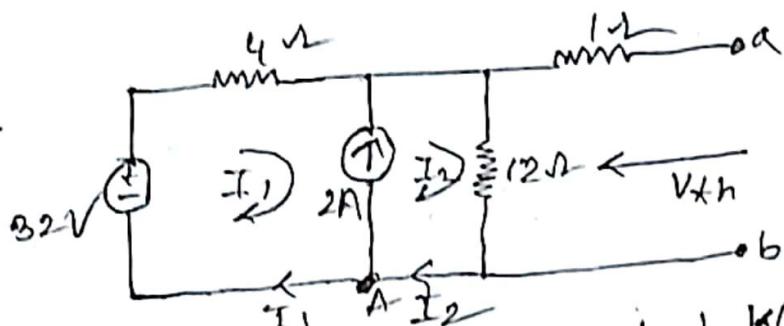Solve

Applying KVL in supermesh,

$$-32 + 4I_1 + 12I_2 = 0$$

$$\Rightarrow 4I_1 + 12I_2 = 32$$

$$\Rightarrow I_1 + 3I_2 = 8 \quad \text{--- (1)}$$

KCL in node A,

$$I_2 = 2 + I_1 \quad \text{--- (2)}$$

$$\Rightarrow I_1 - I_2 = -2$$

Solving eqv,

$$\therefore I_2 = 2.5 \text{ A}$$

$$\therefore V_{th} = I_2 \times 12$$

$$= 2.5 \times 12$$


$$= 30 \text{ V}$$

$$R_{Th} = (4 \parallel 12) + 1$$


$$= \frac{4 \times 12}{4+12} + 1$$


$$= 3 + 1$$

$$= 4 \Omega$$

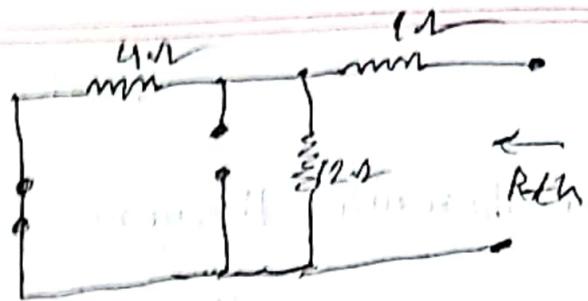

Thevenin equivalent circuit,

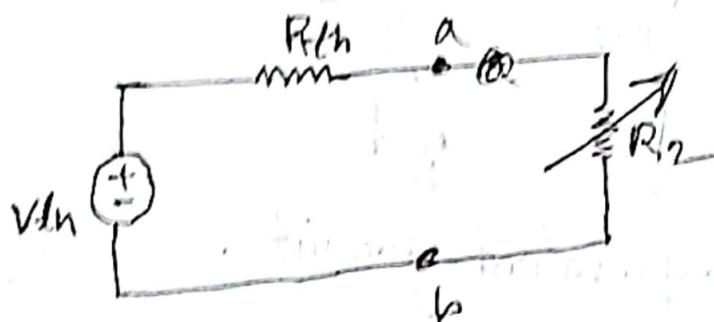

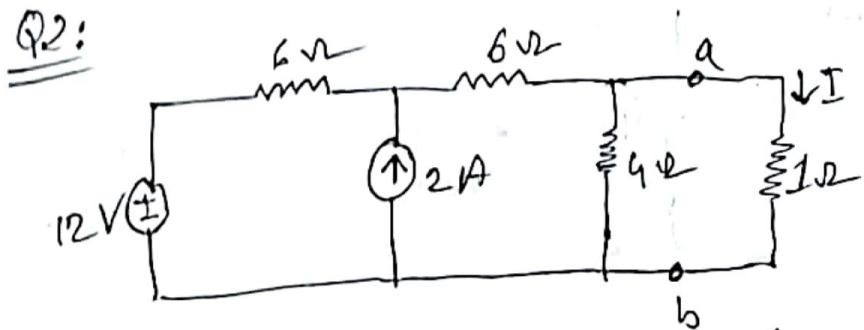
2Q2:

Draw the Thévenin equivalent circuit and find I ,

SOLVE

Applying KVL in supermesh,

$$-12 + 6I_1 + 6I_2 + 4I_2 = 0$$

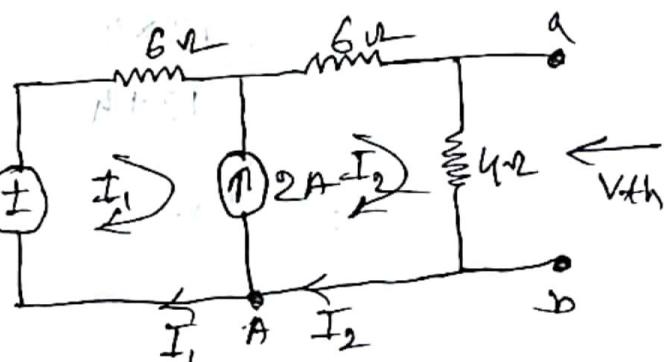

$$\Rightarrow 6I_1 + 10I_2 = 12$$

$$\Rightarrow 3I_1 + 5I_2 = 6 \quad \text{--- (1)}$$

Applying KCL in node -A

$$I_2 = I_1 - 2$$


$$\Rightarrow I_1 - I_2 = 2 \quad \text{--- (2)}$$

Solving eq \Rightarrow

$$I_1 = 3A$$

$$I_2 = 0A$$


$$V_{th} =$$

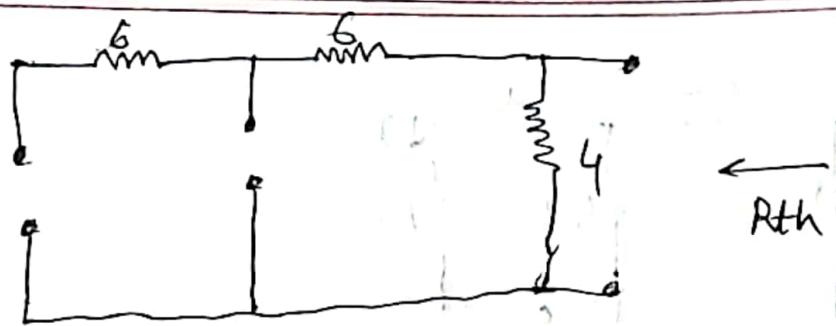

$$R_{th} = \frac{(6+6)114}{6+6+4}$$



$$= \frac{12 \times 4}{12+4}$$

$$= 3 \Omega$$

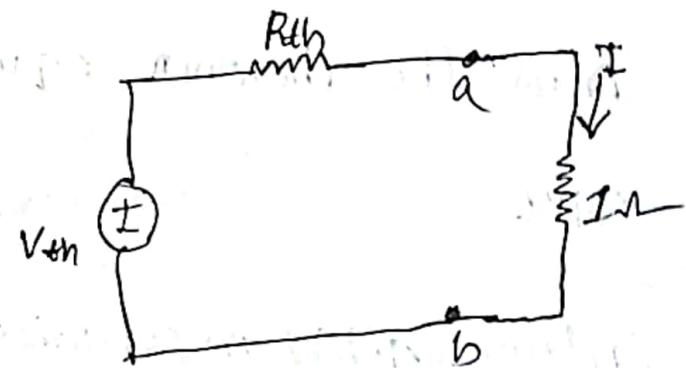

Applying CDR,

$$I = I_2 \times \frac{R_{th}}{R_{th} + 1}$$

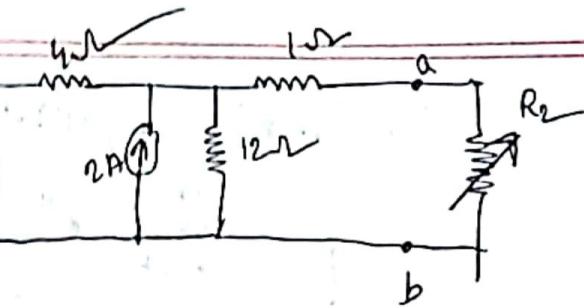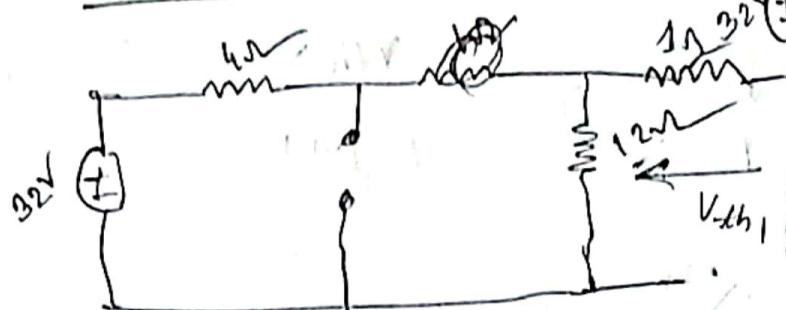
3Superposition

Using VDR,

$$V_{th1} = \frac{12 \times 4}{6+6+4} = 3V$$

Applying CDR,
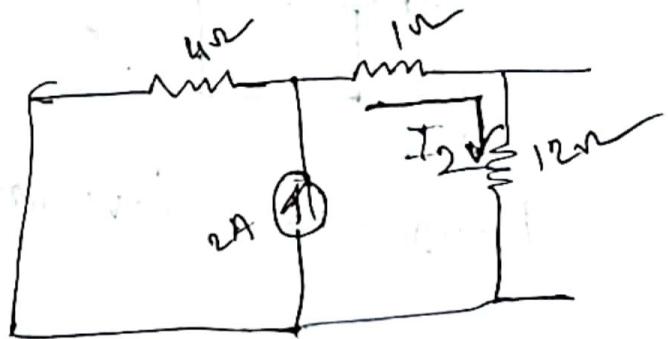
$$I_2 = \frac{2 \times 6}{6+6+4} = \frac{3}{4} A$$



Using Ohm's Law,

$$\therefore R_{th} = (6+6) // 4$$

$$V_{th2} = I_2 \times 4$$

$$= \frac{3}{4} \times 4$$

$$= 3V$$


$$= \frac{12 \times 4}{12+4}$$

$$= 3V$$


$$V_{thb} = V_{th1} + V_{th2}$$

$$= 3 + 3$$

$$= 6V$$

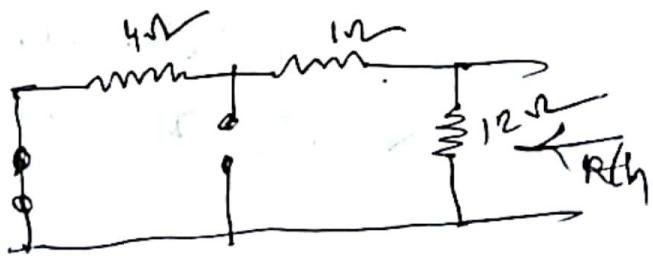


Thevenin equivalent circuit.

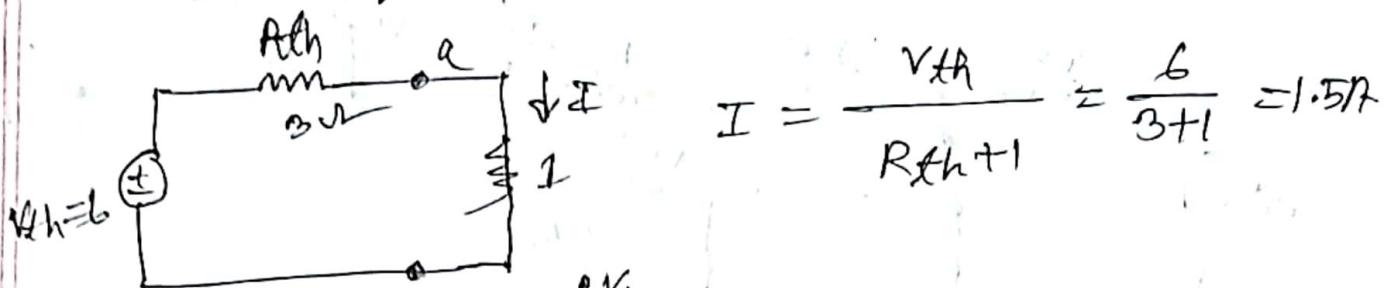

4

Q3:

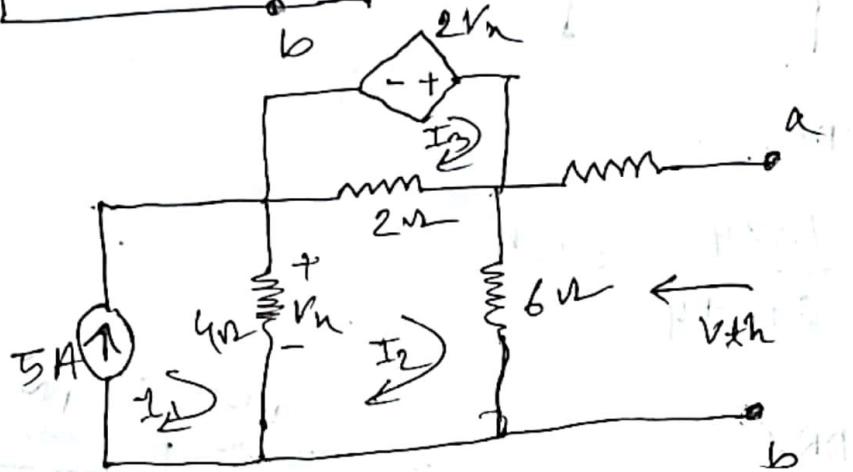

Draw the Thevenin equivalent circuit.

Solve

From mesh-1,

$$I_1 = 5 \text{ A}$$

Applying KVL in mesh-2 \rightarrow

$$\therefore -4I_1 + 12I_2 - 2I_3 = 0$$

$$\Rightarrow -2I_1 + 6I_2 - I_3 = 0$$

$$\Rightarrow 6I_2 - I_3 = 10 \quad \text{--- (1)}$$

$$4(I_2 - I_1) + 2(I_2 - I_3) + 6I_2 = 0$$

$$\Rightarrow 4I_2 - 4I_1 + 2I_2 - 2I_3 + 6I_2 = 0$$

$$\Rightarrow -4I_1 + 12I_2 - 2I_3 = 0$$

$$\Rightarrow 2I_1 - 6I_2 + I_3 = 0$$

$$\xleftarrow{\text{Same}} \Rightarrow 6I_2 - I_3 = 10 \quad \text{--- (1)}$$

mesh-3

$$2(I_3 - I_2) - 2V_n = 0$$

$$\Rightarrow 2I_3 - 2I_2 - 2V_n = 0$$

$$\Rightarrow 2I_3 - 2I_2 - 2(4I_2 - 20) = 0$$

$$\Rightarrow 2I_3 - 2I_2 - 8I_2 + 40 = 0$$

$$\Rightarrow -10I_2 + 2I_3 = -40$$

$$\Rightarrow 10I_2 - 2I_3 = 40$$

$$\Rightarrow 5I_2 - I_3 = 20 \quad \text{--- (1)}$$

Solving eq $\rightarrow I_2 = -10 \text{ A}$

$$v_{th} = I_2 \times 6$$

$$= -10 \times 6$$

$$= -60 \text{ V}$$

Using ohms law,
from mesh-2,

$$V_n = -4(I_2 - I_1)$$


$$= -4I_2 + 4I_1$$

$$= 4I_2 - 20$$

Mesh - 2

$$\Rightarrow 4I_b + 2(I_b - I_a) + 6(I_b - I_c) = 0$$
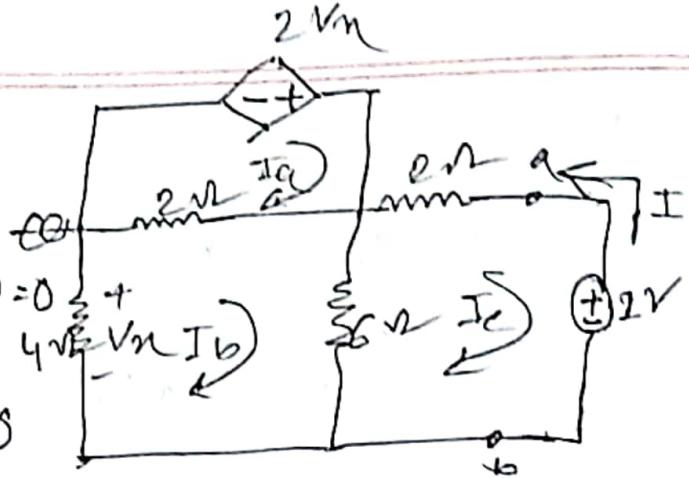
$$\Rightarrow 4I_b + 2I_b - 2I_a + 6I_b - 6I_c = 0$$



$$\Rightarrow -2I_a + 12I_b - 6I_c = 0$$

$$\Rightarrow I_a - 6I_b + 3I_c = 0 \quad \text{--- (1)}$$

Mesh - 1

$$2(I_a - I_b) - 2V_m = 0$$

$$V_m = -4I_b$$

$$\Rightarrow 2I_a - 2I_b - 2$$

Mesh - 3

$$6(I_c - I_b) + 2I_c + 2 = 0$$

$$\Rightarrow 6I_c - 6I_b + 2I_c = -2$$

$$\Rightarrow 6I_b - 8I_c = 2 \quad \text{--- (2)}$$

$$\Rightarrow 3I_b - 4I_c = 1 \quad \text{--- (III)}$$

calculate, $I = -I_c$

Grad

H.W


R_{th}

V_{th}

5

Norton Theorem



Q4:

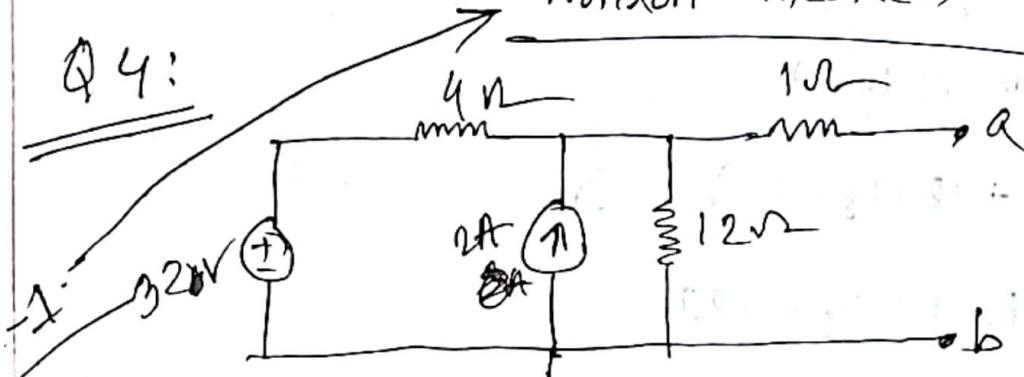


$$I_N = \frac{V_{th}}{R_{th}} = \frac{30}{4} = 7.5A$$

$R_N = \text{Norton eq resistance}$
 $I_N = \text{Norton eq current}$

$$I_N = \frac{V_{th}}{R_{th}}$$

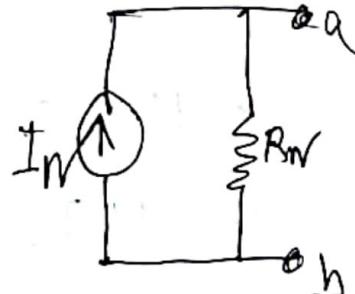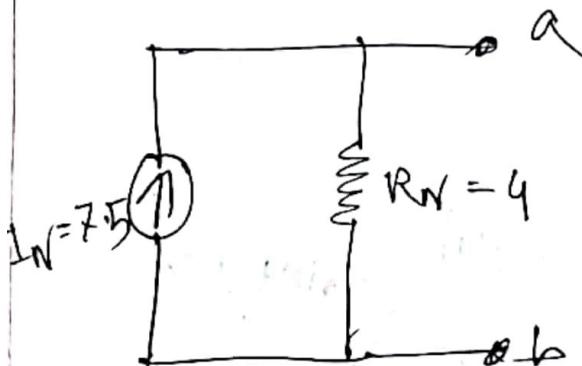

Type - 2

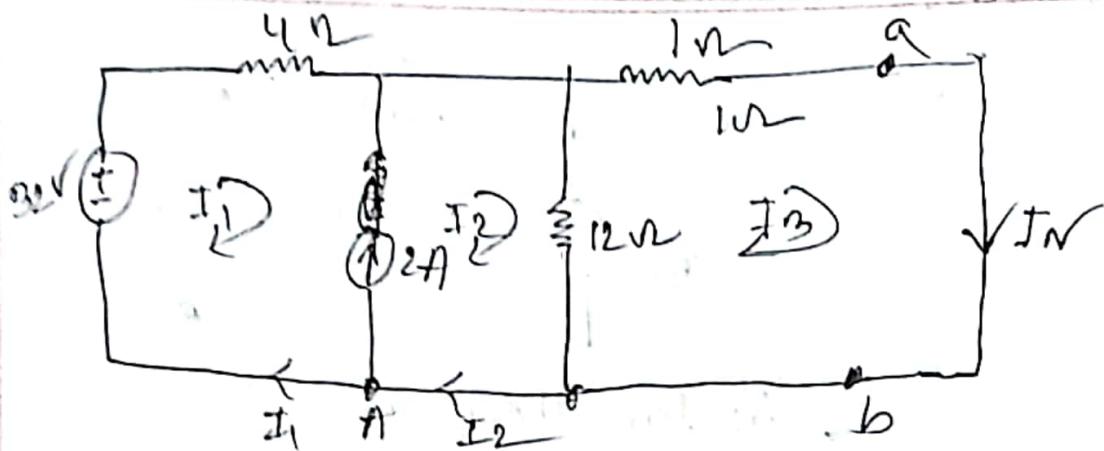

From supermesh →

$$-32 + 4I_1 + 12(I_2 - I_3) = 0$$

$$\Rightarrow -32 + 4I_1 + 12I_2 - 12I_3 = 0$$

$$\Rightarrow I_1 + 3I_2 - 3I_3 = 8 \quad \text{--- (1)}$$

from Mesh - 3

$$12(I_3 - I_2) + 1I_3 = 0$$

$$\Rightarrow 12I_3 - 12I_2 + I_3 = 0$$

$$\Rightarrow 12I_2 - 13I_3 = 0 \quad \text{--- (2)}$$

KCL in node - A

$$I_2 = I_1 + 2$$

$$\Rightarrow I_2 - I_1 = 2 \quad \text{--- (3)}$$

solving eqn

$$I_1 = 6.12$$

$$I_2 = 8.12$$

$$I_3 = 2.5 = I_N$$

$$I_N = I_3 = 2.5 \text{ A}$$

R_{th}

V_{th}/IN

$$\text{Power} = I_t^V R_2$$

$$= \left(\frac{V_{th}}{R_{th} + R_L} \right)^V \times R_2$$

max Power Transfer Theorem:

$$R_{th} = R_L$$

$$= \frac{V_{th}^V}{(R_{th} + R_L)^V} \times R_{th}$$

$$= \frac{V_{th}^V}{(2R_{th})^V} \times R_{th}$$

$$P_{max} = \frac{V_{th}^V}{4R_{th}}$$




$$\therefore P_{max} = \frac{30^V}{4 \times 4} W$$

math 1


$$= 56.25 W$$

AC


Date: 11-08-2025

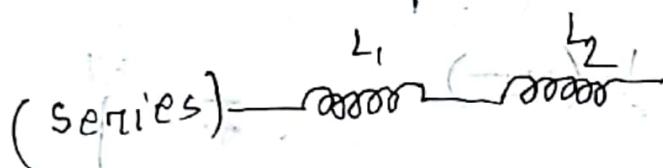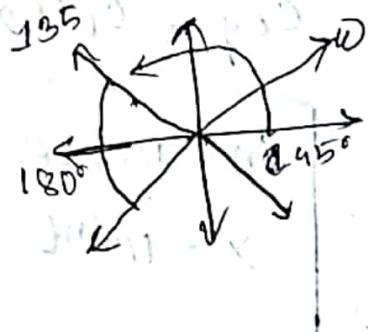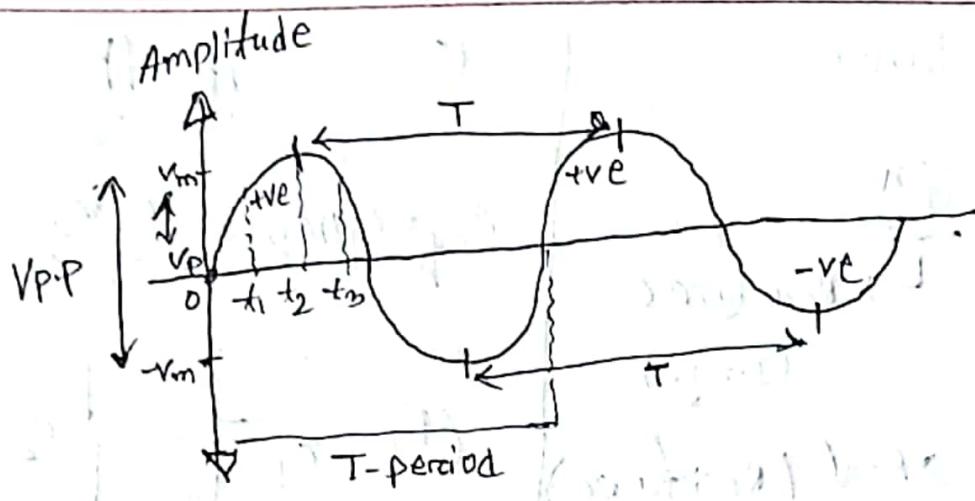

$$L_{eq} = L_1 + L_2$$

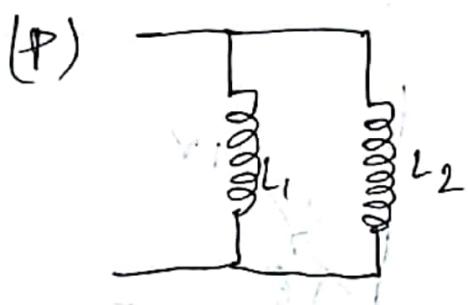

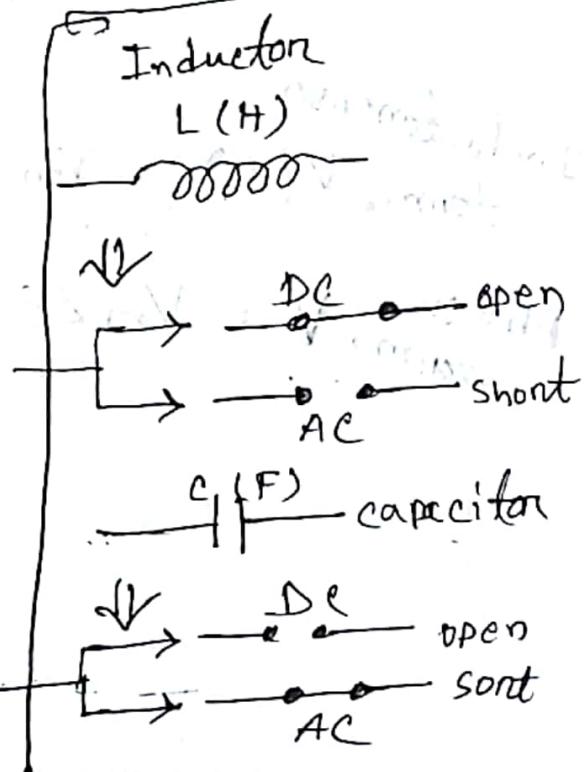
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$



$\boxed{Z \Rightarrow \text{Impedance}}$

$$Z = R + jX$$

↓
Reactance
(Img.)
Real (Resistance)

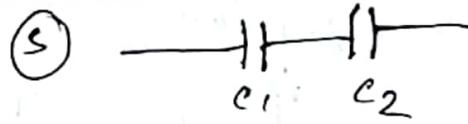

$$C_{eq} = C_1 || C_2 = \frac{C_1 \times C_2}{C_1 + C_2}$$



$$\text{Rec} \rightarrow r + jy = r(\cos\theta + j\sin\theta)$$

$$\text{Pol} \rightarrow r\angle\theta \rightarrow r = \sqrt{r^2 + y^2}$$

$$\theta = \tan^{-1} \frac{y}{r}$$


$$C_{eq} = C_1 + C_2$$

$$r = r \cos\theta \\ y = r \sin\theta$$

Admittance, $y = \frac{1}{Z} = \frac{1}{r} (\cos\theta + j\sin\theta)$


Instantaneous form, $V(t) = V_m \sin(\omega t + \theta) V$

phasor form, $V = V_m \angle \theta V$





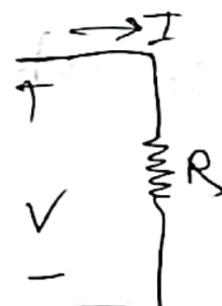


phase

difference = 0

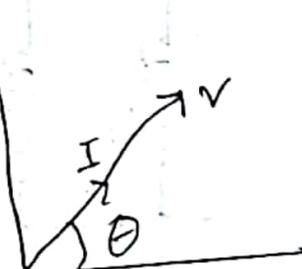


$$I = V = \theta = 0$$

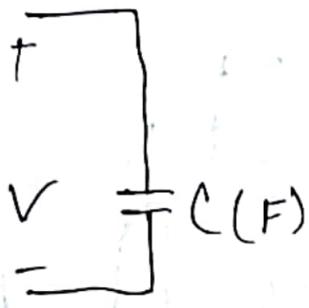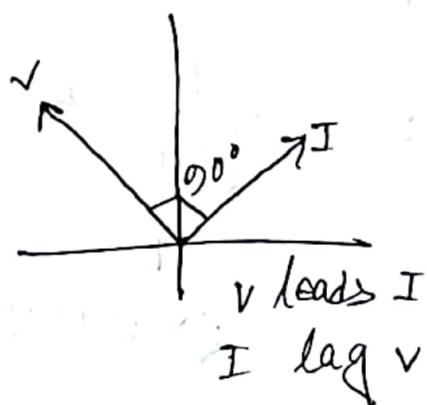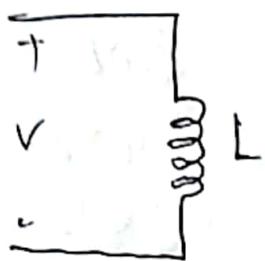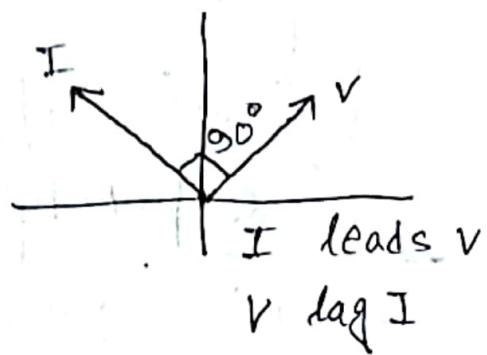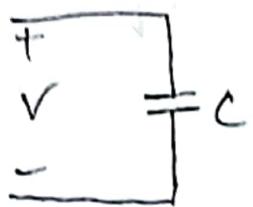

\vec{F} to \vec{r}


$$F = \frac{1}{j\omega C} \vec{v} \quad \left[\frac{1}{j} = -\frac{1}{j} \right]$$

$$= -\frac{1}{j\omega C}$$

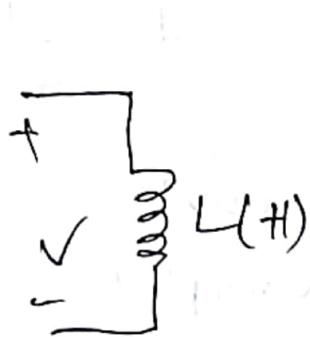

\vec{H} to \vec{r}
Hanging

$$H = j\omega L \vec{v}$$

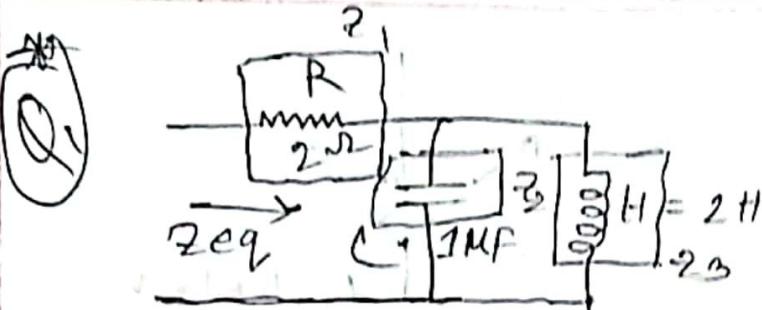

To find Z_{eq} when
 $\omega = 4 \text{ rad/s}$?

$$Z = R + j\omega L = 2 + 0$$

$$Z_1 = 2 \cancel{\text{ohm}}$$

$$\frac{1}{j} = -j$$

$$Z_2 = \frac{1}{j\omega C} \cancel{\text{ohm}}$$

$$= \frac{1}{j \times 4 \times 1 \times 10^{-6}} \cancel{\text{ohm}}$$

$$= -j(2.5 \times 10^5) \cancel{\text{ohm}}$$


$$Z_3 = j\omega L$$

$$= j4 \times 2$$

$$= j8 \cancel{\text{ohm}}$$

$$Z_{eq} = Z_1 + Z_2 // Z_3$$
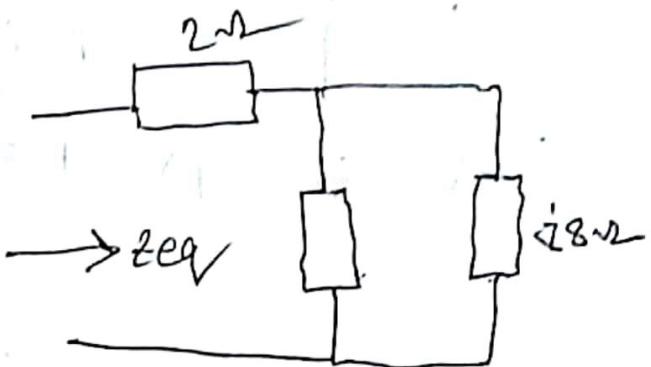
$$= 2 + \frac{-j(2.5 \times 10^5) \times j8}{-j(2.5 \times 10^5) + j8}$$



rect \rightarrow polar

$$= (2 + j8) \cancel{\text{ohm}}$$


$$= 2\sqrt{17} \angle 75.96^\circ$$

[using calculator]

* mode & complex

$$* \frac{-(2.5 \times 10^5)j \times 8j}{-(2.5 \times 10^5)j + 8j}$$

* i = ENG (cal)

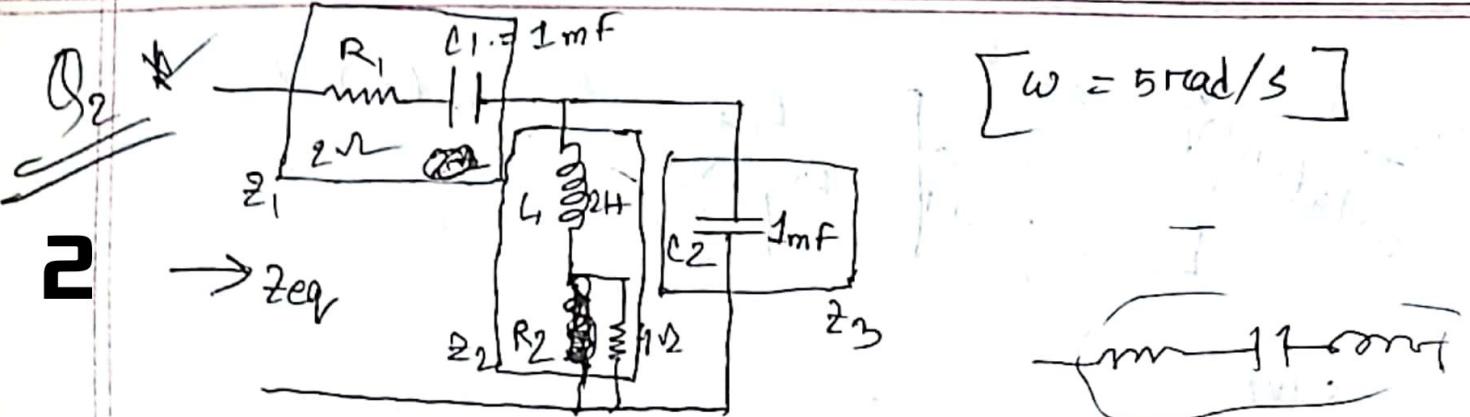

2

$\rightarrow z_{eq}$

$$z_1 = 2 + \frac{1}{j\omega 5 \times 1 \times 10^{-3}}$$

$$= (2 - j(200)) \Omega$$

$$z_2 = j\omega L + R$$

$$= j\omega 5 \times 2 + 1$$

$$= (4 + j10) \Omega$$

$$z_3 = \frac{1}{j\omega C}$$


$$= \frac{1}{j5 \times 1 \times 10^{-3}}$$


$$= (-j200) \Omega$$

$$z_{eq} = z_1 + (z_2 // z_3)$$

$$= (2 - j200) + \frac{(4 + j10)(-j200)}{(4 + j10) + (-j200)}$$

$$= 6.4 - j189.6 \Omega$$

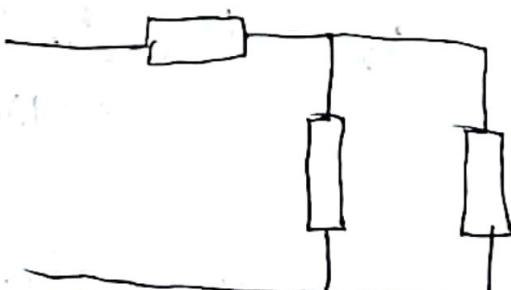

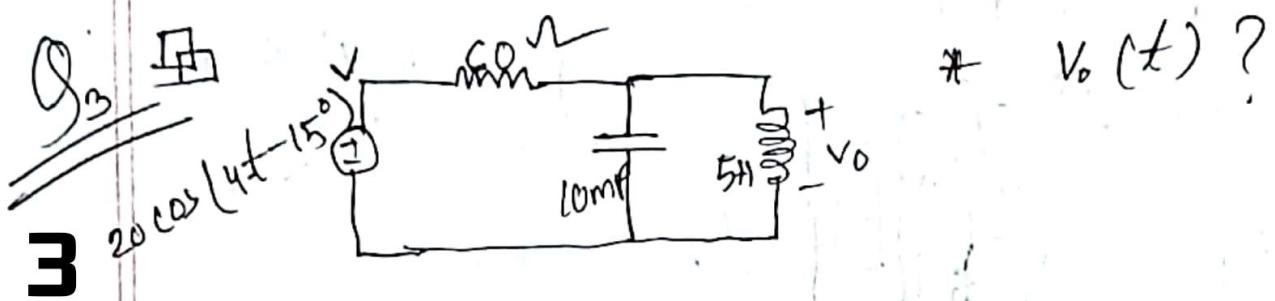

Solve

$$20 \cos(4t - 15^\circ) \Rightarrow 20 \angle -15^\circ \text{ V}$$

$$\omega = 4 \text{ rad/s}$$


$$10\text{mF} \Rightarrow \frac{1}{j\omega C} = \frac{1}{j4 \times 10 \times 10^{-3}} = -j25 \Omega$$

$$5\text{H} \Rightarrow j\omega L = j4 \times 5 = j20 \Omega$$

$$-\dot{j}25 \parallel j20 = \frac{-\dot{j}25 \times j20}{-\dot{j}25 + j20} = \dot{j}100 \Omega$$

Using NDR,
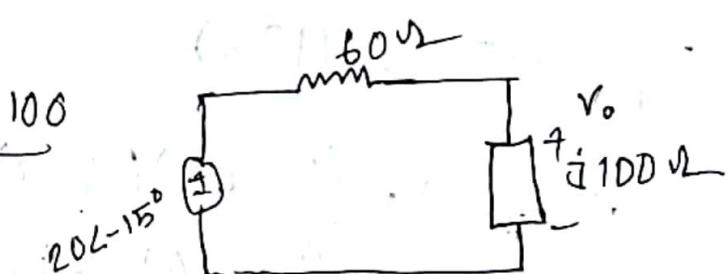
$$V_o = \frac{20 \angle -15^\circ \times \dot{j}100}{60 + \dot{j}100}$$




$$= 16.49 + j4.70$$

$$= 17.15 \angle 15.96^\circ \text{ V}$$

$$\therefore V_o(t) = 17.15 \cos(4t + 15.96^\circ) \quad \underline{\text{Ans}}$$

Q4

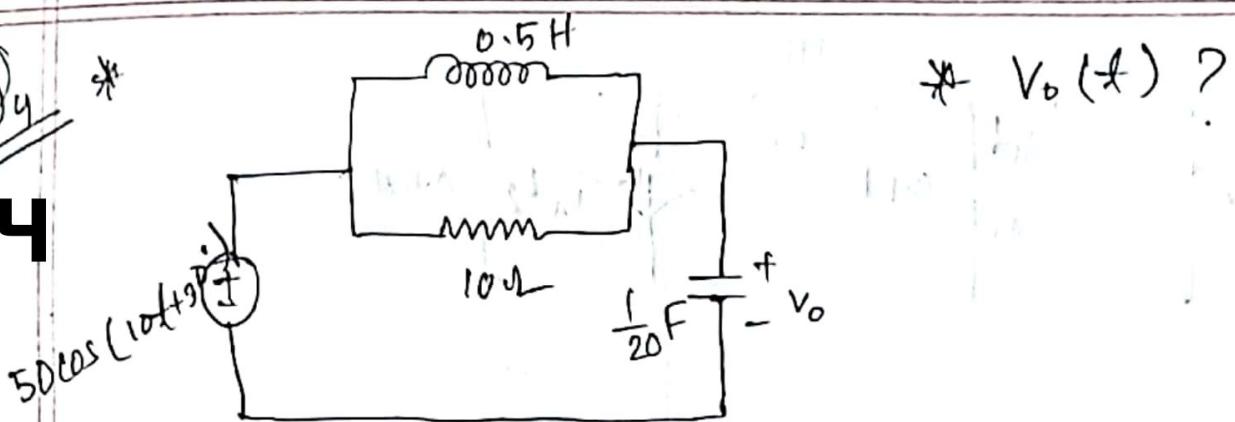

SOLVE

$$50\cos(10t + 30^\circ) \Rightarrow 50 \angle 30^\circ \text{ V}$$

$$\omega = 10 \text{ rad/s}$$

$$0.5 \text{ H} \Rightarrow j\omega L = j10 \times 0.5 = j5$$

$$\frac{1}{20} \text{ F} \Rightarrow \frac{1}{j\omega C} = \frac{1}{j10 \times 0.05} = -j2$$

$$\frac{j5}{j5 + 10} = \frac{j5 \times 10}{j5 + 10} = 2 + j4$$


Using VDR,

$$V_o = \frac{50 \angle 30^\circ \times (-j2)}{-j2 + (2 + j4)}$$

$$= -9.15 - j34.15$$

$$= 35.35 \angle -104.9^\circ$$

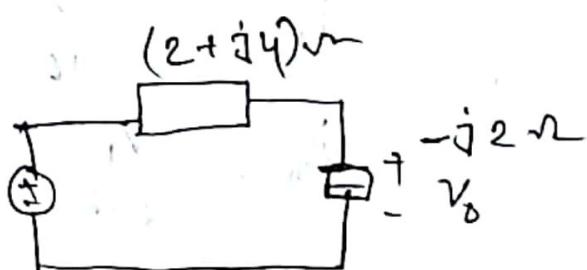
$$V_o(t) = 35.35 \cos(10t - 104.9^\circ) \text{ Ans.}$$



Nodal Analysis

Date : 13-08-25

5

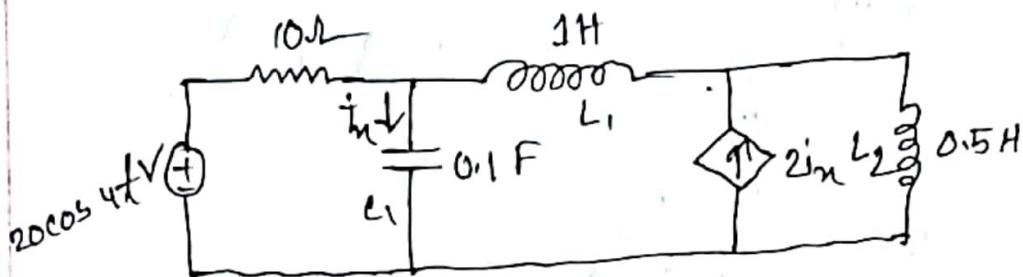

Solve

$$20\cos 4t \text{ V} \Rightarrow 20\angle 0^\circ \text{ V}, \omega = 4 \text{ rad/s}$$

$$0.1 \text{ F} \Rightarrow \frac{1}{j\omega C_1} = \frac{1}{j4 \times 0.1} = -j2.5 \Omega$$

$$1 \text{ H} \Rightarrow j\omega L_1 = j4 \times 1 = j4 \Omega$$

$$0.5 \text{ H} \Rightarrow j\omega L_2 = j4 \times 0.5 = j2 \Omega$$

Using Ohm's Law,


$$i_1 = \frac{20\angle 0^\circ - v_1}{10}$$

$$i_n = \frac{v_1}{-j2.5}$$

$$i_2 = \frac{v_1 - v_2}{j4}$$

$$i_3 = 2i_n = \frac{2v_1}{-j2.5}$$

$$i_4 = \frac{v_2}{j2}$$

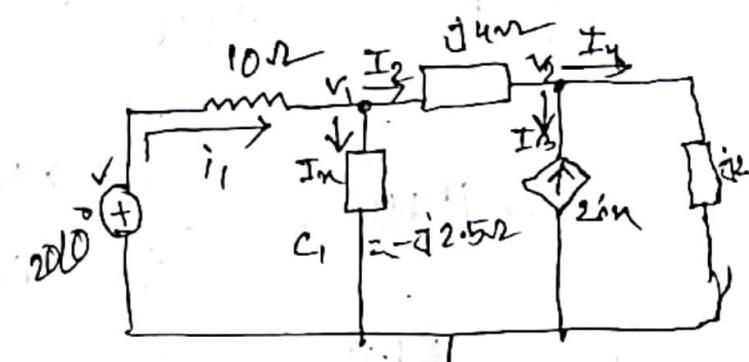

Applying KCL in node - $V_1 \Rightarrow$

$$i_1 = i_m + i_2$$

$$\Rightarrow \frac{20\angle 0^\circ - V_1}{10} = -\frac{jV_1}{-j2.5} + \frac{V_1 - V_2}{j4}$$

$$\Rightarrow \frac{20\angle 0^\circ - V_1}{10} = \frac{j4V_1 - V_1 j2.5 + V_2 j2.5}{(-j2.5) \times j4}$$

$$\Rightarrow \frac{20\angle 0^\circ - V_1}{10} = \frac{j4V_1 - j2.5V_1 + j2.5V_2}{10}$$

$$\Rightarrow 20\angle 0^\circ - V_1 = j9V_1 - j2.5V_1 + j2.5V_2$$

$$\Rightarrow 20\angle 0^\circ - V_1 = j1.5V_1 + j2.5V_2$$

$$\Rightarrow V_1 + j1.5V_1 + j2.5V_2 = 20\angle 0^\circ \quad \boxed{1}$$

$$\Rightarrow V_1(1 + j1.5) + j2.5V_2 = 20\angle 0^\circ$$

Applying KCL in node 0 - $v_2 \leq$

$$i_2 + i_3 = i_4$$

$$\Rightarrow \frac{v_1 - v_2}{j4} + 2i_m = \frac{v_2}{j2}$$

$$\Rightarrow \frac{v_1 - v_2}{j4} + 2 \times \frac{v_1}{-j2.5} = \frac{v_2}{j2}$$

$$\Rightarrow \frac{-j2.5v_1 + j2.5v_2 + \cancel{i_4}(2v_1)}{j4 \times (-j2.5)} = \frac{v_2}{j2}$$

$$= \frac{11v_1 + 15v_2}{10} = \frac{v_2}{j2}$$

$$\Rightarrow -11v_1 - 5v_2 = 10v_2 \quad \rightarrow \text{---}$$

$$\Rightarrow -11v_1 - 5v_2 - 10v_2 = 0 \quad \checkmark$$

$$\Rightarrow -11v_1 - 15v_2 = 0$$

$$\Rightarrow 11v_1 + 15v_2 = 0 \quad \leftarrow \text{---} \quad (1)$$

$$\Rightarrow 5v_1 - 5v_2 - 16v_1 - 10v_2 = 0$$

$$\Rightarrow 5v_1 - 5v_2 - 16v_1 - 10v_2 = 0$$

$$\Rightarrow$$

Using cramer's rule,

$$\begin{bmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20\angle 0^\circ \\ 0 \end{bmatrix}$$


$$\Delta = \begin{bmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{bmatrix} = (15 + j22.5) - (j2.5) = 15 - j5$$

$$\Delta_1 = \begin{bmatrix} 20\angle 0^\circ & j2.5 \\ 0 & 15 \end{bmatrix} = 20\angle 0^\circ \times 15 = 300\angle 0^\circ$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{15 + j5}{300\angle 0^\circ} = \frac{18 + j6}{15 - j5} = 18 + j6$$

$$I_n = \frac{V_1}{-j2.5} = \frac{18 + j6}{-j2.5} = 2.4 - j2.2$$

6

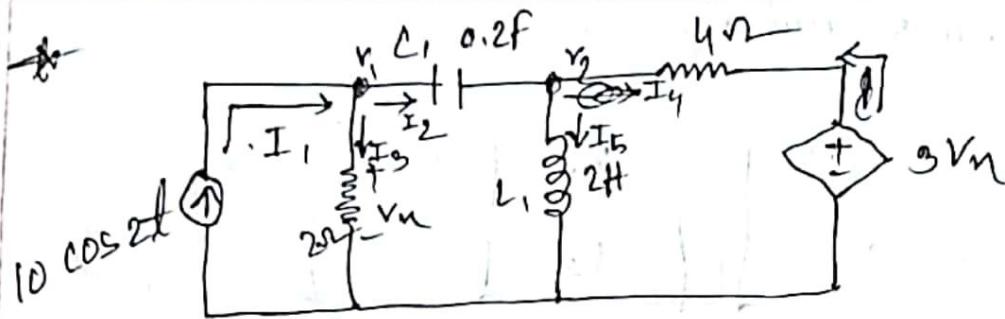

solve

$$10 \cos 2t \Rightarrow 10 \angle 0^\circ, \omega = 2 \text{ rad/s}$$

$$0.2F \Rightarrow \frac{1}{j\omega C_1} = \frac{1}{j2 \times 0.2} \\ = -j2.5 \text{ nH}$$

$$I_1 = 10 \angle 0^\circ$$

$$I_2 = \frac{V_1 - V_2}{-j2.5}$$

$$2H \Rightarrow j\omega L_1 = j2 \times 2 \quad \cancel{I_3} = \frac{V_1}{2} \\ = j4 \text{ V} \quad I_4 = \cancel{\frac{3V_n - V_2}{4}}$$

$$I_5 = \frac{V_2}{j4} = \frac{j3 \times 2 I_3 - V_2}{4} \\ = \frac{6 I_3 - V_2}{4}$$

$$V_n = 2 I_3 = \frac{6 \cdot \frac{V_1}{2} - V_2}{4} \\ = \frac{3V_1 - V_2}{4}$$

Applying KCL in node v_1 ,

$$I_1 = I_2 + I_3$$

$$\Rightarrow 10\angle 0^\circ = \frac{v_1 - v_2}{-j2.5} + \frac{v_1}{2}$$

$$\Rightarrow 10\angle 0^\circ = \frac{2v_1 - 2v_2 - j2.5v_1}{-j2.5 \times 2}$$

$$\Rightarrow -j50 = 2v_1 - 2v_2 - j2.5v_1$$

$$\Rightarrow v_1(2 - j2.5) - 2v_2 + j50 = 0$$

Applying KCL in node v_2 ,

$$I_4 + I_2 = I_5$$

$$\Rightarrow \frac{3v_1 - 6}{j} + \frac{v_1 - v_2}{-j2.5} = \frac{v_2}{j4}$$


$$\Rightarrow \frac{-j7.5v_1 + j2.5v_2 + 4v_1 - 4v_2}{4 \times (-j2.5)} = \frac{v_2}{j4}$$

$$\Rightarrow \frac{v_1(4 - j7.5) + v_2(j2.5 - 4)}{-j10} = \frac{v_2}{j4}$$

$$\Rightarrow v_1(30 + j16) + v_2(-10 + j16) = -j10v_2$$

$$v_2 = 33.42 \angle 57.12^\circ V$$
$$v_1 = 11.325 \angle 60.01^\circ V$$

7

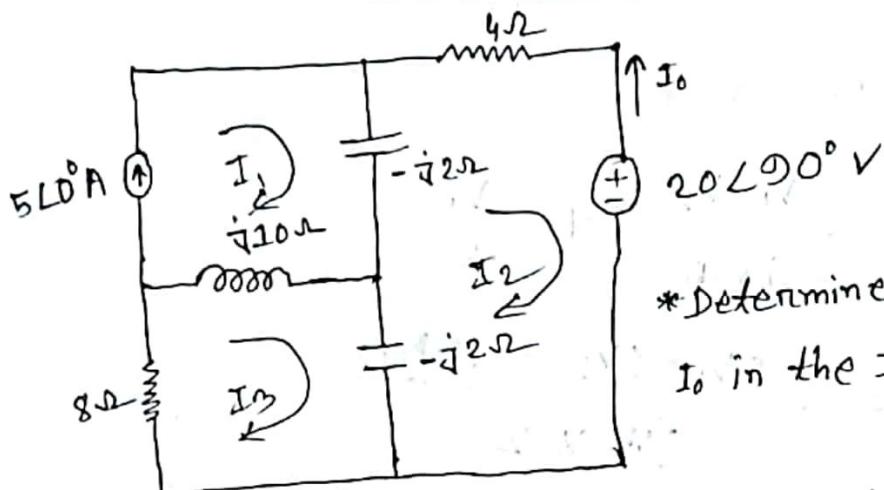Mesh Analysis

*Determine the current I_o in the following circuit.

Solve:

from mesh-1,

$$I_1 = 5 \angle 0^\circ \text{ A}$$

From mesh-3,

$$8I_3 + j10(I_3 - I_1) + (-j2)(I_3 - I_2) = 0$$

$$\Rightarrow 8I_3 + \cancel{j10I_3} - \cancel{j10I_1} - \cancel{j2I_3} + j2I_2 = 0$$

$$\Rightarrow \cancel{8I_3} + \cancel{j10I_3} - \cancel{j10I_1} - \cancel{j2I_3} + (8 + j8)I_3 = 0$$

$$\Rightarrow -j10 \times 5 \angle 0^\circ + j2I_2 + (8 + j8)I_3 = 0$$

$$\Rightarrow -j50 + j2I_2 + (8 + j8)I_3 = 0$$

$$\Rightarrow j2I_2 + (8 + j8)I_3 = j50 \quad \text{--- (1)}$$

8

From mesh-2,

$$(-j2)(I_2 - I_3) + (-j2)(I_2 - I_1) + 4I_2 + 20 \angle 90^\circ = 0$$

$$\Rightarrow -j2I_2 + j2I_3 - j2I_2 + j2I_1 + 4I_2 + 20 \angle 90^\circ = 0$$

$$\Rightarrow j2I_1 + (4 - j4)I_2 + j2I_3 = -20 \angle 90^\circ \quad \text{--- (1)}$$

$$\Rightarrow j2 \times 5 \angle 0^\circ + (4 - j4)I_2 + j2I_3 = -20 \angle 90^\circ$$

$$\Rightarrow \cancel{(4 - j4)I_2} + j2I_3 = \frac{-j30}{-20 \angle 90^\circ} \quad \text{--- (1)}$$

Using crammer's rule,

$$\begin{bmatrix} j2 & 8 + j8 \\ 4 - j4 & j2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} j50 \\ -j30 \end{bmatrix}$$

$$D = \begin{bmatrix} j2 & 8 + j8 \\ 4 - j4 & j2 \end{bmatrix} = -4 - 64 = -68$$

$$D_1 = \begin{bmatrix} j50 & 8 + j8 \\ -j30 & j2 \end{bmatrix}$$


$$D_2 = \begin{bmatrix} j2 & j50 \\ 4 - j4 & -j30 \end{bmatrix} = 60 - (200 + 200j)$$

$$= 340 - j240$$

$$I_2 = \frac{a_2}{\Delta} = \frac{340 - j240}{68} = 6.12 \angle -35.21^\circ A$$

$$\therefore I_0 = I_2 = -6.12 \angle -35.21^\circ A$$

9

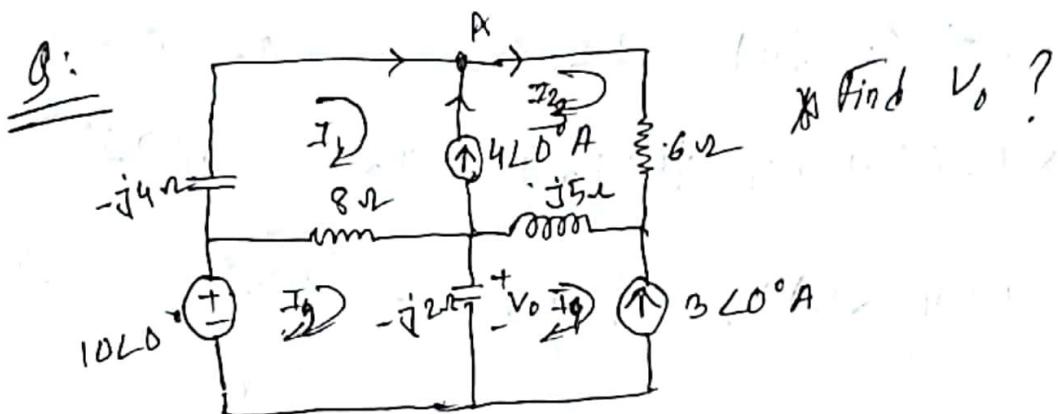

From mesh - 1,

$$-j4 - 4L0^\circ + 8(I_1 - I_2) = 0$$

$$\Rightarrow -j4 - 4L0^\circ + 8I_1 - 8I_2 = 0$$

\Rightarrow

From mesh - 4,

$$I_4 = -3L0^\circ A$$

From ~~KVL~~ KVL in supermesh,

$$-j4 + 6I_3 + j5(I_2 - I_4) + 8(I_1 - I_2) = 0$$

$$\Rightarrow -j4 + 6I_3 + j5I_2 - j5I_4 + 8I_1 - 8I_2 = 0$$

$$\Rightarrow (8 - j4)I_1 + (j5 - 8)I_2 + 6I_3 - j5I_4 = 0$$

$$\Rightarrow 8I_1 + (\frac{1}{2}5 - 8)I_2 + 6I_3 - \sqrt{2}(- / 3\angle 0^\circ) = 0$$

KVL in supermesh.

$$-j4I_1 + 6I_3 + j5(I_2 - I_4) + 8(I_1 - I_2) = 0$$

$$\Rightarrow (8 - j4)I_1 - 8I_2 + (6 + j5)I_3 = -j15 \quad \text{--- (1)}$$

KVL in mesh - 2

$$-10\angle 0^\circ + 8(I_2 - I_1) - j2(I_2 - I_4) = 0$$

$$\Rightarrow 8I_2 - 8I_1 - j2I_2 + j2I_4 = 10\angle 0^\circ$$

$$\Rightarrow -8I_1 + (8 - j2)I_2 + j2I_4 = 10\angle 0^\circ$$

$$\Rightarrow -8I_1 + (8 - j2)I_2 = 10\angle 0^\circ - j2(-3\angle 0^\circ) = \cancel{-6}$$

$$= 11.66\angle 30.96^\circ \quad \text{--- (11)}$$

Applying KCL in node A,

$$I_3 = I_1 + 4\angle 0^\circ$$

$$\Rightarrow I_3 - I_1 = 4\angle 0^\circ$$

Using Cramen's rule,

$$\begin{bmatrix} 8 - j4 & -8 & 6 + j5 \\ -8 & 8 - j2 & 0 \\ -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -j15 \\ 11.66 \angle 30.96^\circ \\ 4 \angle 0 \end{bmatrix}$$

$$I = \begin{bmatrix} 8 - j4 & -8 & 6 + j5 \\ -8 & 8 - j2 & 0 \\ -1 & 0 & 1 \end{bmatrix}$$

$$= (8 - j4)(8 - j2) + (-8)(6 + j5)(8 - j2)$$

$$= 50 - j20$$

$$I_2 = \begin{bmatrix} 8 - j4 & -j15 & 6 + j5 \\ -8 & 11.66 \angle 30.96^\circ & 0 \\ -1 & 4 \angle 0 & 1 \end{bmatrix}$$

$$= (8 - j4)(11.66 \angle 30.96^\circ) + (-8)(j15)$$

$$+ (6 + j5)(-32 + 11.66 \angle 30.96^\circ)$$

$$= -58.02 - j186.02$$

=

$$I_2 = \frac{A_2}{\Delta} = \frac{-58.02 - j186.02}{50 - j20}$$

$$= 0.28 - j3.6$$

$$\Delta = 50 - 20j$$

$$A_1 = -182 - 184j$$


$$A_2 = -58 - 186j$$

$$V_o = -j2 \times (I_2 - I_4)$$

$$= -j2 \left\{ (0.28 - j3.6) + 3 \cancel{4.9} \right\}$$

Superposition Theorem

10

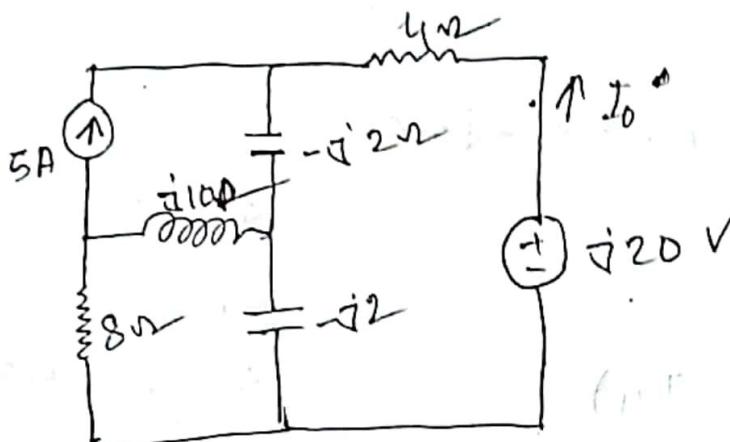

* Find I_o

Solve

$$\begin{aligned}
 & (8 + j10) || (-j2) \\
 &= \frac{(8 + j10)(-j2)}{8 + j10 - j2} \\
 &= (0.25 - j2.25) \text{ n}
 \end{aligned}$$

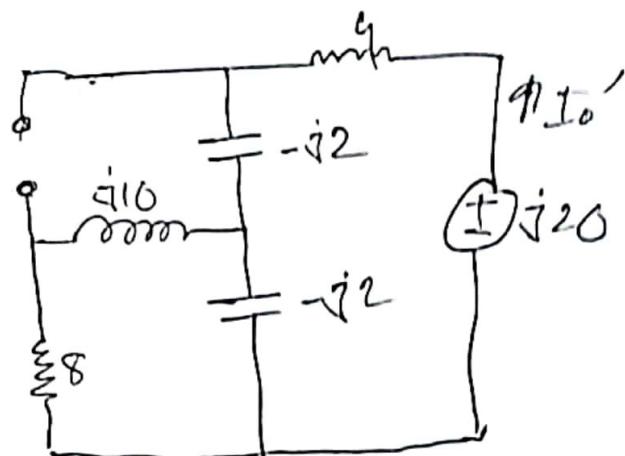


fig (1)

$$\begin{aligned}
 I_o' &= \frac{j20}{(0.25 - j2.25) + (-j2) + 4} \\
 &= 3.32 \angle 135^\circ
 \end{aligned}$$

from mesh - 1,

$$I_1 = 5A$$

mesh - 2

$$8I_2 + \dot{j}10(I_2 - I_1) - \dot{j}2(I_2 - I_3) = 0$$

$$\Rightarrow \underline{8I_2} + \dot{j}10\underline{I_2} - \dot{j}10I_1 - \dot{j}2\underline{I_2} + \dot{j}2\underline{I_3} = 0$$

$$\Rightarrow -\dot{j}10I_1 + (8 + \dot{j}8)I_2 + \dot{j}2I_3 = 0$$

$$\Rightarrow -\dot{j}50 + (8 + \dot{j}8)I_2 + \dot{j}2I_3 = 0 \quad \textcircled{1}$$


mesh - 3

$$-\dot{j}2(I_3 - I_2) - \dot{j}2(I_3 - I_1) + 4I_3 = 0$$

$$\Rightarrow -\dot{j}2\underline{I_3} + \dot{j}2\underline{I_2} - \dot{j}2\underline{I_3} + \dot{j}2I_1 + 4I_3 = 0$$

$$\Rightarrow \dot{j}2I_1 + \dot{j}2I_2 + (4 - \dot{j}4)I_3 = 0 \quad \textcircled{11}$$
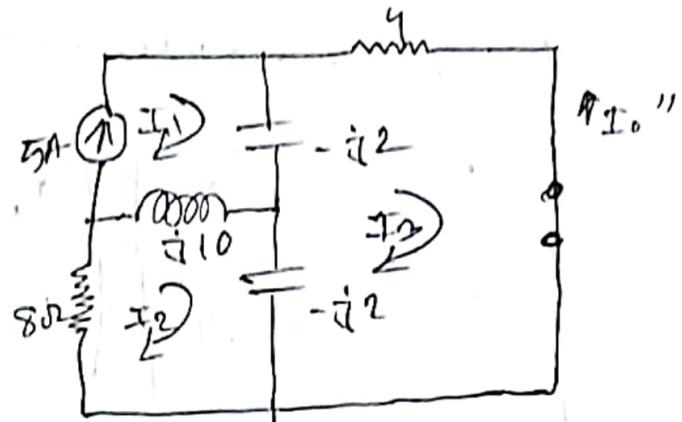
$$\Rightarrow \dot{j}10 + \dot{j}2I_2 + (4 - \dot{j}4)I_3 = 0$$



Using cramer's rule,

$$\begin{bmatrix} 8+j8 & j2 \\ j2 & 4-j4 \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} j50 \\ -j10 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 8+j8 & j2 \\ j2 & 4-j4 \end{bmatrix} = 68$$

$$\Delta_3 = \begin{bmatrix} 8+j8 & j50 \\ j2 & -j10 \end{bmatrix} = 180 - j80 \angle 0^\circ$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{180 - j80}{68} = 2.6 - j1.18$$


$$I_0'' = -I_3 = -2.6 - j1.18 = 2.9 \angle -23.96^\circ A$$

$$\begin{aligned} I_0 &= I_0' + I_0'' \\ &= (-5 + j3.5) A \end{aligned}$$

18 Inductor - short
capacitor - open

11

* find V_o ?

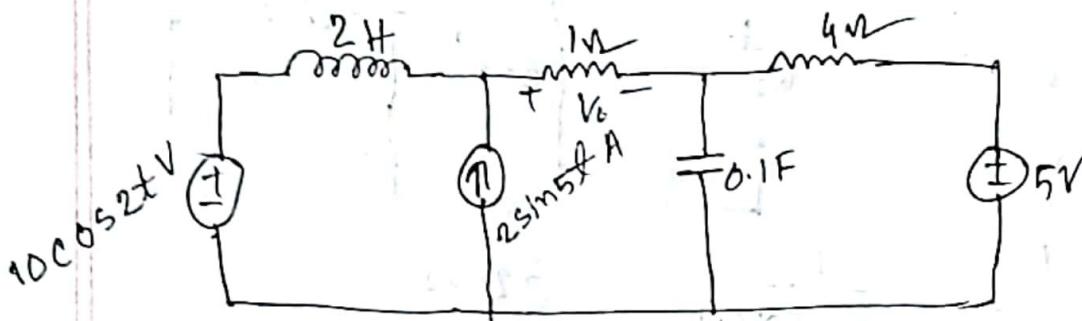

Solve

Using VDR,

$$V_o' = \frac{5 \times 1}{1+4} = 1 \text{ V}$$

$$10 \cos 2t = 10 \cos^{\circ} \text{ V}$$

$$\omega = 2 \text{ rad/s}$$

$$2 \text{ H} = j\omega L = j2 \text{ } \Omega$$

$$0.1 \text{ F} = \frac{1}{j\omega C} = \frac{1}{j2 \times 0.1} = -j5$$

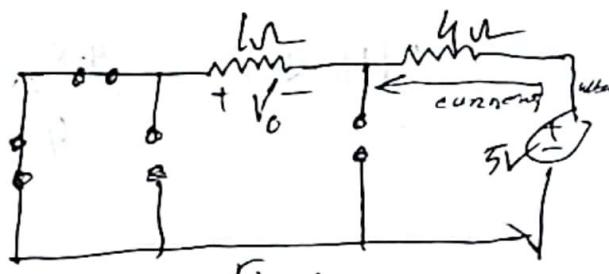


Fig-1

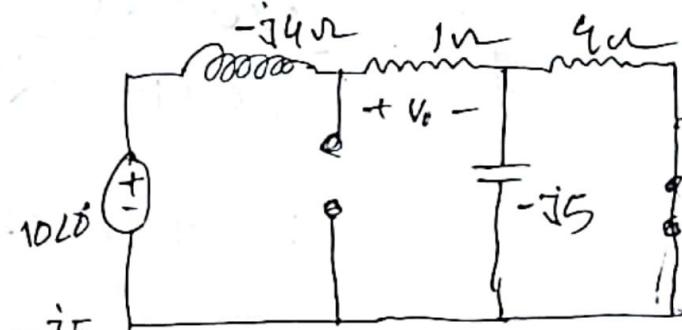


Fig-2

$$V_o''(-j5) = \frac{4 \times (-j5)}{9 - j5} = (2.43 - j1.95) \text{ V}$$

Using VDR,

$$= \frac{10 \cos^{\circ} \times 1}{-j4 + 1 + 2.43 - j1.95}$$

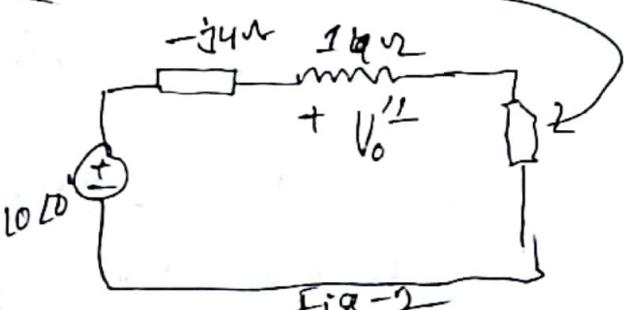


Fig-2

$$V_o'' = 2.14 - j1.27 = 2.49 \angle -30.78^{\circ} \text{ V}$$

$$V_o''(t) = 2.49 \cos(2t - 30.78^{\circ}) \text{ V}$$


$$2\sin 5t / 2\cos^\circ V$$

$$\omega = 5 \text{ rad/s}$$

$$2H = j\omega L$$

$$= j \times 5 \times 2$$

$$= j10 \text{ v}$$

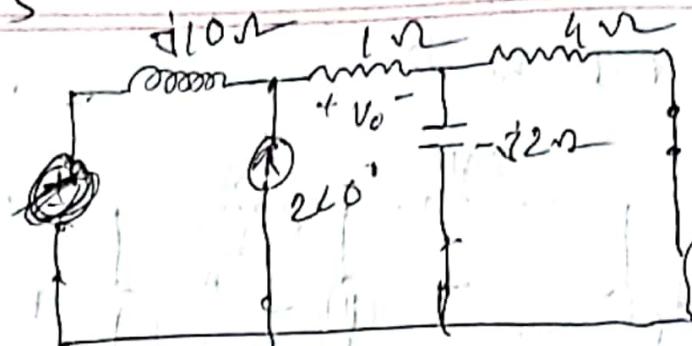


$$0.1F = \frac{1}{j\omega C} = \frac{1}{j \times 5 \times 0.1} = -j2 \Omega$$

$$V_o = \frac{4 \times (-j2)}{4 + j2} = (0.8 - j1.6) \text{ v}$$

Using CDR,
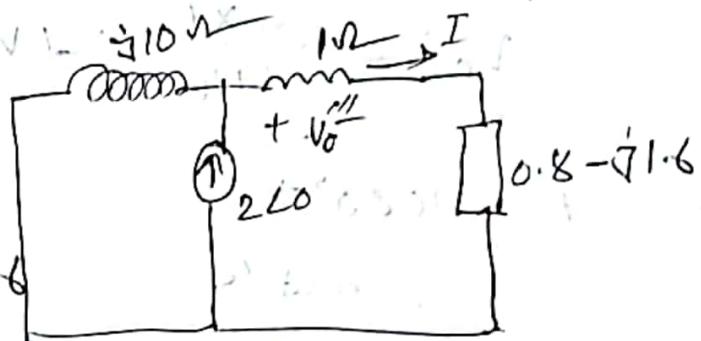
$$I_{\text{CDR}} = \frac{2L\omega \times j10}{j10 + 1 + 0.8 - j1.6}$$



$$= 23.48 \angle 12.09^\circ \text{ A}$$

Using Ohm's law,

$$V_o''' = I \times 1$$

$$= 23.48 \angle 12.09^\circ \text{ v}$$

$$V_o'''(t) = 23.48 \sin(5t + 12.09^\circ) \text{ v}$$



$$V_o = V_o' + V_o'' + V_o'''$$

$$= -1 + 2.49 \cos(2t - 30.78^\circ) + 23.48 \sin(5t + 12.09)$$

Date: 20-08-25

Thevenin's Theorem

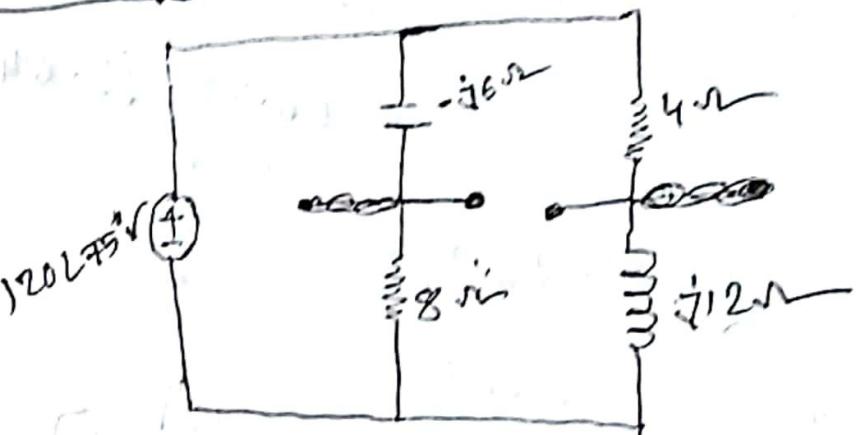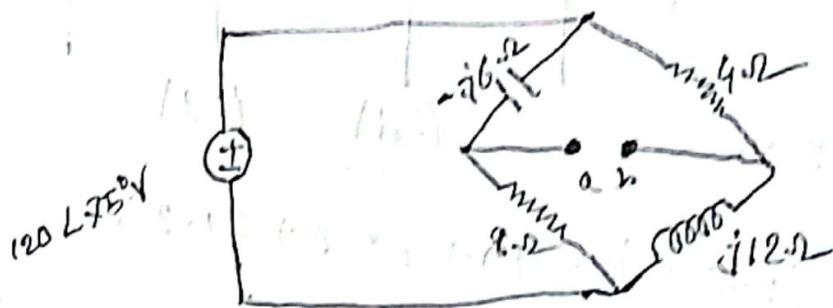
12 Obtain the Thevenin equivalent at terminals a-b.



$$Z_1 = (jG/18) = \frac{-j6 \times 8}{-j6 + 8} = 2.88 - j3.84 \Omega$$


$$Z_2 = (j12/14) = \frac{j12 \times 4}{j12 + 4} = 3.6 + j1.2 \Omega$$
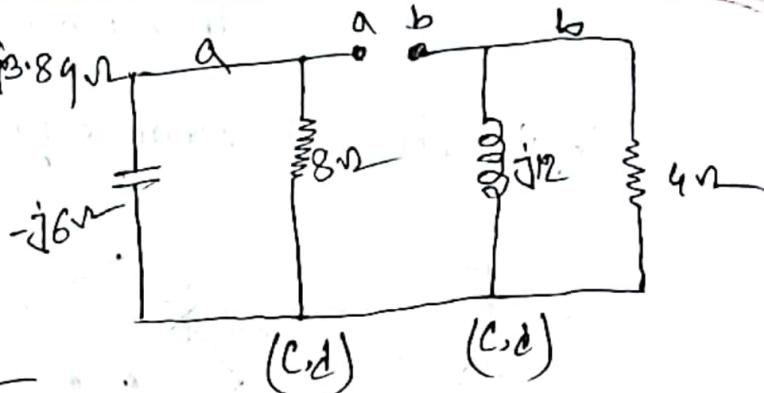
$$Z_{th} = Z_1 + Z_2 = (2.88 - j3.84) + (3.6 + j1.2) \\ = (6.48 - j2.64) \Omega \quad \underline{\underline{Ans}}$$




Using Ohm's Law,
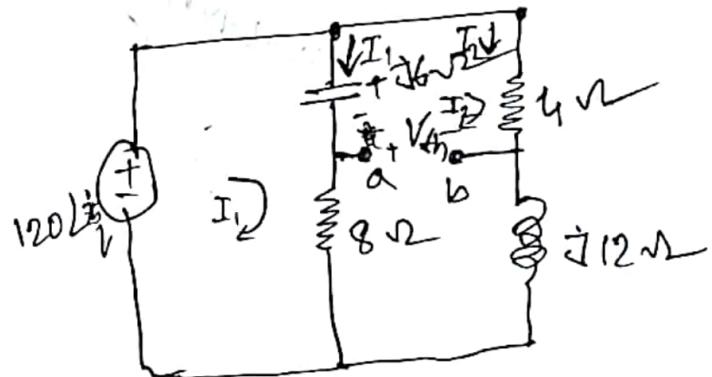
$$I_1 = \frac{120 \angle 75^\circ}{8 - j6} \\ = -4.47 + j11.13$$


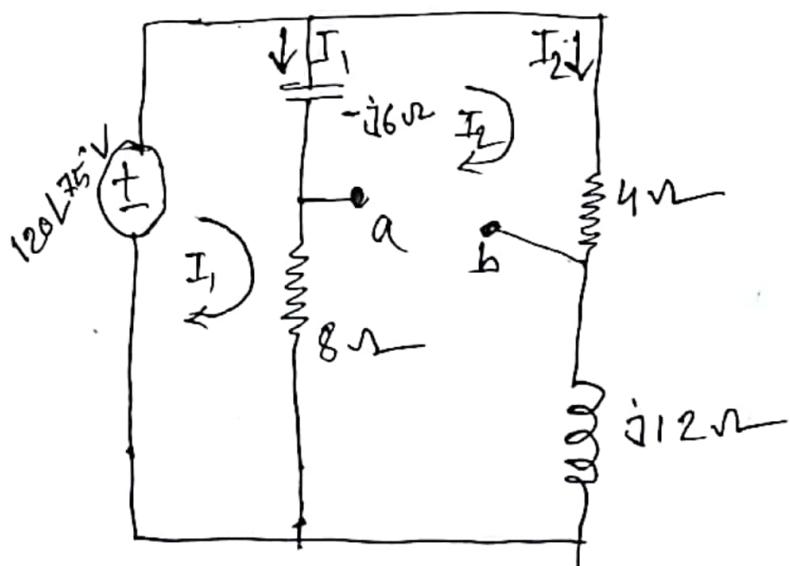
$$I_2 = \frac{120 \angle 75^\circ}{4 + j12} \\ = 9.47 + j0.56$$




Applying KVL, in loop -2,

$$-(-j6)I_1 + I_2 4 = V_{th}$$


$$\Rightarrow V_{th} = j6I_1 + I_2 4$$

$$= j6(-4.47 + j11.13) + \cancel{(0.47 + j0.56) \times 4}$$

$$\therefore V_{th} =$$

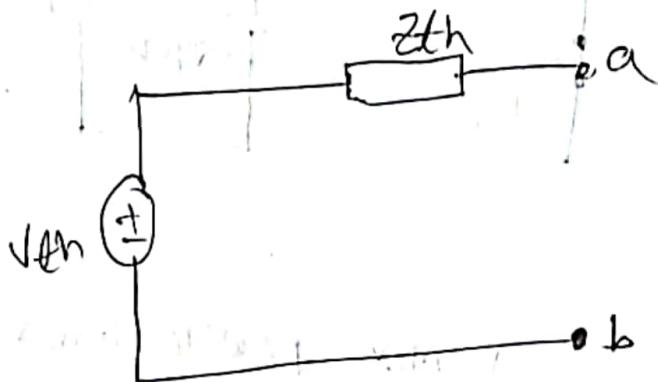

13

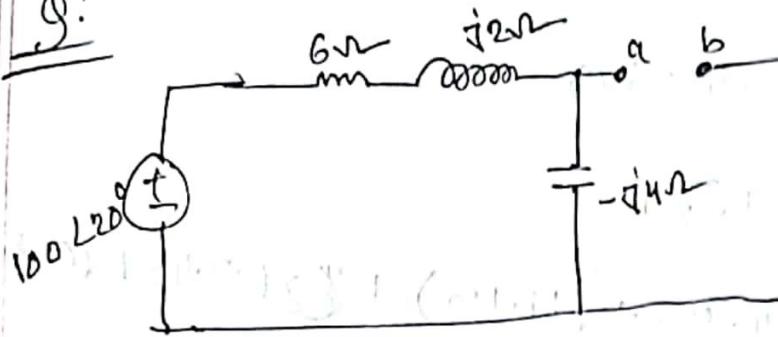

Solve

$$(6 + j2) \parallel (-j4)$$

$$Z_1 = \frac{(6 + j2) \times (-j4)}{6 + j2 - (-j4)}$$


$$= 2.4 - j3.2$$

$$Z_2 = 10 \Omega$$

$$\therefore Z_{th} = Z_1 + Z_2$$

$$= 2.4 - j3.2 + 10$$

$$= 12.4 - j3.2$$

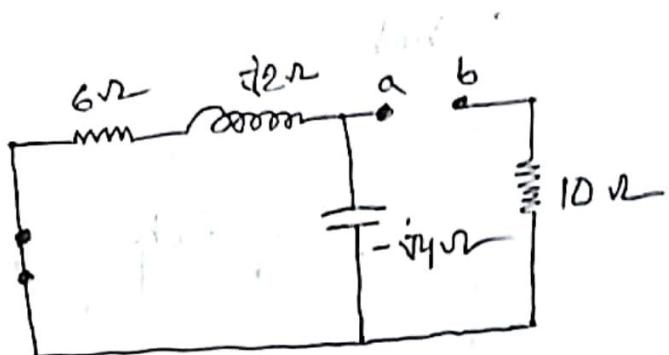

Max power Transfer.

$$Z_L = Z_{th}^* = \frac{12.4 + j3.2}{R_{th}}$$


$$P_{max} = \frac{V_{th}^2}{8R_{th}}$$

$$= \frac{(63.25 \text{ E-3150})^2}{8 \times 12.4}$$

$$= 40.33 \text{ W}$$

Lab → 26 Aug

Qulz → 01 sept

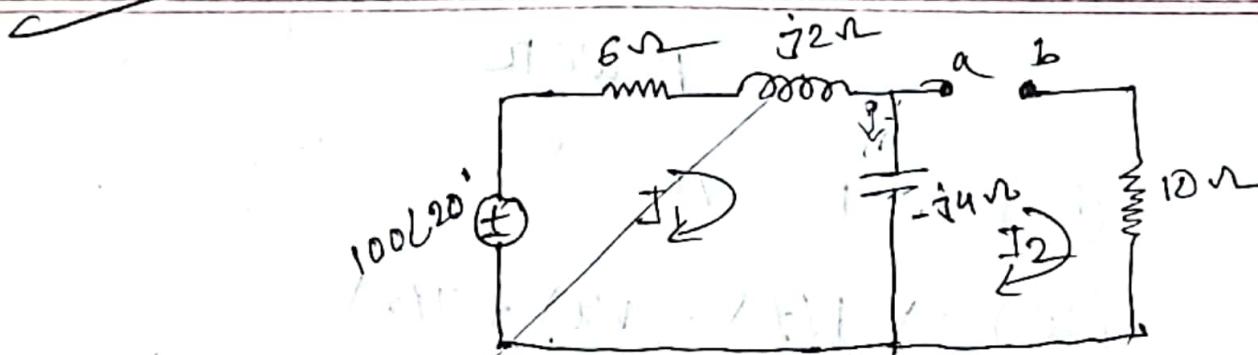

KVL in mesh 1, \rightarrow

$$-100\angle 20^\circ + 6I_1 + j2I_1 - j4(I_1 - I_2) = 0$$

$$\Rightarrow -100\angle 20^\circ + 6I_1 + j2I_1 - j4I_1 + j4I_2 = 0$$

$$\Rightarrow -100\angle 20^\circ + 6I_1 - j2I_1 + j4I_2 = 0$$

$$\Rightarrow -100\angle 20^\circ + (6 - j2)I_1 + j4I_2 = 0$$

Using VDR,

$$V_{th} = \frac{100\angle 20^\circ \times (-j4)}{6 + j2 - j4}$$

$$= \frac{63.24}{V_{th}} \angle -51.56^\circ \text{ V}$$

power

$$(DC) \rightarrow P = VI$$

$$(AC) \rightarrow p(t) = V(t) I(t)$$

$$V(t) = V_m \cos(\omega_m t + \theta_V)$$

POWER

$$(\text{DC}) \rightarrow P = VI$$

$$(\text{AC}) \rightarrow P(t) = v(t) \cdot i(t)$$

$$v(t) = V_m \cos(\omega_m t + \theta_v)$$

$$i(t) = I_m \cos(\omega_m t + \theta_i)$$

$$\text{POWER : } P(t) = v(t) \cdot i(t)$$

$$= V_m \cos(\omega_m t + \theta_v) \times I_m \cos(\omega_m t + \theta_i)$$

$$= V_m I_m \cos(\omega_m t + \theta_v) \cdot \cos(\omega_m t + \theta_i)$$

$$= \frac{V_m I_m}{2} \times 2 \cos(\omega_m t + \theta_v) \cos(\omega_m t + \theta_i)$$

$$= \frac{V_m I_m}{2} \times [\cos(\omega_m t + \theta_v + \omega_m t + \theta_i) + \cos(\omega_m t + \theta_v - \omega_m t - \theta_i)]$$

$$= \frac{1}{2} V_m I_m [\cos(2\omega_m t + \theta_v + \theta_i) + \cos(\theta_v - \theta_i)]$$

$$= \frac{1}{2} V_m I_m \times [\cos(2\omega_m t + 2\theta_v)]$$

$$= V_m I_m \cos(\omega_m t + \theta_v)$$

↓ Instantaneous power

Avg power:

$$P_{avg} = \frac{1}{2} k_m I_m \cos(\theta_v - \theta_i)$$

Given,

$$v(t) = 120 \cos(377t + 45^\circ) \text{ V and } i(t) = 10 \cos(377t - 10^\circ)$$

Find the instantaneous power and the average power absorbed by the passive linear network.

Solve

The instantaneous power,

$$P(t) = v(t) I(t)$$

$$= 120 \cos(377t + 45^\circ) \cdot 10 \cos(377t - 10^\circ)$$

$$= \frac{120 \times 10}{2} \times 2 \cos(377t + 45^\circ) \cos(377t - 10^\circ)$$

$$= \frac{120 \times 10}{2} \times [\cos(377t + 45^\circ + 377t - 10^\circ) + \cos(377t + 45^\circ - 377t + 10^\circ)]$$

$$= 600 [\cos(754t + 35^\circ) + \cos(55^\circ)]$$

$$\therefore P(t) = 600 \cos(754t + 35^\circ) + 600 \times \cos(55^\circ)$$

$$= 600 \cos(754t + 35^\circ) + 344.14 \text{ W}$$

The average power:

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} \times 120 \times 10 \times \cos(45 - (-10))$$

$$= 344.2 \text{ W}$$

2

Calculate the average power absorbed by an impedance $z = 30 - j70 \Omega$. When a voltage $V = 120 \angle 0^\circ$ is applied across it.

Solve

$$\text{Given, } z = 30 - j70 \Omega ; V = 120 \angle 0^\circ$$

$$I = \frac{120}{30 - j70} = 1.5 \angle 66.8^\circ$$


Average power,

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$


$$= \frac{1}{2} \times 120 \times 1.5 \times \cos(0^\circ - 66.8^\circ)$$

$$= 37.1 \text{ W}$$

Phasor diagram of v & I :

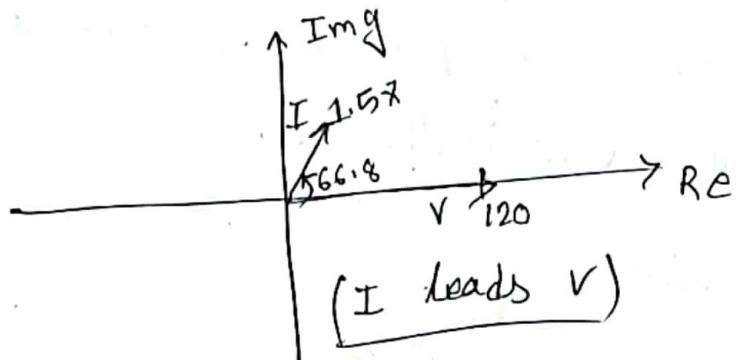

3

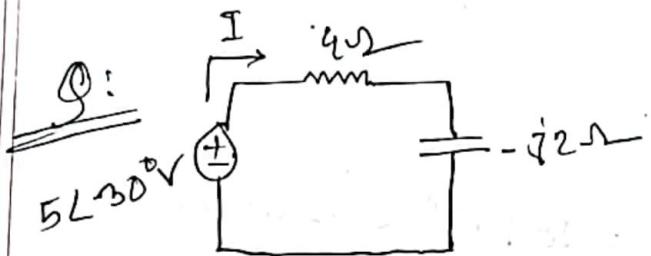

Find the avg power supplied by the source and the avg power absorbed by the resistor.

Solve

$$I = \frac{5\angle 30^\circ}{4 + j2} = 0.6 + j0.9 = 1.11 \angle 56.56^\circ$$

$$V_1 = 4.44 \angle 56.56^\circ$$

$$V_2 = 2.22 \angle -33.44^\circ$$


$$\begin{aligned} P_{avg_1} &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \\ &= \frac{1}{2} \times 5 \times 1.11 \times \cos(30^\circ - 56.56^\circ) \\ &= 2.48 \text{ W} \end{aligned}$$

$$\begin{aligned} P_{avg_1} &= \frac{1}{2} \times 4.44 \times 1.11 \times \cos(56.56^\circ - 56.56^\circ) \\ &= 3.19 \text{ W} \end{aligned}$$

$$\begin{aligned} P_{avg_2} &= \frac{1}{2} \times 2.22 \times 1.11 \times \cos(-33.44^\circ - 56.56^\circ) \\ &= 0.62 \text{ W} \end{aligned}$$

4

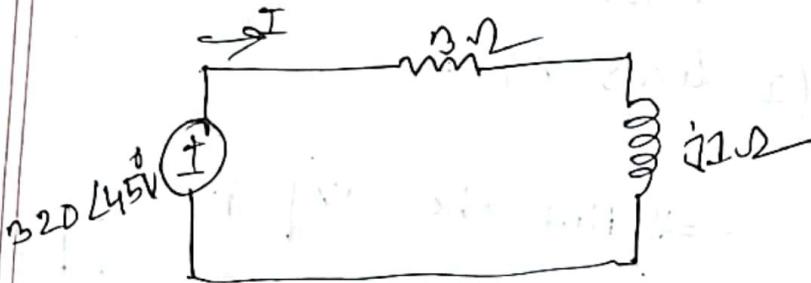Q: Find the average power supplied by the source and the avg power absorbed by the Resistor and the inductor.



Solve -

$$I = \frac{320 \angle 45^\circ}{3 + j1} = 101.19 \angle 26.56^\circ$$

$$P_{avg} = \frac{1}{2} \times 320 \times 101.19 \times \cos(45 - 26.56)$$

$$= \cancel{+546.69} \text{ W} \quad 15359.11 \text{ W} = 15.35 \text{ kW}$$

$$V_R = 303.57 \angle 26.56^\circ$$

$$V_I = 101.19 \angle 116.56^\circ$$

$$P_{Ravg} = \frac{1}{2} \times 303.57 \times 101.19 \times \cos(26.56^\circ - 26.56^\circ)$$
$$= \cancel{1546} \quad 15359.11 \text{ W} = 15.35 \text{ kW}$$

$$P_{Iavg} = \frac{1}{2} \times 101.19 \times 101.19 \times (11.56 - 26.56)$$
$$= 0 \text{ W}$$

$$Z = R + jX \rightarrow \text{reactive power} \\ \rightarrow \text{real power}$$

~~The~~ Complex power: $S = P + jQ = V_{n.m.s} I_{n.m.s}^*$
~~Q.~~ $= |V_{n.m.s}| |I_{n.m.s}| \angle \theta_v - \theta_i$

~~Apparent power:~~

$$S_A = |V_{n.m.s}| |I_{n.m.s}| \\ = \sqrt{P^2 + Q^2}$$



Real Power: $P = \text{Re}(S) = S_A \cos(\theta_v - \theta_i)$

~~Imag~~ / Reactive power: $Q = \text{Im}(S) = S_A \sin(\theta_v - \theta_i)$

power factor: $\text{pf} = \frac{P}{S_A} = \cos(\theta_v - \theta_i)$

~~Ex~~

$$Z = R + jX$$

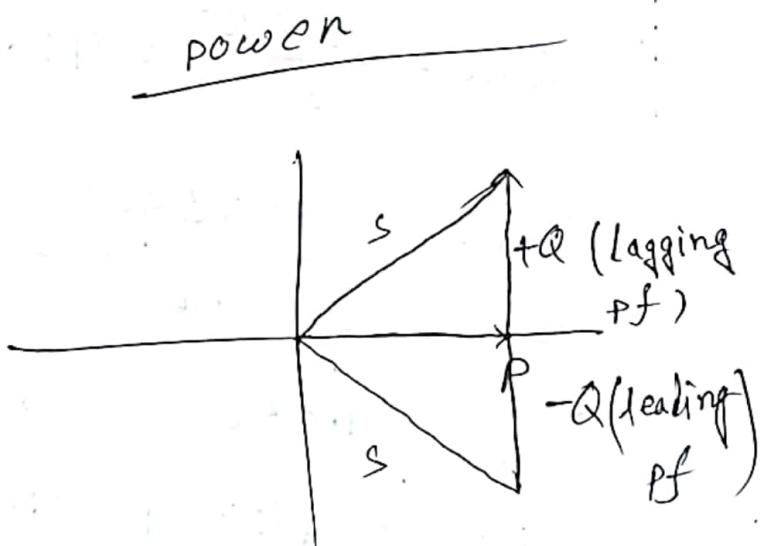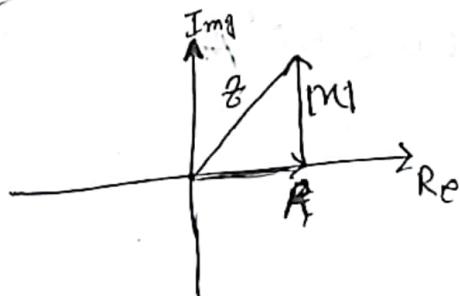

5 Q: The voltage across a load is $V(t) = 60 \cos(\omega t - 10^\circ)$ and the current through the element in the direction of the voltage drop is $i(t) = 1.5 \cos(\omega t + 50^\circ)$ A

Find: a) The complex and apparent power.
 b) The real and the reactive power and the power factor and the load impedance.

solve $V(t) = 60 \cos(\omega t - 10^\circ) = 60 \angle -10^\circ$ V

$$I(t) = 1.5 \cos(\omega t + 50^\circ) = 1.5 \angle 50^\circ$$
 A

$$V_{\text{r.m.s.}} = \frac{60 \angle -10^\circ}{\sqrt{2}} = 42.42 \angle -10^\circ$$
 V

$$I_{\text{r.m.s.}} = \frac{1.5 \angle 50^\circ}{\sqrt{2}} = 1.06 \angle 50^\circ$$
 A

$$I_{\text{r.m.s.}}^* = 1.06 \angle -50^\circ$$
 A

The complex power:

$$S = P + jQ = V_{\text{r.m.s.}} I_{\text{r.m.s.}}^*$$

$$= 42.42 \angle -10^\circ \times 1.06 \angle -50^\circ$$
 A


$$= 44.96 \angle -60^\circ$$
 VA = (22.48 - j38.92) VA

apparent power.

$$S_A = |V_{\text{r.m.s}}| |I_{\text{r.m.s}}|$$

$$= 44.96 / \sqrt{P^2 + Q^2}$$

$$= \sqrt{(22.48)^2 + (-38.92)^2}$$

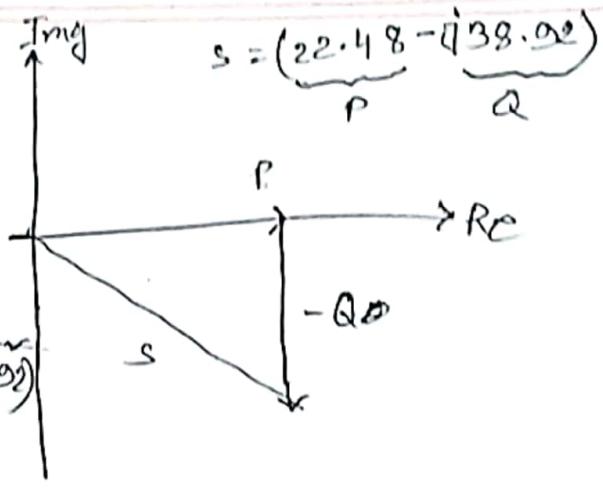

b) Real power:

$$P = \text{Re}(s) = S_A \cos(\theta_V - \theta_I)$$

$$= 44.96 \times \cos(-10 - 50)$$

$$= 22.48 \text{ W}$$

$$Q = \text{Im}(s) = S_A \sin(\theta_V - \theta_I)$$

$$= 44.96 \times \sin(-10 - 50)$$

$$= -38.92 \text{ VAR}$$

power factor:

$$\text{pf} = \cos(\theta_V - \theta_I)$$

$$= \cos(-10 - 50)$$

$$= 0.5 \text{ leading } (-Q)$$

~~→ Impedance~~

$$Z = \frac{V}{I}$$

$$= \frac{60 \angle -10^\circ}{1.5 \angle 50^\circ}$$

$$= 20 - j34.6$$

$$= 40 \angle -68^\circ$$

Date: 27-08-25

Q1 A load Z draws 12kVA at a power factor of 0.856 lagging from a 120 V r.m.s sinusoidal source calculate.

6

(Pf)

a) The average and reactive power delivered to the load.

b) The peak current, and c) the load impedance.

Solve

a) Given, $P_f = 0.856$

$S_A = 12 \text{ kVA}$

$V_s = 120 \text{ V.r.m.s}$

$$P_f = \frac{P}{S_A}$$

$$\Rightarrow P = P_f \times S_A$$

$$= 0.856 \times 12000$$

$$= 10272 \text{ W}$$

$$= 10.272 \text{ kW}$$

↓
average power.

* $\theta_V - \theta_i = \theta$

$\therefore P_f = \cos \theta = 0.856$

$$\therefore \theta = \cos^{-1}(0.856)$$

$$= 31.12^\circ$$

* Reactive power:

$$Q = S_A \sin \theta$$

$$= 12000 \times \sin(31.12^\circ)$$

$$= 6203.8 \text{ VAR}$$

$$= 6.2038 \text{ kVAR}$$

b) peak current:

Complex power,

$$S = P + jQ$$

$$= 10.27 + j6.20$$

$$S = V_{r.m.s} I_{r.m.s}$$

$$\Rightarrow 10.27 + j6.20 = 120 \cdot I_{r.m.s}$$

$$\therefore I_{r.m.s}^* = \frac{10.27 + j6.20}{120}$$

$$= 0.09 \angle 31.11^\circ A$$

$$\therefore I_{r.m.s} = \frac{100}{0.09 \angle -31.11^\circ A}$$

c) Impedance,

$$Z = \frac{V_{r.m.s}}{I_{r.m.s}}$$

$$= \frac{120}{100 \angle -31.11^\circ} = \text{J} \Omega$$

$$= 1.2 \angle 31.11^\circ \text{ J} \Omega$$

$$\text{Impedance} = 6.20 \angle 31.11^\circ$$


$$(\text{impedance}) \cdot 120 = 72.0$$

$$= 72.0 \angle 31.11^\circ$$

Amplification

Amplification

Q2
7

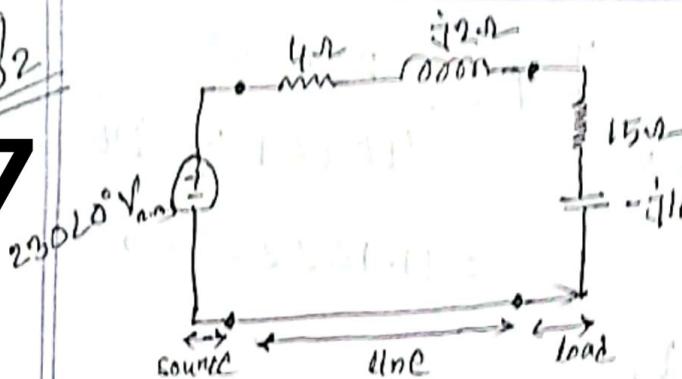

If in the following circuit
find the real and reactive
power absorbed by
a) source, b) the line
c) the load.

Solve

$$I = \frac{230\angle 20^\circ}{4 + j2 + 15 - j10} = 12.04 \angle -6.000^\circ A \\ = 11.16 \angle 22.83^\circ A$$

b) $V_{\text{Line}} = I Z_{\text{Line}}$

$$= 11.16 \angle 22.83^\circ \\ = 12.04 \angle -6.000^\circ \times (4 + j2) \\ = 53.84 \angle 20.5^\circ \text{ V}_{\text{n.m.s}} \\ = 49.0 \angle 40.4^\circ \text{ V}_{\text{n.m.s}}$$

$$S = V_{\text{Line}} I^*$$

$$= 49.0 \angle 40.4^\circ \times 11.16 \\ \angle -22.83$$

$$= 555.98 \angle 26.56^\circ$$

$$= 497.20 + j248.60 \text{ VA}$$

$$P = 497.20, Q = 248.60$$

c) $V_{\text{Load}} = I Z_{\text{load}}$

$$= 11.16 \angle 22.83^\circ \\ = 12.04 \angle -6.000^\circ \times (15 - j10) \\ = 217.05 \angle -30.60^\circ \text{ V}_{\text{n.m.s}} \\ = 201.18 \angle -10.9^\circ \text{ V}$$

a) $S = V_{\text{n.m.s}} I_{\text{n.m.s}}$

$$= 230\angle 20^\circ \times 12.04 \angle -6.000^\circ \\ = 2760.2 \angle 6.000^\circ$$

Real P:

$$P = 2363.50 \text{ W}$$

$$Q = -895.02 \text{ VAR}$$

$$= 2566.8 \angle -22.83^\circ \text{ VA}$$

$$= (2363.50 - j895.02) \text{ VA}$$

$$a) S = V_{\text{r.m.s}} I_{\text{r.m.s}}^*$$

$$= 230 \angle 0^\circ \times 11.16 \angle -22.83^\circ$$

$$= 2566.8 \angle -22.83^\circ \text{ VA}$$

$$= (2363.59 - j995.02) \text{ VA}$$

$$P = 2363.59 \text{ W}$$

$$Q = -995.02 \text{ VAR}$$

$$b) V_{\text{line}} = I Z_{\text{line}}$$

$$= 11.16 \angle 22.83^\circ \times (4 + j2)$$

$$= 49.9 \angle 49.4^\circ \text{ V}_{\text{r.m.s}}$$

$$I = \frac{230 \angle 0^\circ}{4 + j2 + 15 - j10}$$

$$= 11.16 \angle 22.83^\circ$$

$$c) V_{\text{load}} = 11.16 \angle 22.83^\circ \times (15 - j10)$$

$$= 201.00 \angle -10.86^\circ \text{ V}$$

$$S = V_{\text{load}} I^*$$

$$= 201.00 \angle -10.86^\circ \times 11.16 \angle -22.83^\circ$$

$$= 1864.83 - j1243.2$$

$$S = V_{\text{line}} I^*$$

$$= 49.9 \angle 49.4^\circ \times 11.16 \angle -22.83^\circ$$

$$= 555.08 \angle 26.56^\circ$$

$$P = 497.29 + j248.60 \text{ VA}$$

$$P = 497.29 \text{ W}$$


$$Q = 248.60 \text{ VAR}$$

$$P = 1864.83 \text{ W}$$

$$Q = -1243.2 \text{ VAR}$$

T1

8

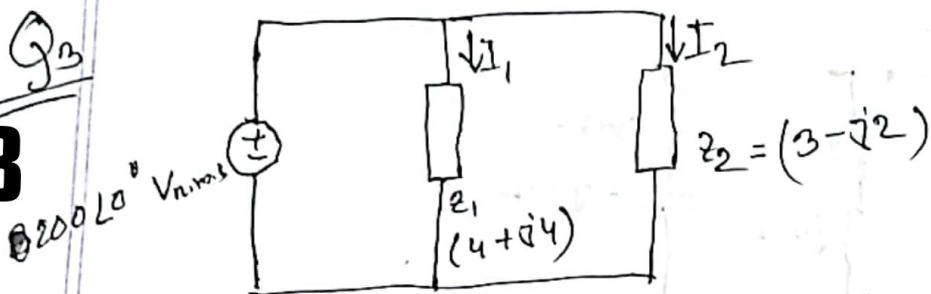

Find the complex power, real power and the reactive power across all the elements of the following circuit. and find total complex power.

Solve

$$I_1 = \frac{200 \angle 0^\circ \times (3 - j2)}{4 + j4 + 3 - j2} = 99.05 \angle -49.6^\circ = 25 - j25$$

$$I_2 = \frac{200 \angle 0^\circ \times (4 + j4)}{4 + j4 + 3 - j2} = 155.4 \angle 29.05^\circ = 55.47 \angle 33.6^\circ$$

$$S_1 = V_{n.m.s} I_1^* = 200 \angle 0^\circ \times (25 - j25) \rightarrow P_1 = \text{lagging}$$

$$= 4999.24 + j4999.24$$


$$S_2 = V_{n.m.s} I_2^* = 200 \angle 0^\circ \times (55.47 \angle 33.6^\circ)$$

$$= 9229.10 - j6154.82 \rightarrow P_2 = \text{leading}$$

Total complex power:

$$S = S_1 + S_2 =$$

G4
9

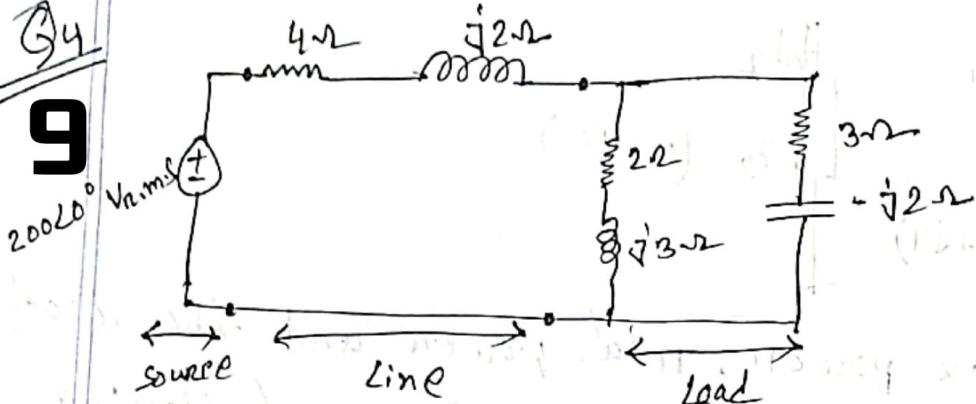


Find the real and reactive power of the load.

Solve

$$Z_{load} = (2+j3)(3-j2) = \frac{(2+j3) \times (3-j2)}{2+j3+3-j2}$$
$$= 2.5 + j0.5 \Omega$$

$$I = \frac{200\angle 0^\circ}{4+j2+(2.5+j0.5)}$$

$$= 20.1 \angle -18.7^\circ$$

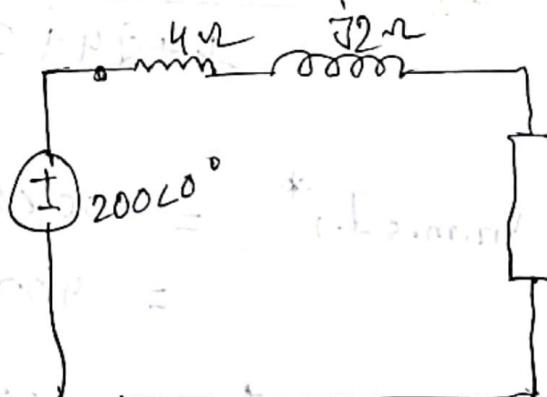

$$V_{load} = I \times Z_{load}$$

$$= 20.1 \angle -18.7 \times (2.5 - j0.5)$$

$$= 24.19 \angle -38^\circ$$

$$\begin{aligned}
 S &= V_{\text{load}} I^* \\
 &= 74.19 \angle -30^\circ \times 29.1 \angle 18.7^\circ \\
 &= 2112.077 - j423.03 \\
 \therefore P &= 2112.077 \text{ W} \\
 Q &= 423.03 \text{ VAR}
 \end{aligned}$$

Practice problem

$$11.1 \rightarrow 11.11$$

Power

- * $P_{\text{avg}} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$ [average power]
- * $P(t) = V(t) \cdot I(t)$ [instantaneous power]
- * $S = P + jQ = V_{\text{rms}} I_{\text{rms}}^*$ [complex power]
- * $S_A = |V_{\text{rms}} I_{\text{rms}}| = \sqrt{P^2 + Q^2}$ [apparent power]
- * [Real power], $P = \text{Re}(S) = S_A \cos(\theta_v - \theta_i)$
- * [Reactive power], $Q = \text{Im}(S) = S_A \sin(\theta_v - \theta_i)$
- * [Power factor] $\text{PF} = \frac{P}{S_A} = \cos(\theta_v - \theta_i)$
- * [Impedance] $Z = \frac{V}{I}$