



East West University

Lab Report

Semester: Summer-2025

Course Title: Electrical Circuits

Course Code: CSE209

Sec: 01

Expt No: 03

Expt Name: Bias Point Detail Analysis of DC Circuit With Independent Sources Using PSpice Schematics.

Group No: 05

Submitted by-

Md. Arifur Rahman Razu

2024-3-60-503

Submitted to-

Dr. Sarwar Jahan
Associate Professor
Department of CSE
East West University

Date of Submission: 10-08-2025

Example of Circuit Solution

(i) Using the steps explained above draw and simulate the following circuit.


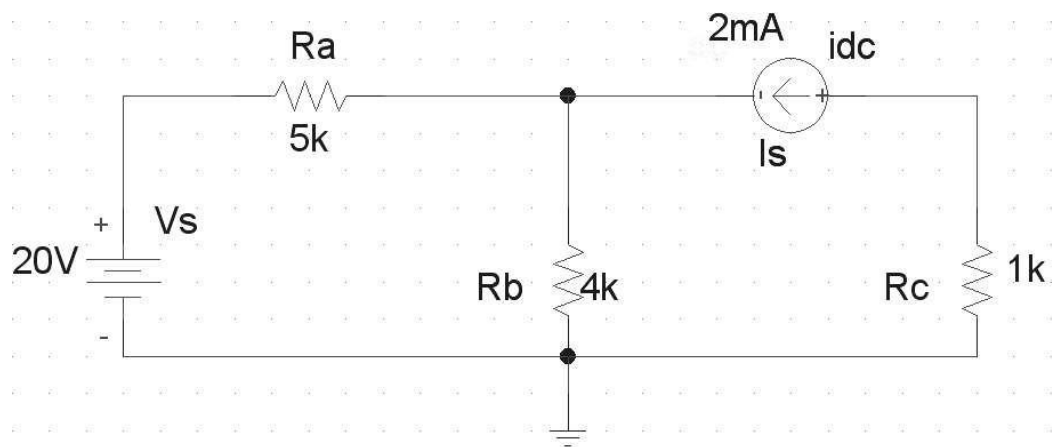


Figure 1: Example circuit.

(ii) In “Analysis Setup” window only enable “Bias Point Detail” option.

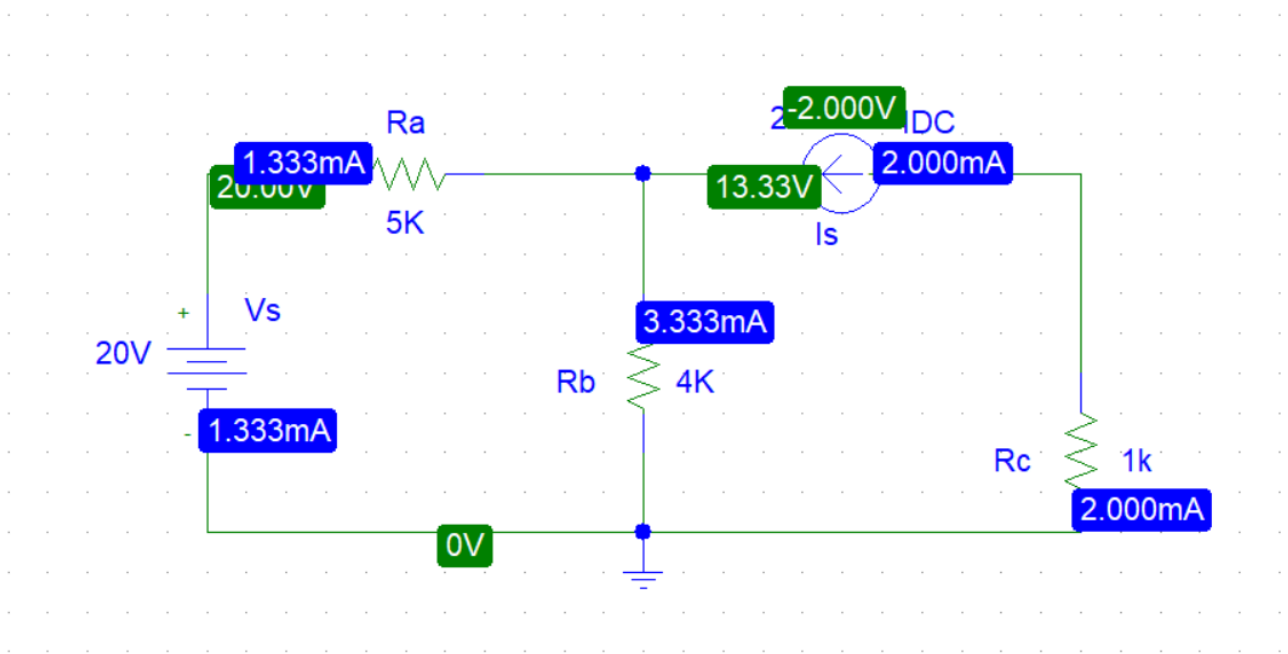(iii) To examine the node voltages click the **V** button and to examine the current through each part click the **I** button.



- (iv) You can also generate the netlist from the schematic by using the Analysis>Create Netlist menu. To see the created netlist use Analysis>Examine Netlist menu. Study the structure of the netlist and relate the entries in the netlist with your schematic circuit diagram.

Lab Practice Problem:

(i)

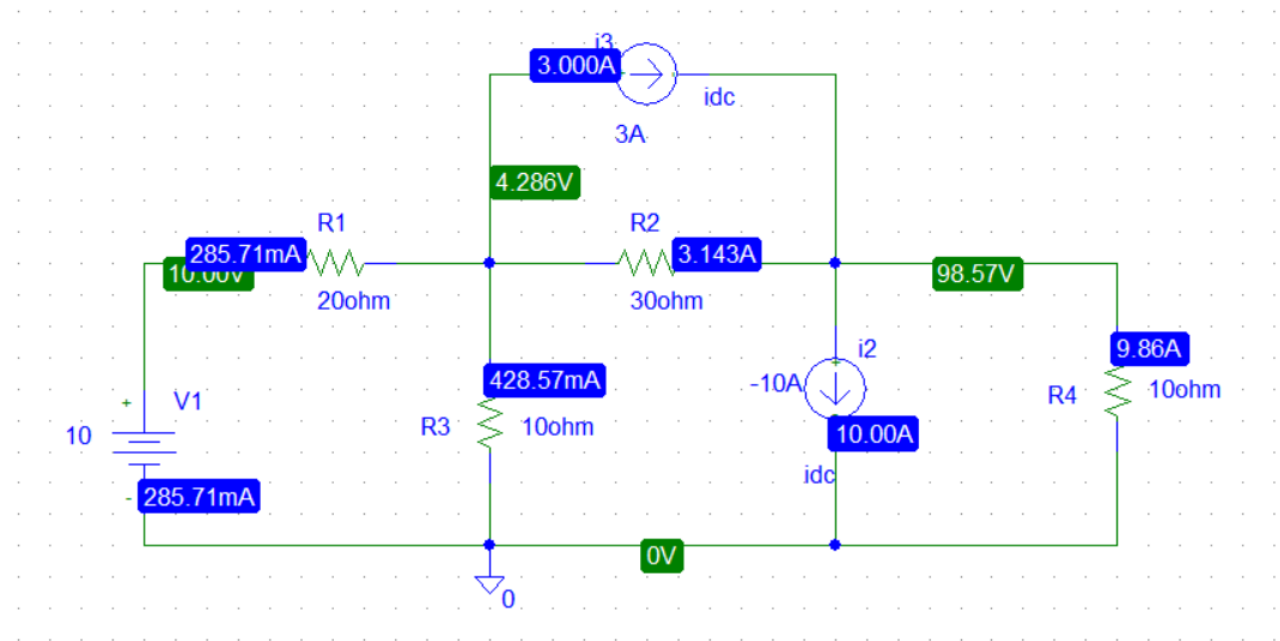


Figure 2. Circuit for lab practice

Post Lab :

1. Theoretically calculate all the currents and the voltages for the circuit shown in Figure 2.

Here, $V_1 = 10\text{ V}$ KCL at node 2:

$$\{(V_2 - V_1) / 20\} + \{(V_2 - V_3) / 30\} + V_2 / 10 = -3$$

$$\text{Or, } -0.5 + 0.183 V_2 - 0.033 V_3 = -3$$

$$\text{Or, } 0.183 V_2 - 0.033 V_3 = -2.5 \dots\dots\dots (1) \text{ KCL at node 3:}$$

$$\{(V_3 - V_2) / 30\} + V_3 / 10 = 3 - (-10)$$

$$\text{Or, } -0.033 V_2 + 0.133 V_3 = 13 \dots\dots\dots (2)$$

By solving equation equations (1) and (2), We get, $V_2 = 4.150\text{ V}$ and $V_3 = 98.774\text{ V}$ By using the value of V_2, V_3 :

$$I_1 = (V_1 - V_2) / R_1 = (10 - 4.2857) / 20 = 285.71\text{mA}$$

$$I_4 = (V_2 - V_3) / R_2 = (4.2857 - 98.57) / 30 = (-94.2843) / 30 = -3.142\text{ A}$$

$$I_5 = V_2 / R_3 = 4.2857 / 10 = 428.57\text{ mA}$$

$$I_6 = V_3 / R_4 = 98.57 / 10 = 9.857\text{ A}$$

2. Compare the theoretical solution of the circuit shown in Figure 2 with the solutions obtained from PSpice.

Values obtained from theoretical solution,

$V_1 = 10 \text{ v}$,

$V_2 = 4.150 \text{ v}$, $V_3 = 98.774 \text{ v}$, $i_1 = 285.71 \text{ mA}$, $i_4 = -3.142 \text{ A}$, $i_5 = 428.57 \text{ mA}$, $i_6 = 9.857 \text{ A}$