



East West University

Lab Report

Semester: Summer-2025

Course Title: Electronic Circuits

Course Code: CSE209

Sec: 01

Expt. No: 2

Expt. Name: Series-Parallel DC Circuit and Verification of Kirchhoff's Laws.

Group No: 5

Group Members:

Student Name	Student Id
Nusrat Jahan Fiha	2023-2-60-137
Purnima Ghosh	2023-3-60-522
Zahin Abdullah Adib	2024-1-60-164
Md. Arifur Rahman Razu	2024-3-60-503

Submitted by-

Md. Arifur Rahman Razu
ID: 2024-3-60-503

Submitted to-

Dr. Sarwar Jahan
Associate Professor
Department of Computer Science & Engineering
East West University

Date of Submission: 06/08/2025

Experiment NO: 02

Experiment Name: Series-Parallel DC Circuit and Verification of Kirchhoff's Laws.

Objectives:

1. To learn analysis of dc series-parallel circuit.
2. To verify Kirchhoff's Voltage Law (KVL).
3. To verify Kirchhoff's Current Law (KCL).

Theory:

Kirchhoff's Voltage Law (KVL) states that **the sum of the voltage rises around a closed path** is equal to the sum of the voltage drops. The KVL can be written in the following mathematical form:

$$\Sigma V \text{ rises} = \Sigma V \text{ drops}$$

The sum of the voltage rises and the sum of the voltage drops are to be calculated in a given direction (normally in the clockwise direction). For example, in the simple series circuit of Figure 1, there are two voltage sources (E_1 and E_2) and two resistors (R_1 and R_2). The voltage drops across the two resistors are V_1 and V_2 , respectively. If we write KVL equation for the clockwise direction, then the KVL equation will be

$$E_1 - E_2 = V_1 + V_2.$$

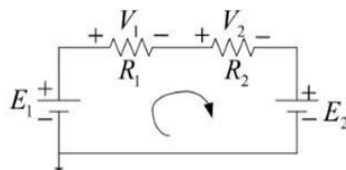


Figure 1. A simple series dc circuit.

Kirchhoff's Current Law (KCL) states that **the sum of the currents entering a node of a circuit is equal to the sum of the currents leaving the node**. The KCL can be written in the following mathematical form:

$$\Sigma I_i = \Sigma I_o.$$

For example, in the simple parallel circuit of Figure 2, there is a voltage source (E) and two resistors (R_1 and R_2). The source current drawn from the voltage source is I_s . The currents through resistors R_1 and R_2 are I_1 and I_2 , respectively. If we consider the node a of the circuit, then I_s enters the node and I_1 and I_2 are leaving the node. Then, the KCL equation for the node a is

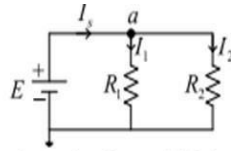


Figure 2. A simple parallel de circuit.
 $I_s = I_1 + I_2$

A series-parallel circuit is one that is formed by a combination of series and parallel resistors. For solving series-parallel circuits, parallel combinations of resistors and series combination of resistors are clearly identified. Then the series-parallel reduction method is used to determine the values of the circuit variables. For example, in the simple series-parallel circuit of Figure 3, the resistors R_1 and R_2 are in parallel and this parallel combination is in series with the resistor R_1 . As the resistors R_2 and R_3 are in parallel, $V_2 = V_3$. Let $R_p = R_2 \parallel R_3$. Then, the equivalent resistance of the series-parallel combination is $R_{eq} = R_1 + R_p$. Now, the circuit variables can be calculated using the formulas

$$I_1 = \frac{E}{R_{eq}}$$

$$V_1 = I_1 R_1$$

$$V_2 = V_3 = I_1 R_p$$

$$I_2 = \frac{V_2}{R_2}$$

$$I_3 = \frac{V_3}{R_3}$$

The KVL equations for the circuit of Figure 3 can be written as

$$E = V_1 + V_2$$

$$E = V_1 + V_3$$

The KCL equation for the circuit of Figure 3 can be written as

$$I_1 = I_2 + I_3$$

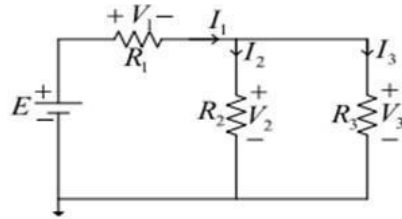


Figure 3. A simple series-parallel dc circuit.

Circuit Diagram:

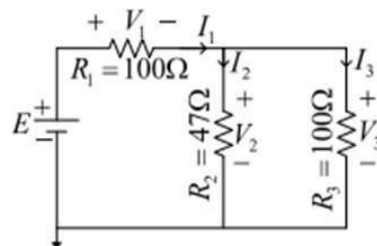


Figure 4. Circuit for experiment.

Pre-Lab Report Questions:

1. Theoretically calculate the values of E , V_1 , V_2 , V_3 , I_1 , I_2 and I_3 of the circuit of Figure 4 with $E = 3V$.

Ans:

Given that,

$$R_1 = 100\Omega$$

$$R_2 = 47\Omega$$

$$R_3 = 100\Omega$$

$$E = 3V$$

Here, R_2 & R_3 is in parallel connection.

$$\text{So, } R_p = \left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} \Omega$$

$$= \left(\frac{1}{47} + \frac{1}{100} \right)^{-1} \Omega$$

$$= 31.98\Omega$$

Now, R_p and R_1 is in series connection.

$$\text{So, } R_{eq} = R_p + R_1$$

$$= (31.98 + 100)\Omega$$

$$= 131.98 \Omega$$

We know that,

$$I_1 = \frac{E}{R_{eq}}$$

$$= \frac{3}{131.98} \text{ A}$$

$$= 0.022A$$

$$\text{So, } I_1 = 0.022A$$

Here,

$$V_{111} = I_1 R_1 = 0.022 \times 100 = 2.27V$$

$$V_2 = I_2 R_2 = 0.022 \times 31.98 = 0.73 \text{ V}$$

$$V_3 = I_3 R_3 = 0.022 \times 31.98 = 0.73 \text{ V}$$

$$I_2 = \frac{V_2}{R_2} = \frac{0.73}{47} = 0.015 \text{ A}$$

$$I_3 = \frac{V_3}{R_3} = \frac{0.73}{100} = 0.0073 \text{ A}$$

2. From the calculated values, show that (i) $V_2 = V_3$, (ii) KVL holds, that is, $E = V_1 + V_2$, and (iii) KCL holds, that is, $I_1 = I_2 + I_3$.

Ans:

i.

$$V_2 = V_3 = 0.72 \text{ V}$$

ii.

From the calculated value we get that,

$$\begin{aligned} & V_1 + V_2 \\ &= (2.23 + 0.72) \text{ V} \\ &= 3 \text{ V} \end{aligned}$$

iii

$$I_2 + I_3 = (0.015 + 0.007)A$$

$$= 0.022A$$

Experimental Datasheet

Measured Value of E (V)	Measured Value of V_1 (V)	Measured Value of V_2 (V)	Measured Value of V_3 (V)	Measured Value of I_1 (mA)	Measured Value of I_2 (mA)	Measured Value of I_3 (mA)	Measured Value of Resistance (Ω)
3	2.3	0.9	0.7	22	7	13	$R_1 = 97.8$
							$R_2 = 98.9$
							$R_3 = 48.2$
5	3.7	1.3	1.1	33	11	20	$R_1 = 97.8$
							$R_2 = 98.9$
							$R_3 = 48.2$

Post-Lab Report Questions:

1. Calculate the values of V_1 , V_2 , V_3 , I_1 , I_2 and I_3 of the circuit of Figure 4 using measured values of E , R_1 and R_2 . Compare the calculated values with the measured values and give reason if any discrepancy is found.

Ans:

Given, $E = 3V$

Here, R_2 & R_3 are in parallel.

So,

$$\begin{aligned}\frac{1}{R_p} &= \frac{1}{R_2} + \frac{1}{R_3} \\ &= \frac{1}{98.9} + \frac{1}{49.2} \Omega\end{aligned}$$

$$R_p = 32.85 \Omega$$

And R_1 & R_p are in series,

$$R_{eq} = R_1 + R_p = 97.8 \Omega + 32.85 \Omega = 130.62 \Omega$$

Now,

$$\begin{aligned}I_1 &= \frac{E}{R_{eq}} \\ &= \frac{3}{130.62} A\end{aligned}$$

$$\begin{aligned}&= 0.023 A \\ &= 23 mA\end{aligned}$$

$$V_1 = I_1 R_1 = 0.023 \times 97.8 = 2.25 V$$

$$V_2 = V_3 = I_1 R_p = 0.023 \times 32.85 = 0.76 V$$

$$\begin{aligned}I_2 &= \frac{V_2}{R_2} \\ &= \frac{0.76}{98.9} A\end{aligned}$$

$$= 0.008 A = 8 mA$$

$$I_3 = \frac{V_3}{R_3}$$

$$= \frac{0.76}{48.2} \text{ A}$$

$$= 0.016 \text{ A} = 16 \text{ mA}$$

Measured Value of E (V)	Measured Value of V_1 (V)	Measured Value of V_2 (V)	Measured Value of V_3 (V)	Measured Value of I_1 (mA)	Measured Value of I_2 (mA)	Measured Value of I_3 (mA)	Measured Value of Resistances (Ω)
3	2.3	0.9	0.7	22	7	13	$R_1=97.8$ $R_2=98.9$ $R_3=48.2$
Calculated Value of E (V)	Calculated Value of V_1 (V)	Calculated Value of V_2 (V)	Calculated Value of V_3 (V)	Calculated Value of I_1 (mA)	Calculated Value of I_2 (mA)	Calculated Value of I_3 (mA)	Calculated Value of Resistances (Ω)
3	2.25	0.76	0.76	23	8	16	$R_1= 100$ $R_2= 47$ $R_3= 100$

Table 2. The discrepancy between theoretical and measured values of V_1 , V_2 , V_3 , I_1 , I_2 , I_3 , R_1 ,

The calculated and measured values for voltages V_1 , V_2 , and V_3 show relatively small differences, which could be attributed to measurement inaccuracies. However, the calculated and measured values for currents I_1 , I_2 , and I_3 exhibit significant discrepancies, suggesting potential measurement errors or incorrect units. It's essential to double-check the measurement equipment, units, and calibration to ensure accurate readings for current values.

2. From the calculated values of V_1, V_2, V_3, I_1, I_2 and I_3 , show that (i) $V_2 = V_3$, (ii) $E = V_1 + V_2$ (KVL), and (iii) $I_1 = I_2 + I_3$ (KCL).

Ans:

From the calculated values,

$$V_1 = 2.25V$$

$$V_2 = 0.76V$$

$$V_3 = 0.76V$$

$$I_1 = 0.023A$$

$$I_2 = 0.008A$$

$$I_3 = 0.016A$$

$$E = 3V$$

i

Here, we can see that $V_2 = V_3$; (As R_2 & R_3 are in parallel and in parallel circuit voltages are Same).

ii

Again,

$$V_1 + V_2 = 2.25V + 0.76V = 3.1V$$

So, we can say that, $E = V_1 + V_2$

iii

Here,

$$I_2 + I_3 = 0.008A + 0.016 A$$

$$= 0.024A$$

$$= I_1$$

So, we can say that, $I_1 = I_2 + I_3$

Discussion:

In this experiment, we verified Kirchhoff's voltage law (KVL) and Kirchhoff's current law (KCL) using a series-parallel DC circuit. Theoretical calculations showed that the total voltage and current matched the expected values, satisfying both KVL and KCL. In the experiment setup, measured voltages were close to calculated ones, but some differences in current values were observed, likely due to measurement errors or component tolerances. Overall, the experiment confirmed the validity of Kirchhoff's Laws and improved our understanding of series-parallel circuit behavior.